


Use Excel To Calculate A-D Level-Shifter Resistor Values

AUBREY KAGAN, *Emphatec Inc, Markham, Ontario, Canada*

• • • akagan@emphatec.com

Many times, the need arises to interface single-supply analog-to-digital converters (ADCs) and comparators to real-world signals like ± 5 V. Of course, it's possible to condition the signal using operational and/or instrumentation amplifiers. But few engineers realize that it's often possible to achieve the level shifting using a resistor network (Fig. 1).

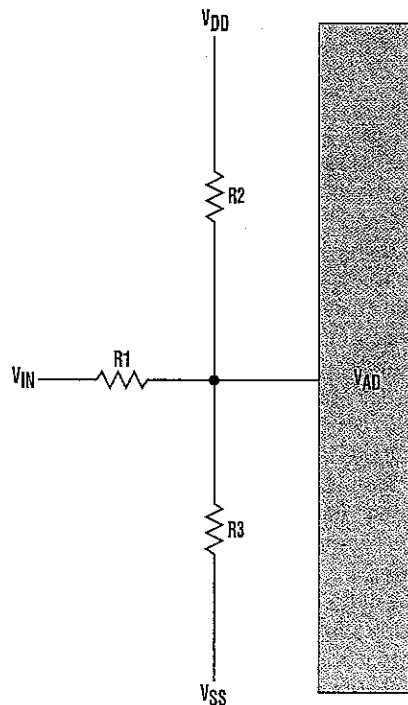Critics of this technique point out that the resistor network can load the source voltage and cause distortion. We can build this limitation into Microsoft Excel to ensure the resistor values don't overload the input. Another possible concern is that some ADCs won't run properly with a high source impedance, so you would probably have to buffer with a suitable operational amplifier.



1. This is the basic resistor level shifter circuit used for the ADC. It's used to derive the equations employed in the Excel spreadsheet.

To calculate resistor values, we need to use Kirchhoff's Law: The sum of currents into a node is zero. Considering the node at the junction of the three resistors, we can write:

$$(V_{IN} - V_{AD})/R1 + (V_{DD} - V_{AD})/R2 + (V_{SS} - V_{AD})/R3 = 0 \quad (1)$$

As an example, let us assume $V_{DD} = 5$ V, $V_{SS} = 0$ V, $V_{IN} = \pm 5$ V, and the ADC input must go from 0 to 2.5 V. For $V_{IN} = -5$ V, we want $V_{AD} = 0$ V. So we can substitute the values in Equation 1:

$$(-5/R1) + (5/R2) = 0 \quad (2)$$

For $V_{IN} = +5$ V, we want the input to be 2.5 V, so substituting in Equation 1:

$$(2.5/R1) + (2.5/R2) - (2.5/R3) = 0 \quad (3)$$

We have two equations with three unknowns, leaving one degree of freedom. Now we can go ahead and solve this. If we reduce the generalization so that V_{SS} is always 0, we can rearrange Equation 1 as follows:

$$V_{AD} = [(-R2 \times R3 \times V_{IN}) - (R1 \times R3 \times V_{DD})] / [(-R1 \times R2) - (R2 \times R3) - (R1 \times R3)] \quad (4)$$

Each time we do this though, it's a tedious process. But Excel has a feature aptly called "Solver," which will trivialize the whole exercise once it's set up. To use Solver, you must enable it as follows:

In Windows, go to Control Panel and select the Add/Remove Software option. Select the Microsoft Office entry, and then opt for changing or updating the installation. Find Excel in the list and for the Solver Add-in, select "Run from my computer." Follow the prompts to complete the installation. Now start Excel. Click on Tools, followed by Add-Ins, and enable the Solver Add-In. Follow whatever installation prompts occur (if any)

	A	B	C
1	Level Shifter For A/D Converter		
2			
3			
4			
5	Supply Voltage, Vdd	5.00	
6	VinMax	10.00	
7	VinMin	-5.00	
8	VadMin	1.00	
9	VadMax	2.50	
10	R1	116666	
11	R2	38758	
12	R3	19434	
13			
14	Kirchoff's Law: Minimum Condition	0.00	
15	Kirchoff's Law: Maximum Condition	0.00	
16			
17	Vin	10.00	
18	Vad	2.50	
19			
20	IinMax (mA)	0.06	
21	IinMin (mA)	-0.05	

2. Once loaded into Excel, the worksheet appears as shown here.

After loading the worksheet, ADinput.xls, which can be found at www.electronicdesign.com, open it to reveal Figure 2. The input parameters are in cells B5 through B9. Cell B14 contains Equation 1 suitably modified for the minimum condition as follows:

$$=((VinMin-VadMin)/RE1)+((Vdd-VadMin)/RE2)-(VadMin/RE3)$$

Similarly cell B15 is modified for the maximum condition:

$$=((VinMax-VadMax)/RE1)+((Vdd-VadMax)/RE2)-(VadMax/RE3)$$

Cells B20 and B21 contain the formula for the input current. Notice that it sources when the maximum input voltage is applied and sinks for the minimum.

To invoke Solver, click on Tools | Solver and then make sure the entry parameters are as in Figure 3. Solver will modify cells B10 through B12, trying to keep cells B14 and B15 at zero and cells

