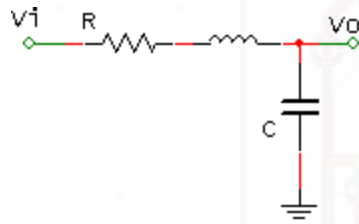


2nd Order Transient Response

- Start with a second order circuit (typically an inductor and a capacitor, or two of each).



- We get a second order differential equation.

$$\frac{d^2 v_o(t)}{dt^2} + \frac{R}{L} \frac{dv_o(t)}{dt} + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_i(t)$$

- First order method from last lab is not helpful, but methods from class are!
- Assume homogeneous response is of the form Ae^{st} .
- Find characteristic values (“s”); for second order circuit we expect two.
- For constant input (this lab) assume particular solution is a constant.

Homogeneous Response

- Rewrite differential equation (with no input):

$$\frac{d^2 v_o(t)}{dt^2} + \frac{R}{L} \frac{dv_o(t)}{dt} + \frac{1}{LC} v_o(t) = 0$$

$$\frac{d^2 v_o(t)}{dt^2} + 2\zeta\omega_0 \frac{dv_o(t)}{dt} + \omega_0^2 v_o(t) = 0$$

- Assume homogeneous response is of the form Ae^{st} .

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0$$

$$s_{1,2} = \frac{-2\zeta\omega_0 \pm \sqrt{2\zeta\omega_0^2 - 4\omega_0^2}}{2}$$
$$= -\zeta\omega_0 \pm \omega_0 \sqrt{\zeta^2 - 1}$$

- Three cases of interest with passive circuits.

$\zeta > 1$: two distinct real roots, overdamped

$\zeta = 1$: two distinct real roots, critically damped

$0 \leq \zeta < 1$: two distinct complex roots, underdamped

- We will consider only first (overdamped) and third (underdamped) cases.

Overdamped Case ($\zeta > 1$)

This is the easy case (for calculations, but not in lab)

- Find roots.

$$s_{1,2} = -\zeta\omega_0 \pm \omega_0\sqrt{\zeta^2 - 1}$$

- Write homogeneous response (constants are unknown).

$$\begin{aligned} v_{o,h}(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ &= A_1 e^{t/\tau_1} + A_2 e^{t/\tau_2} \end{aligned}$$

$$\tau_{1,2} = \frac{1}{-\zeta\omega_0 \pm \omega_0\sqrt{\zeta^2 - 1}}$$

Underdamped Case ($0 \leq \zeta < 1$)

This is the easy case (in lab, but not for calculations)

- Find roots.

$$\begin{aligned} s_{1,2} &= -\zeta\omega_0 \pm \omega_0\sqrt{\zeta^2 - 1} \\ &= -\zeta\omega_0 \pm j\omega_0\sqrt{1 - \zeta^2} \\ &= -\alpha \pm j\omega_d \quad (\text{book's notation}) \end{aligned}$$

- Write homogeneous response. There are several forms, use whichever is convenient (constants are unknown).

$$\begin{aligned} v_{o,h}(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (A_1, A_2 \text{ complex}) \\ &= e^{-\zeta\omega_0 t} B_1 \cos \omega_0 \sqrt{1 - \zeta^2} t + B_2 \sin \omega_0 \sqrt{1 - \zeta^2} t \\ &= C e^{-\zeta\omega_0 t} \cos \omega_0 \sqrt{1 - \zeta^2} t + \phi \end{aligned}$$

Particular, Complete Response

- For unit step input, particular response = constant.

$$v_{o,p}(t) = K$$

- Complete response (overdamped):

$$\begin{aligned} v_o(t) &= v_{o,p}(t) + v_{o,h}(t) \\ &= K + A_1 e^{s_1 t} + A_2 e^{s_2 t} \end{aligned}$$


- Complete response (underdamped):

$$\begin{aligned} v_o(t) &= v_{o,p}(t) + v_{o,h}(t) \\ &= K + C e^{-\zeta \omega_0 t} \cos \omega_0 \sqrt{1 - \zeta^2} t + \phi \end{aligned}$$

- Note: K is determined by input and differential equation. Constants of homogeneous response are determined by initial conditions.

Initial Conditions


For this circuit, and step input:

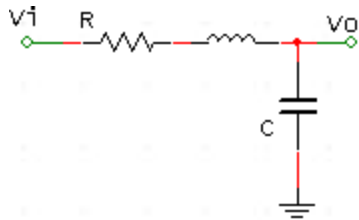

$$\frac{d^2 v_o(t)}{dt^2} + \frac{R}{L} \frac{dv_o(t)}{dt} + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_i(t)$$


$$v_o(0^+) = \dots? \quad v_o(0^+) = 0$$

$$\left. \frac{dv_o(t)}{dt} \right|_{t=0^+} = \dots? \quad \left. \frac{dv_o(t)}{dt} \right|_{t=0^+} = 0$$

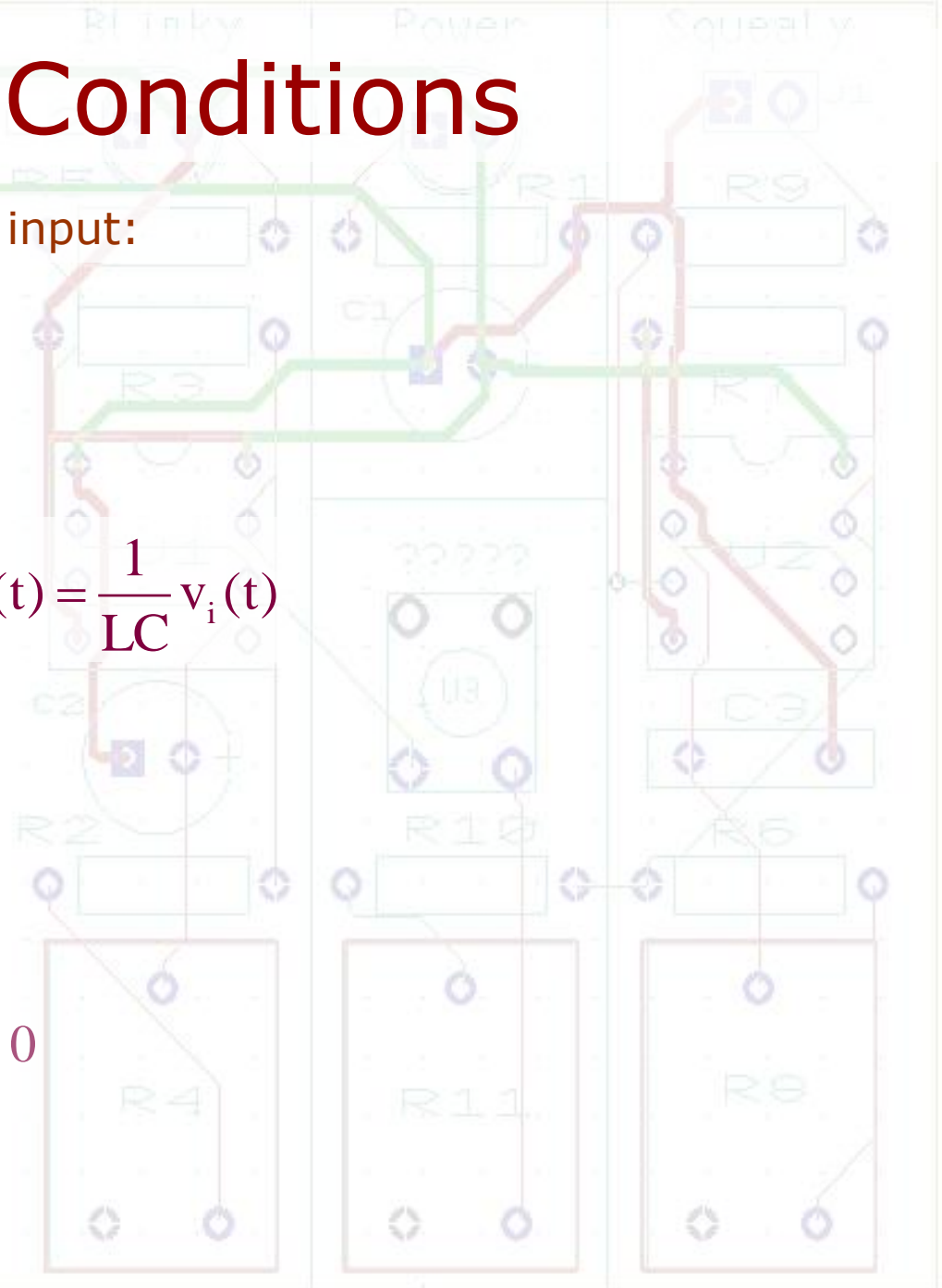

Effect of ζ

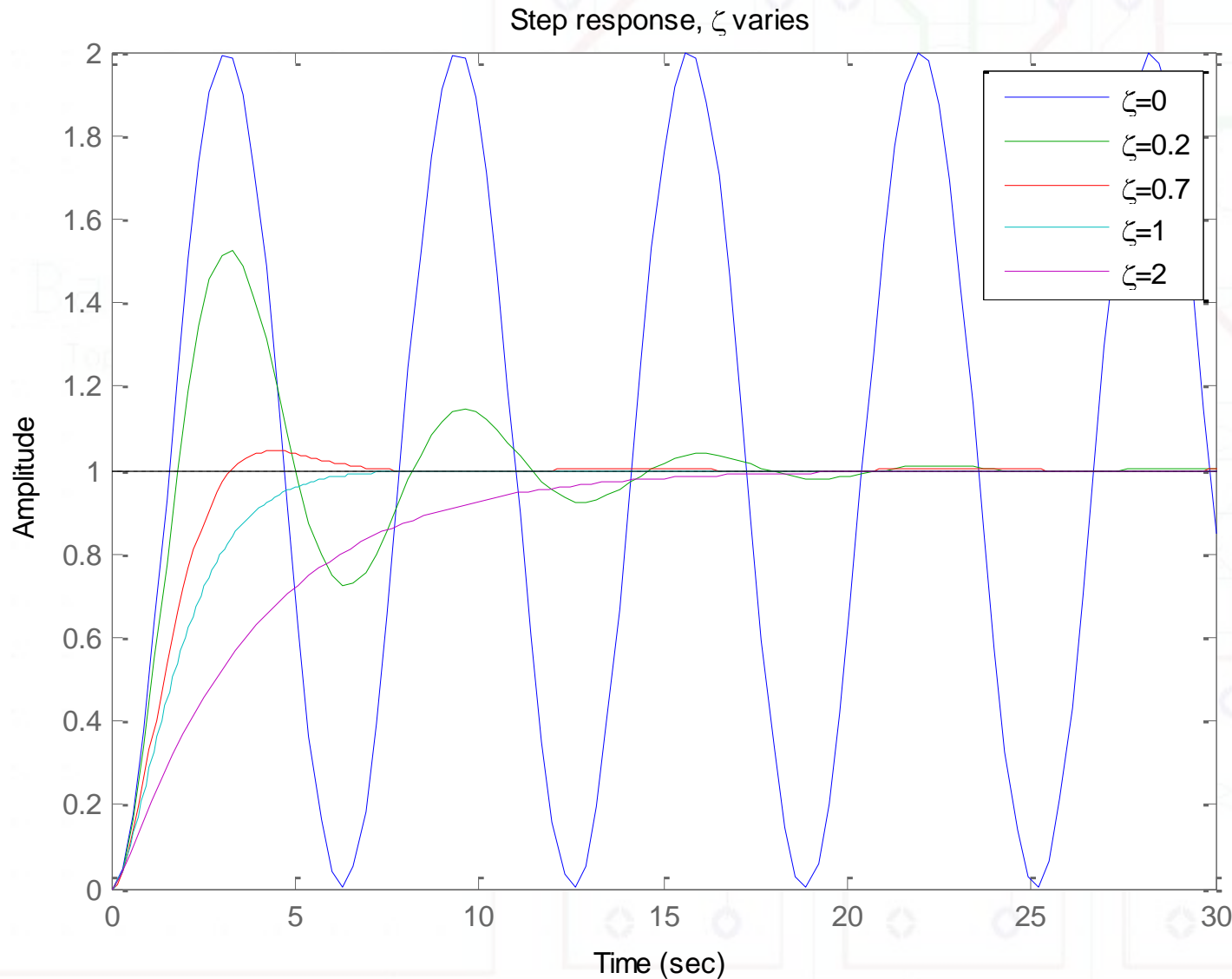
Increasing ζ denotes increasing damping (ζ determines nature of response)



Effect of ω_0

Increasing ω_0 denotes increasing speed (ω_0 determines speed of response)


Step response, ω_n varies

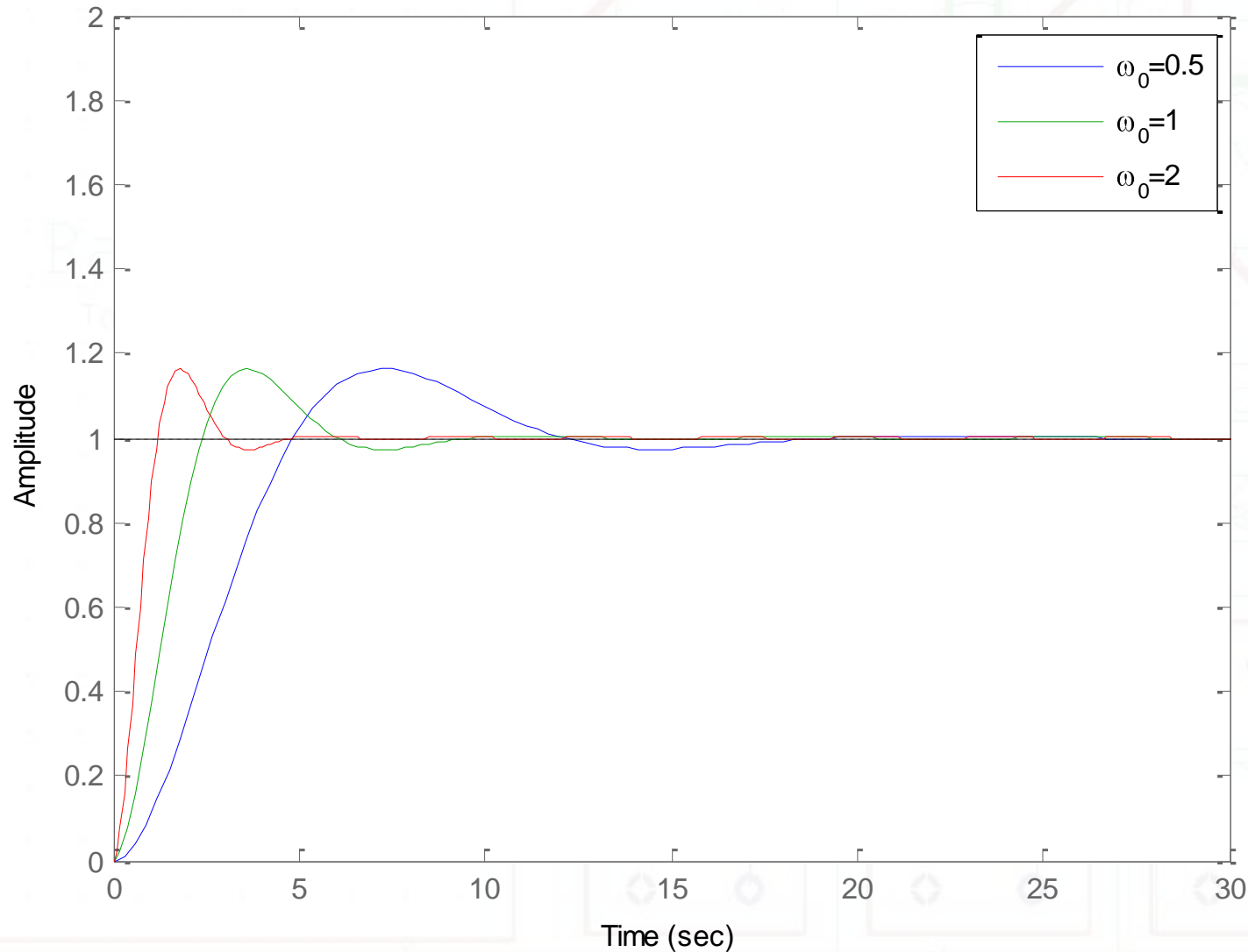

In-Lab Measurements (ω_d)

(underdamped case only)

Measuring ω_d

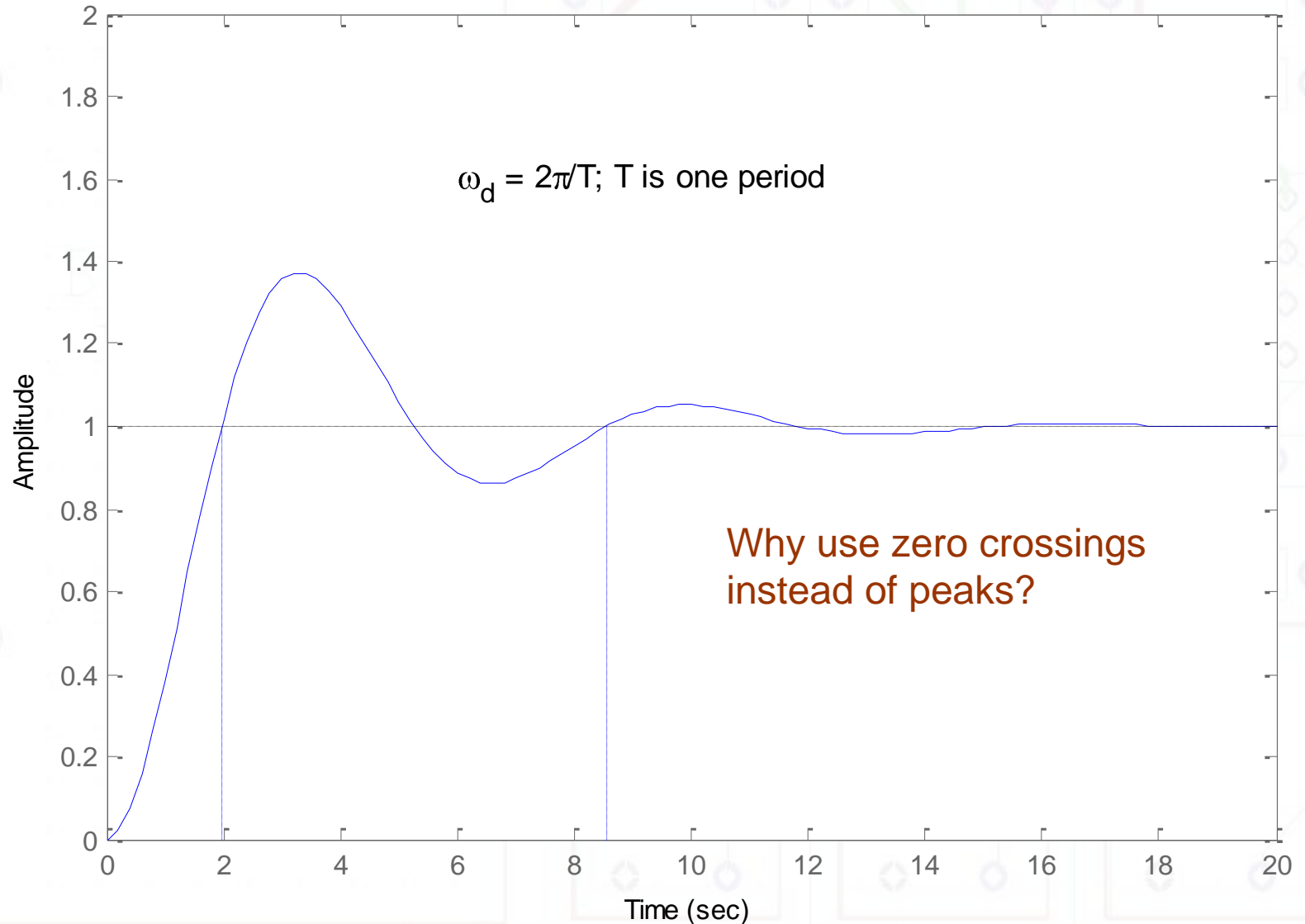

In-Lab Measurements (α)

(underdamped case only)

$$y_1 = a + b \cdot e^{-\alpha \cdot t_1}$$


$$y_2 = a + b \cdot e^{-\alpha \cdot t_2}$$

$$\frac{y_1 - a}{y_2 - a} = \frac{b \cdot e^{-\alpha \cdot t_1}}{b \cdot e^{-\alpha \cdot t_2}}$$
$$= e^{-\alpha \cdot t_1 - t_2}$$

$$\log\left(\frac{y_1 - a}{y_2 - a}\right) = -\alpha \cdot t_1 - t_2$$

This is called the logarithmic decrement.
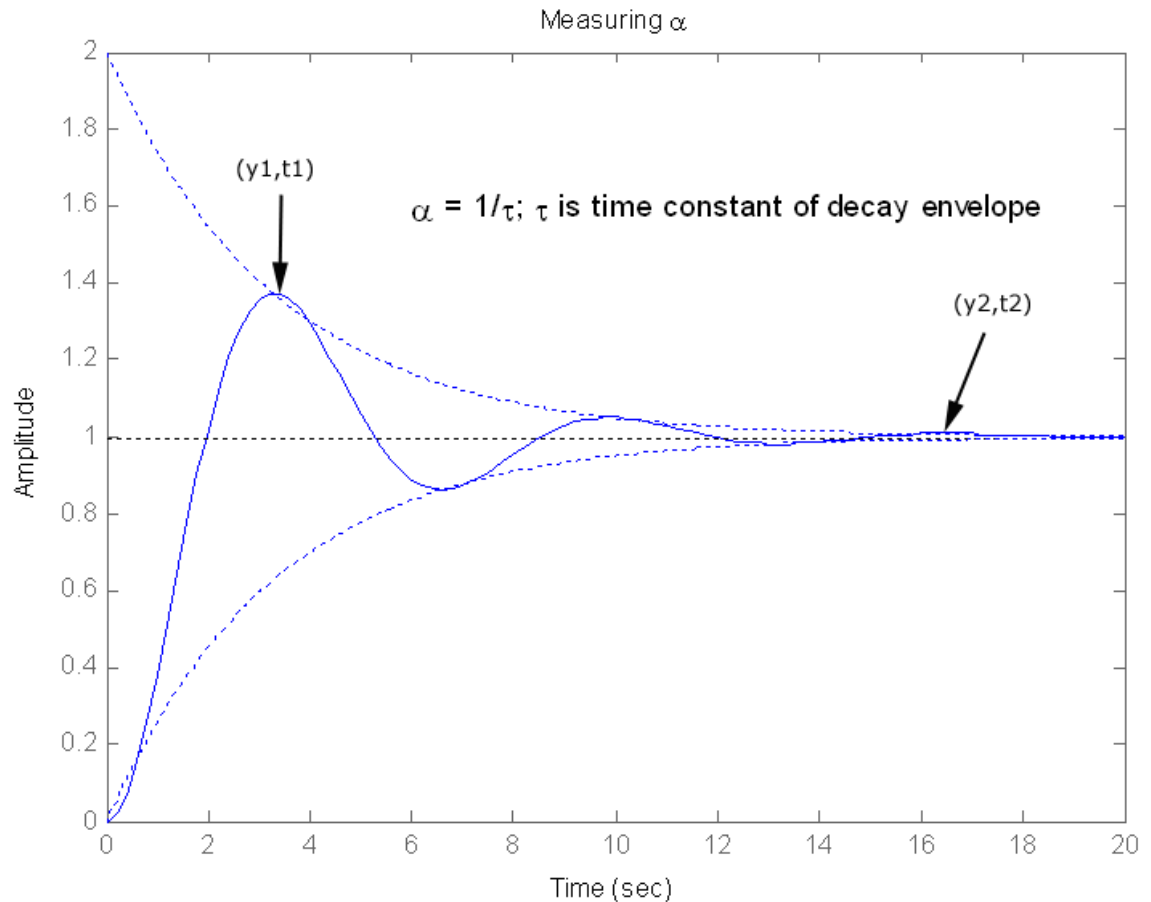
$$\alpha = \frac{\log\left(\frac{y_1 - a}{y_2 - a}\right)}{t_2 - t_1}$$



Note: we could also do a curve fit for more accuracy (and use all the data).

Switching parameters

(underdamped case only)

$$\alpha = \zeta \omega_0$$

$$\omega_d = \omega_0 \sqrt{1 - \zeta^2}$$

$$\alpha^2 = \zeta^2 \omega_0^2$$


$$\omega_d^2 = \omega_0^2 (1 - \zeta^2)$$

$$\begin{aligned} \omega_d^2 &= \omega_0^2 - \zeta^2 \omega_0^2 \\ &= \omega_0^2 - \alpha^2 \end{aligned}$$

$$\omega_0 = \sqrt{\omega_d^2 + \alpha^2}$$


$$\zeta = \frac{\alpha}{\omega_0}$$

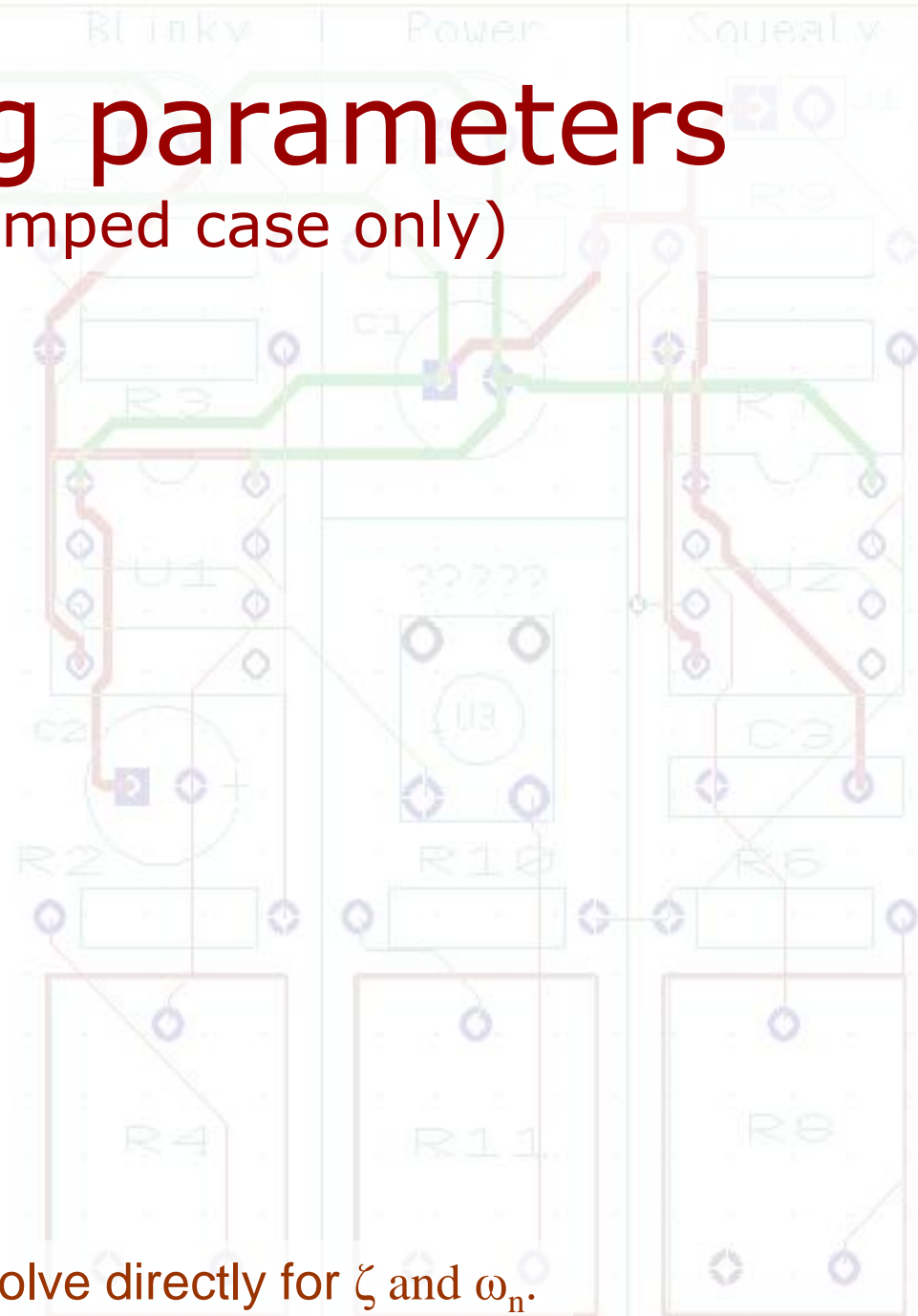If you do a curve fit, you can solve directly for ζ and ω_n .



The Overdamped Case

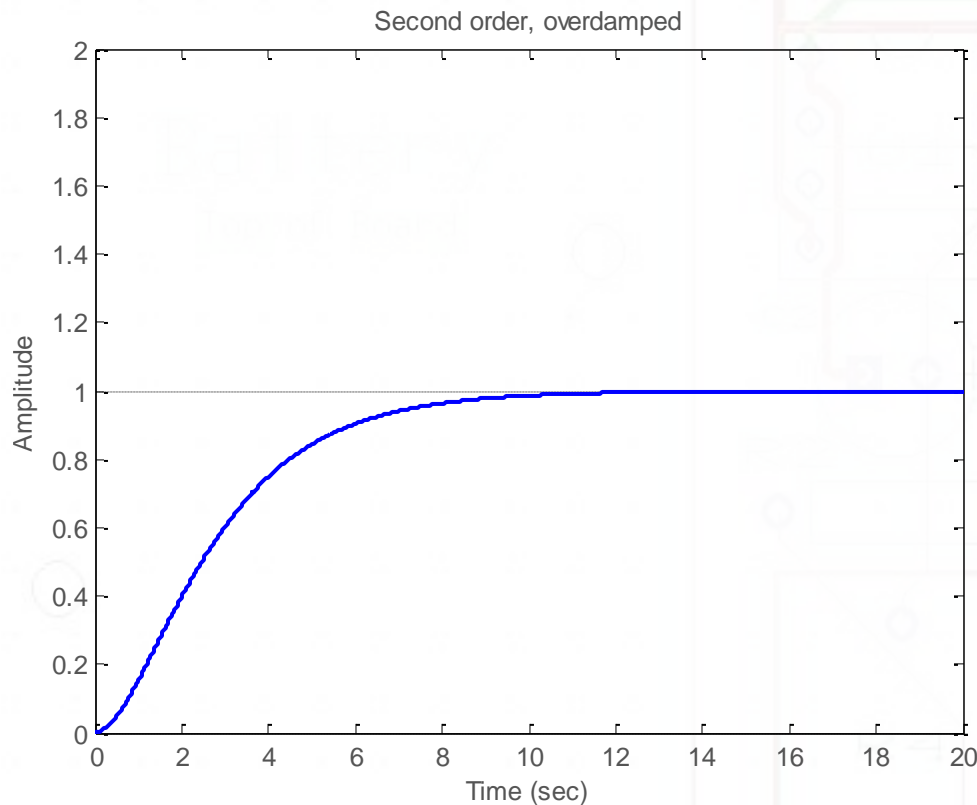For overdamped (and critically damped) case, there is no easy way to find the two time constants from the experimental data unless you do a curve fit.



$$y(t) = A_1 e^{-t/\tau_1} + A_2 e^{-t/\tau_2} + 1$$

A curve fit is made difficult because the unknown coefficients (A_1 , A_2 , τ_1 , τ_2) are hard to make initial guesses for by looking at the graph – but you can use theoretical values as your initial guesses.

If you do a curve fit, you can solve directly for ζ and ω_n .