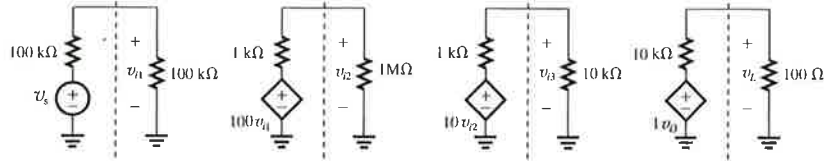


# WEEK 1

Chapter 1-14

ALSO - SOME  
EXTRA SOLUTIONS  
FOR REVIEW


This figure belongs to 1.47



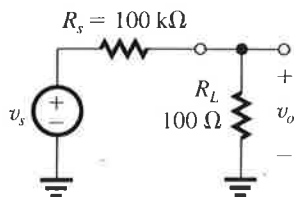1.45 continued here


The signal loses about 90% of its strength when connected to the amplifier input (because  $R_i = R_s/10$ ). Also, the output signal of the amplifier loses approximately 90% of its strength when the load is connected (because  $R_L = R_o/10$ ). Not a good design! Nevertheless, if the source were connected directly to the load,

$$\begin{aligned} \frac{v_o}{v_s} &= \frac{R_L}{R_L + R_s} \\ &= \frac{100 \Omega}{100 \Omega + 100 \text{ k}\Omega} \\ &\approx 0.001 \text{ V/V} \\ R_s &= 100 \text{ k}\Omega \end{aligned}$$



which is clearly a much worse situation. Indeed inserting the amplifier increases the gain by a factor  $8.3/0.001 = 8300$ .

1.46

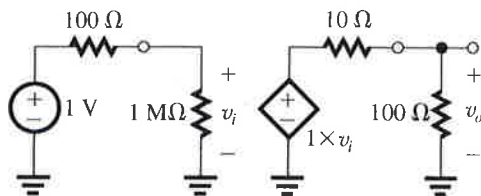


$$\begin{aligned} v_o &= 1 \text{ V} \times \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 100 \text{ k}\Omega} \times 1 \times \frac{100 \Omega}{100 \Omega + 10 \Omega} \\ &= \frac{1}{1.1} \times \frac{100}{110} = 0.83 \text{ V} \end{aligned}$$

$$\text{Voltage gain} = \frac{v_o}{v_s} = 0.83 \text{ V/V or } -1.6 \text{ dB}$$

Current gain =

$$\begin{aligned} \frac{v_o / 100 \Omega}{v_s / 1.1 \text{ M}\Omega} &= 0.83 \times 1.1 \times 10^4 \\ &= 9091 \text{ A/A or } 79.2 \text{ dB} \end{aligned}$$

This figure belongs to 1.48a

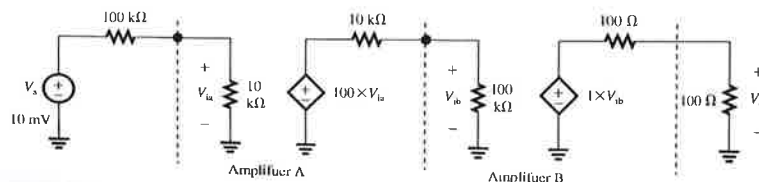

$$\text{Power gain} = \frac{v_o^2 / 100 \Omega}{v_s^2 / 1.1 \text{ M}\Omega} = 7578 \text{ W/W}$$

$$\text{or } 10 \log 7578 = 38.8 \text{ dB}$$

(This takes into acct. the power dissipated in the internal resistance of the source.)

1.47 In example 1.3 when the first and the second stages are interchanged, the circuit looks like the figure above

$$\frac{v_{i1}}{v_s} = \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega + 100 \text{ k}\Omega} = 0.5 \text{ V/V}$$

$$A_{v1} = \frac{v_{i2}}{v_{i1}} = 100 \times \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 1 \text{ k}\Omega}$$

$$= 99.9 \text{ V/V}$$

$$A_{v2} = \frac{v_{i3}}{v_{i2}} = 10 \times \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 1 \text{ k}\Omega}$$

$$= 9.09 \text{ V/V}$$

$$A_{v3} = \frac{v_L}{v_{i3}} = 1 \times \frac{100 \Omega}{100 \Omega + 10 \Omega} = 0.909 \text{ V/V}$$

$$\text{Total gain} = A_v = \frac{v_L}{v_{i1}} = A_{v1} \times A_{v2} \times A_{v3}$$

$$= 99.9 \times 9.09 \times 0.909 = 825.5 \text{ V/V}$$

The voltage gain from source to load is

$$\frac{v_L}{v_s} = \frac{v_L}{v_{i1}} \times \frac{v_{i1}}{v_s} = A_v \cdot \frac{v_{i1}}{v_s}$$

$$= 825.5 \times 0.5$$

$$= 412.7 \text{ V/V}$$

The overall voltage has reduced appreciably. It is due to the reason because the input impedance of the first stage,  $R_{in}$ , is comparable to the source resistance  $R_s$ . In example 1.3 the input impedance of the first stage is much larger than the source resistance

1.48 a. Case S-A-B-L


$$\frac{V_o}{V_s} = \frac{V_o}{V_{ib}} \times \frac{V_{ib}}{V_{ia}} \times \frac{V_{ia}}{V_s} =$$

$$\left(1 \times \frac{100}{100 + 100}\right) \times \left(100 \times \frac{100}{100 + 10}\right) \times \left(\frac{10}{100 + 10}\right)$$

$$\frac{V_o}{V_s} = 4.13 \text{ V/V and gain in dB } 20 \log 4.1 =$$

$$12.32 \text{ dB (See figure below)}$$

This figure belong to 1.48b

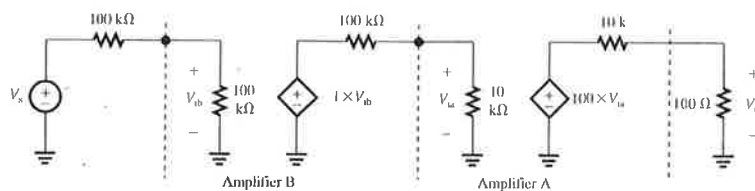

b. Case S-B-A-L

$$\frac{V_O}{V_S} = \frac{V_O}{V_{ia}} \cdot \frac{V_{ia}}{V_{ib}} \cdot \frac{V_{ib}}{V_S}$$

$$= \left(100 \times \frac{100}{100 + 10 \text{ K}}\right) \times \left(1 \times \frac{10 \text{ K}}{10 \text{ K} + 100}\right) \times \left(\frac{100 \text{ K}}{100 \text{ K} + 100}\right)$$

$$\frac{V_O}{V_S} = 0.49 \text{ V/V and gain in dB is } 20 \log 0.49 = -6.19 \text{ dB}$$

case a is preferred as it provides higher voltage gain.

1.49


Required overall voltage gain = 2 V/10 mV = 200 V/V. Each stage is capable of providing a *maximum* voltage gain of 10 (the open-circuit gain value). For *n* stages in cascade the maximum (unattainable) voltage gain in 10<sup>n</sup>. We thus see that we need at least 3 stages. For 3 stages, the overall voltage gain obtained is

$$\frac{v_O}{v_S} = \frac{10}{10 + 10} \times 10 \times \frac{10}{1 + 10} \times 10 \times \frac{10}{1 + 10}$$


$$\times 10 \times \frac{1}{1 + 1}$$

$$= 206.6 \text{ V/V}$$

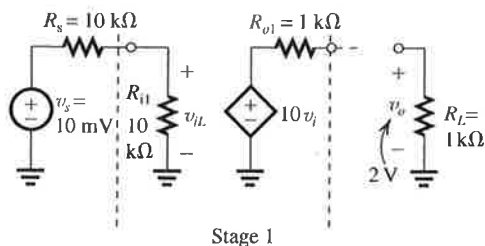
Thus, three stages suffice and provide a gain slightly larger than required. The output voltage actually obtained is 10 mV × 206.6 = 2.07 V.



This figure belongs to 1.50

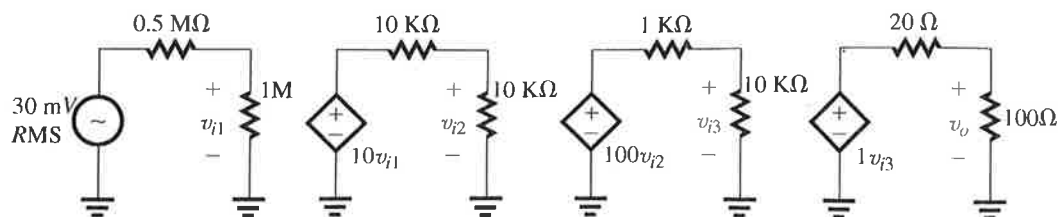

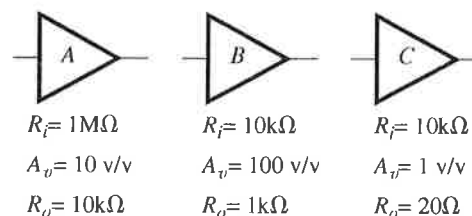1.50 Deliver 0.5W to a 100Ω load  
Source is 30mV RMS with 0.5MΩ source resistance. Choose from 3 amplifiers types



Choose order to eliminate loading on input and output

- A - 1st - to minimize loading on 0.5 MΩ source
  - B - 2nd - to boost gain
  - C - 3rd - to minimize loading at 100Ω output.
- (See figure below)

$$\frac{v_O}{v_S} = \frac{2 \text{ V}}{30 \text{ mV}} = 235.7 < \left(\frac{1 \mu}{0.5 \mu + 1 \mu}\right)(10)$$

$$\left(\frac{10}{10 + 10}\right)(100)\left(\frac{10}{10 + 1}\right)(1)\left(\frac{100}{20 + 100}\right)$$

$$235.7 < 253.6$$

$$v_O = (253.6)(30 \text{ mV}) = 7.61 \text{ v RMS}$$

$$P = \frac{v_O^2}{R_L} = \frac{(7.61)^2}{100} = 0.58 \text{ W}$$

1.51 (a) Required voltage gain =  $\frac{v_O}{v_S}$

$$= \frac{3 \text{ V}}{0.01 \text{ V}} = 300 \text{ V/V}$$

(b) The smallest *R<sub>i</sub>* allowed is obtained from


$$0.1 \mu\text{A} = \frac{10 \text{ mV}}{R_S + R_i} \Rightarrow R_S + R_i = 100 \text{ k}\Omega$$

Thus *R<sub>i</sub>* = 90 kΩ.


For *R<sub>i</sub>* = 90 kΩ, *i<sub>i</sub>* = 0.1 μA peak, and

$$\text{Overall current gain} = \frac{v_O / R_L}{i_i}$$

This figure belongs to 1.55b

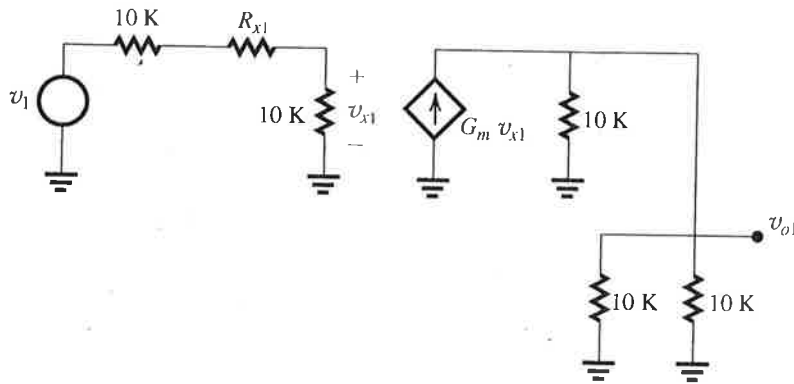

1.54

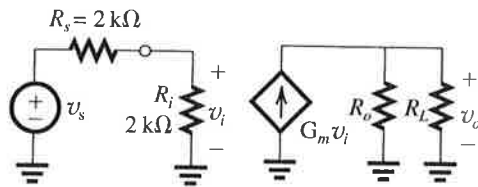

$G_m = 40 \text{ mA/V}$   
 $R_o = 20 \text{ k}\Omega$   
 $R_L = 1 \text{ k}\Omega$

$$v_i = v_s \frac{R_i}{R_s + R_i}$$

$$= v_s \frac{2}{2 + 2} = \frac{v_s}{2}$$

$$v_o = G_m v_i (R_L \parallel R_o)$$


$$= 40 \frac{20 \times 1}{20 + 1} v_i$$

$$= 40 \frac{20}{21} \frac{v_s}{2}$$

$$\text{Overall voltage gain} = \frac{v_o}{v_s} = 19.05 \text{ V/V}$$

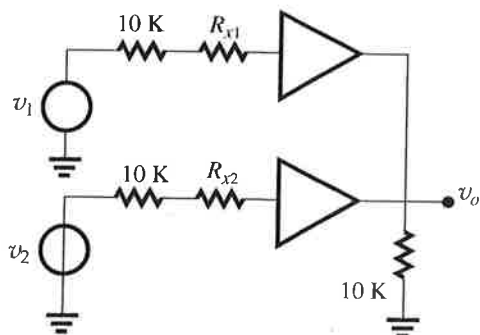1.55 Need  $V_0 = 10v_1 + 20v_2$

$R_{x1}$  and  $R_{xe}$  are used to get the appropriate gains on  $v_1$  and  $v_2$



Use superposition (See figure above)

$$v_{o1} = G_m v_{x1} \left( \frac{10 \text{ K}}{5 \text{ K} + 10 \text{ K}} \right) (5 \text{ K})$$

$$= G_m \left( \frac{10 \text{ K}}{5 \text{ K} + 10 \text{ K}} \right) (5 \text{ K}) \left( v_1 \left( \frac{10 \text{ K}}{10 \text{ K} + 10 \text{ K} + R_{x1}} \right) \right)$$

$$v = i \times R$$

$$\frac{v_{o1}}{v_1} = 10 = \left( \frac{20 \text{ mA}}{\text{V}} \right) \left( \frac{10 \text{ K}}{15 \text{ K}} \right) 5 \text{ K} \left( \frac{10 \text{ K}}{20 \text{ K} + R_{x1}} \right)$$

$$0.15 = \frac{10 \text{ K}}{20 \text{ K} + R_{x1}}$$

$$\therefore R_{x1} = 46.67 \text{ k}\Omega$$

Use same procedure for  $v_2$  but you will find 1

stage is not enough again, thus: (See figure below)


$$\frac{v_{o2}}{v_2} = 20 = \left( \frac{20 \text{ mA}}{\text{V}} \right) \left( \frac{10 \text{ K}}{5 \text{ K} + 10 \text{ K}} \right) (5 \text{ K}) \left( \frac{20 \text{ mA}}{\text{V}} \right)$$

$$\left( \frac{10 \text{ K}}{10 \text{ K} + 10 \text{ K}} \right) (10 \text{ K}) \left( \frac{10 \text{ K}}{10 \text{ K} + 10 \text{ K} + R_{x2}} \right)$$

$$20 = 6.67 \times 10^3 \left( \frac{10 \text{ K}}{20 \text{ K} + R_{x2}} \right)$$

$$\therefore R_{x2} = 3.3 \text{ M}\Omega \text{ series}$$


or can use of  $v_2$

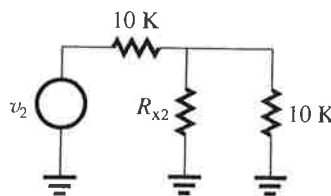


then

$$R_{x2} = 30 \Omega$$


This figure belongs to 1.55c

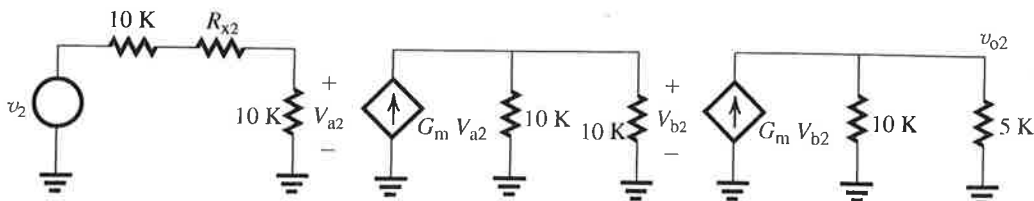


Finally,

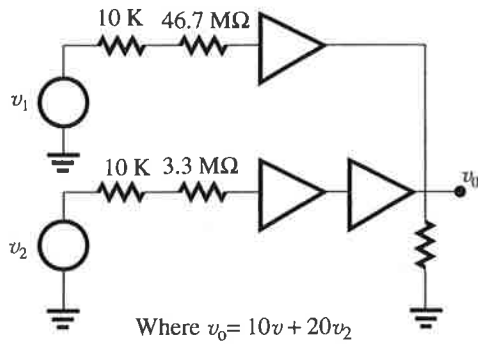


1.56

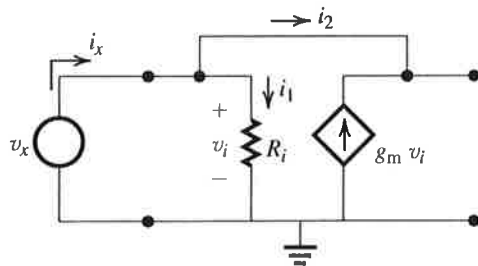
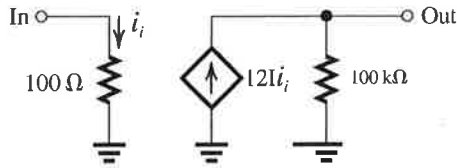
$$\begin{cases} i_x = i_1 + i_2 \\ i_1 = v_i / R_i \\ i_2 = g_m v_i \\ v_i = V_x \end{cases} \Rightarrow \begin{cases} i_x = v_x / R_i + g_m v_x \\ i_x = v_x + \left( \frac{1}{R_i} + g_m \right) v_x \\ \frac{v_x}{i_x} = \frac{1}{1/R_i + g_m} \\ = \frac{R_i}{1 + g_m R_i} = R_{in} \end{cases}$$



1.57 Transconductance amplifier.

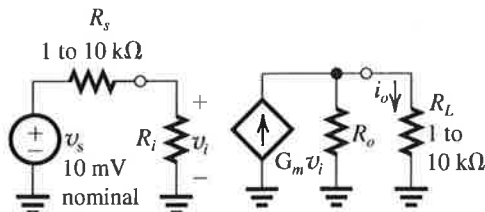

For  $R_s$  varying in the range 1 to 10 k $\Omega$ , and  $\Delta i_o$  limited to 10% we have to select  $R_i$  sufficiently large;

$$\begin{aligned} R_i &\geq 10R_{smax} \\ R_i &= 100 \text{ k}\Omega \end{aligned}$$

For  $R_L$  varying in the range 1 to 10 k $\Omega$ , the change in  $i_o$  can be kept to 10% if  $R_o$  is selected sufficiently large;


$$R_o \geq R_{Lmax}$$

$$\text{Thus } R_o = 100 \text{ k}\Omega$$

$$\text{For } v_s = 10 \text{ mV,}$$

$$\begin{aligned} i_{o \min} &= 10^{-2} \frac{R_i}{R_i + R_{smax}} G_m \frac{R_o}{R_o + R_{Lmax}} \\ 10^{-3} &= 10^{-2} \frac{100}{100 + 10} G_m \frac{100}{100 + 10} \end{aligned}$$
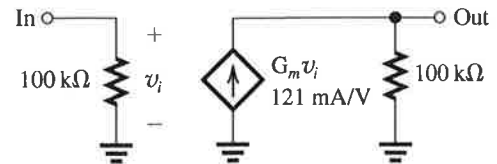
$$\begin{aligned} G_m &= 1.21 \times 10^{-1} \text{ A/V} \\ &= 121 \text{ mA/V} \end{aligned}$$



1.58 Transresistance amplifier

To limit  $\Delta v_o$  to 10% corresponding to  $R_s$  varying in the range 1 to 10 k $\Omega$ , we select  $R_i$  sufficiently low;

$$R_i \leq \frac{R_{smin}}{10}$$


$$\text{Thus, } R_i = 100 \Omega$$

To limit  $\Delta v_o$  to 10% while  $R_L$  varies over the range 1 to 10 k $\Omega$ , we select  $R_o$  sufficiently low;


$$R_o \leq \frac{R_{Lmin}}{10}$$

$$\text{Thus, } R_o = 100 \Omega$$
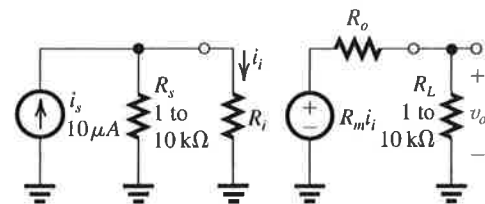
$$\text{Now, for } i_s = 10 \mu\text{A,}$$



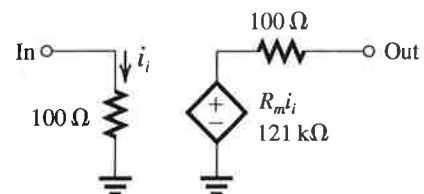
$$\begin{aligned} v_{o \min} &= 10^{-5} \frac{R_{smin}}{R_{smin} + R_i} R_m \frac{R_{Lmin}}{R_{Lmin} + R_o} \\ 1 &= 10^{-5} \frac{1000}{1000 + 100} R_m \frac{1000}{1000 + 100} \\ \Rightarrow R_m &= 1.21 \times 10^5 \\ &= 121 \text{ k}\Omega \end{aligned}$$



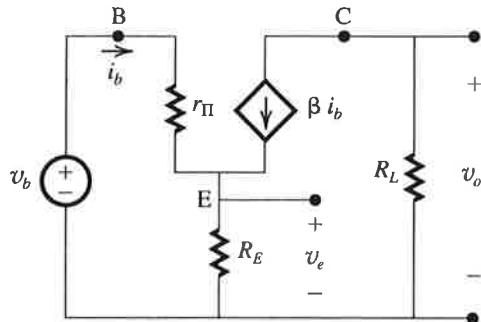1.61

Apply kirchhoff's current law in the mesh on the left



$$-\bar{V}_b + r_{\pi}i_b + R_E(\beta i_b + i_b) = 0$$

$$v_b = i_b[r_{\pi} + (\beta + 1)R_E]$$

Now  $v_c = -\beta \times i_b \times R_L$

$$\frac{v_c}{v_b} = -\frac{\beta R_L}{r_{\pi} + (\beta + 1)R_E}$$

$$v_c = (i_b + \beta i_b)R_E$$

$$= i_b(\beta + 1)R_E$$


$$\frac{v_c}{v_b} = \frac{(\beta + 1)R_E}{r_{\pi} + (\beta + 1)R_E}$$

$$= \frac{R_E}{\frac{r_{\pi}}{\beta + 1} + R_E}$$

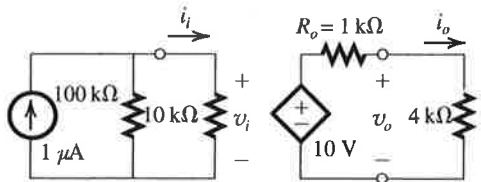1.62

$$R_o = \frac{\text{Open-circuit output voltage}}{\text{Short-circuit output current}} = \frac{10 \text{ V}}{10 \text{ mA}} = 1 \text{ k}\Omega$$

$$v_o = 10 \times \frac{4}{1 + 4} = 8 \text{ V}$$



$$A_v = \frac{v_o}{v_i} = \frac{8}{1 \times 10^{-3} \times (100 \parallel 10) \times 10^3} = 888 \text{ V/V or } 58.9 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o / R_L}{10^{-3} \times \frac{100}{100 + 10}} = \frac{8 / (4 \times 10^3)}{10^{-3} \times \frac{100}{110}} = 2200 \text{ A/A or } 66.8 \text{ dB}$$

$$A_i = \frac{v_o / R_L}{i_i^2 R_i} = \frac{8^2 / (4 \times 10^3)}{\left(10^{-3} \times \frac{100}{100 + 10}\right)^2 10 \times 10^3}$$


$$= 19.36 \times 10^5 \text{ W/W or } 62.9 \text{ dB}$$

Overall current gain  $\equiv \frac{i_o}{1 \mu\text{A}}$

$$= \frac{v_o / R_L}{1 \mu\text{A}} = \frac{8 / (4 \times 10^3)}{10^{-3}}$$

$$= 2000 \text{ A/A or } 66 \text{ dB}$$

1.63 Using the voltage divider rule

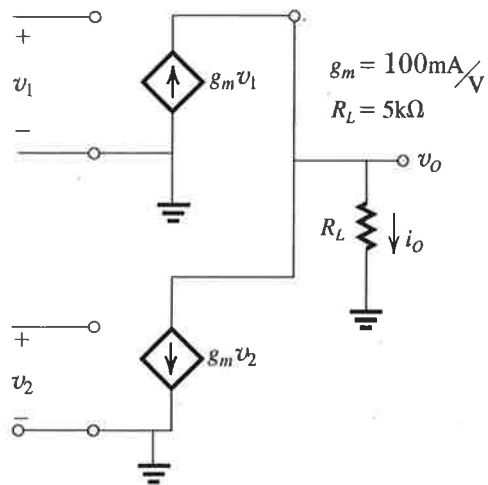

a.  $i_o = g_m v_1 - g_m v_2$

$$v_o = i_o R_L = g_m R_L (v_1 - v_2) = v_o$$

b.  $v_1 = v_2 \therefore v_o = 0 \text{ V}$

$$\left. \begin{matrix} v_1 = 1.01 \\ v_2 = 0.99 \end{matrix} \right\} \therefore v_o = 10 \text{ V}$$

1.64

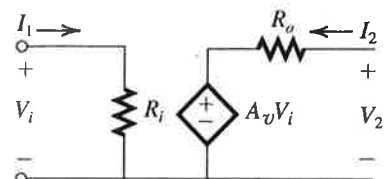
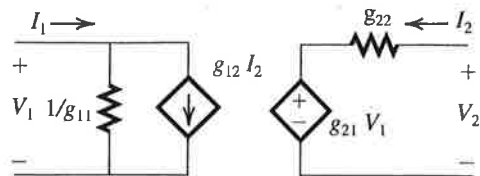


Figure 1.16a

$$I_1 = g_{11}V_1 + g_{12}I_a$$

$$V_2 = g_{21}V_1 + g_{22}I_a$$


thus

$$\left. \frac{V_2}{I_2} \right|_{v_1=0} = g_{22} = R_0 \quad \left. \frac{I_1}{V_1} \right|_{I_2=0} = g_{11} = \frac{1}{R_i}$$

$$\left. \frac{V_2}{I_2} \right|_{I_a=0} = g_{21} = Av \quad \left. \frac{I_2}{I_1} \right|_{v_1=0} = g_{12} = \infty$$

due to unilateral nature of Figure 1.16a

1.65

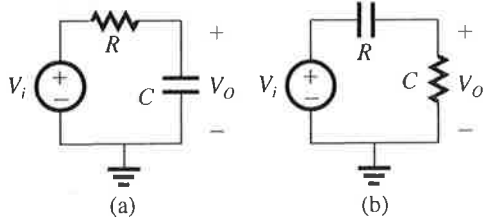

for (a)  $V_o = V_i \left( \frac{1/sC}{1/sC + R} \right)$

$$\frac{V_o}{V_i} = \frac{1}{1 + sCR}$$

where  $k=1$

$\omega_0 = \frac{1}{RC}$  from table 1.2 it is low pass.

for (b)  $V_o = V_i \left( \frac{R}{R + \frac{1}{sC}} \right)$


$$\frac{V_o}{V_i} = \frac{sRC}{1 + sCR}$$

$$\frac{V_o}{V_i} = \frac{s}{s + \frac{1}{RC}}$$

where  $k=1$

$\omega_0 = \frac{1}{RC}$  from table 1.2 it is high pass.

1.66

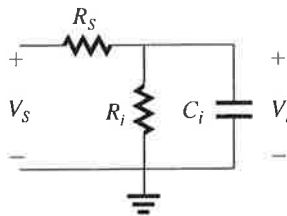

$$\frac{V_i}{V_s} = \frac{\frac{R_i \frac{1}{sC_i}}{R_i + \frac{1}{sC_i}}}{R_s + \left( \frac{R_i \frac{1}{sC_i}}{R_i + \frac{1}{sC_i}} \right)} = \frac{R_i}{1 + sC_i R_i} \cdot \frac{1}{R_s + \left( \frac{R_i}{1 + sC_i R_i} \right)}$$

$$= \frac{R_i}{R_s + sC_i R_i R_s + R_i}$$


$$\frac{V_i}{V_s} = \frac{R_i}{(R_s + R_i) + sC_i R_i R_s} = \frac{\frac{R_i}{(R_s + R_i)}}{1 + s \left( \frac{C_i R_i R_s}{R_s + R_i} \right)}$$

Where  $K = \frac{R_i}{(R_s + R_i)}$

$\omega = \frac{R_s + R_i}{C_i R_i R_s}$  from table 1.2 low pass for given

values  $\omega_0 = 12.5$  MHz

1.67 Using the voltage-divider rule.

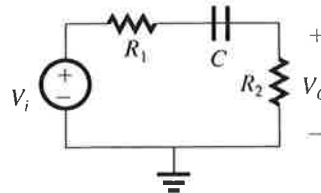

$$T(s) = \frac{V_o}{V_i} = \frac{R_2}{R_2 + R_1 + \frac{1}{sC}}$$

$$T(s) = \left( \frac{R_2}{R_1 + R_2} \right) \left( \frac{s}{s + \frac{1}{C(R_1 + R_2)}} \right)$$

which is from Table 1.2 is of the high-pass type with

$$K = \frac{R_2}{R_1 + R_2} \quad \omega_0 = \frac{1}{C(R_1 + R_2)}$$

As a further verification that this is a high-pass network and  $T(s)$  is a high-pass transfer function, we assume as  $s \Rightarrow 0$ ,  $T(s) \Rightarrow 0$ ; and as  $s \rightarrow \infty$ ,  $T(s) = R_2 / (R_1 + R_2)$ . Also, from the circuit

observe as  $s \rightarrow \infty$ ,  $(1/sC) \rightarrow 0$  and


$$V_o / V_i = R_2 / (R_1 + R_2)$$

$R_1 = 10$  k $\Omega$ ,  $R_2 = 40$  k $\Omega$ , and  $C = 0.1$   $\mu$ F.

$$f_o = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \times 0.1 \times 10^{-6} (10 + 40) \times 10^3} = 31.8$$
 Hz

$$|T(j\omega_0)| = \frac{K}{\sqrt{2}} = \frac{40}{10 + 40} \frac{1}{\sqrt{2}} = 0.57$$
 V/V

1.68 Using the voltage divider rule,

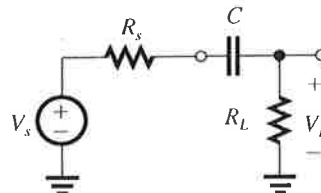

$$\text{CMRR} = 20 \log \left| \frac{A_d}{A_{CM}} \right| = 20 \log \frac{G_m}{\Delta G_m}$$

$$20 \log_{10} A_d = 80 \text{ dB} \Rightarrow A_d = 10^4$$

$$\frac{A_{CM}}{A_d} = \frac{\Delta G_m}{G_m} \Rightarrow A_{cm} = 10^4 \times \frac{0.1}{100} = 10$$


$$\text{CMRR} = 20 \log \frac{G_m}{\Delta G_m} = 20 \log \frac{1}{0.1/100} = 60$$

2.8

Circuit	$v_o/v_i$ (V/V)	$R_{in}$ (k $\Omega$ )
a	$\frac{-100}{10} = -10$	10
b	-10	10
c	-10	10
d	-10	10

virtual ground no current in 10 k $\Omega$

2.9

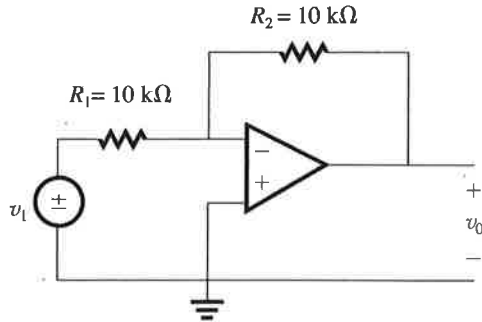

Closed loop gain is  $\frac{v_o}{v_i} = A$

$$A = \frac{v_o}{v_i} = -\frac{R_2}{R_1} = -\frac{10 \text{ k}\Omega}{10 \text{ k}\Omega} = -1 \text{ V/V}$$

For  $v_i = +1.000 \text{ V}$

$$v_o = A v_i = +1 \times 1.000 = -1.000 \text{ V}$$

The two resistors are 1% resistors


$$\left( \frac{v_o}{v_i} \right)_{\min} = -\frac{10(1-0.01)}{10(1+0.01)} = -0.98 \text{ V/V}$$

$$\left( \frac{v_o}{v_i} \right)_{\max} = -\frac{10(1+0.01)}{10(1-0.01)} = -1.02 \text{ V/V}$$


Range is -0.98 to -1.02 V/V

2.10


There are four possibilities:

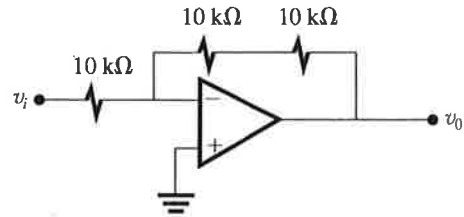

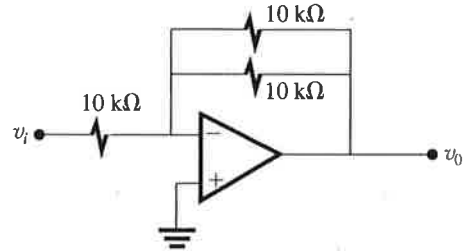
$$\frac{v_o}{v_i} = -2 \text{ V/V} \quad R_{in} = 10 \text{ k}\Omega$$


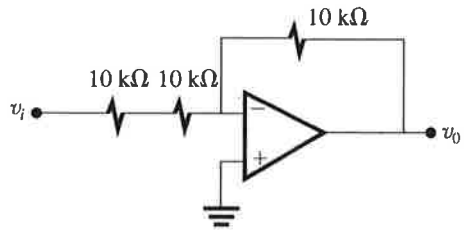
$$\frac{v_o}{v_i} = -0.5 \text{ V/V} \quad R_{in} = 10 \text{ k}\Omega$$


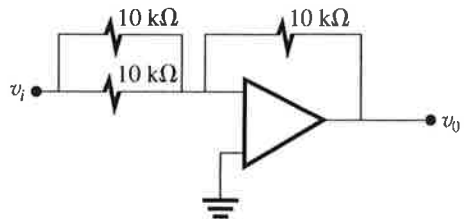
$$\frac{v_o}{v_i} = -0.5 \text{ V/V} \quad R_{in} = 20 \text{ k}\Omega$$



$$\frac{v_o}{v_i} = -2 \text{ V/V} \quad R_{in} = 5 \text{ k}\Omega$$

2.11

- a.  $G = -1 \text{ V/V}$
- b.  $G = -10 \text{ V/V}$
- c.  $G = -0.1 \text{ V/V}$
- d.  $G = -100 \text{ V/V}$
- e.  $G = -10 \text{ V/V}$

2.12


a.  $G = -1 \text{ V/V} = \frac{-R_2}{R_1} \Rightarrow R_1 = R_2 = 10 \text{ k}\Omega$

b.  $G = -2 \text{ V/V}$   
 $= \frac{-R_2}{R_1} \Rightarrow R_1 = 10 \text{ k}\Omega, R_2 = 20 \text{ k}\Omega$

c.  $G = -0.5 \text{ V/V}$   
 $= \frac{-R_2}{R_1} \Rightarrow R_1 = 20 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega$

d.  $G = -100 \text{ V/V}$   
 $= \frac{-R_2}{R_1} \Rightarrow R_1 = 10 \text{ k}\Omega, R_2 = 1 \text{ M}\Omega$

2.13

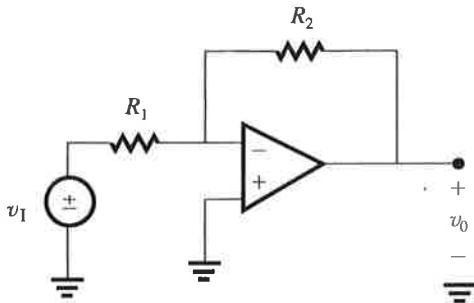

$$\frac{v_o}{v_i} = -4 \text{ V/V} = -\frac{R_2}{R_1}$$

$$\Rightarrow R_2 = 4 R_1$$

Total resistance used is  $100 \text{ k}\Omega$

$$\therefore R_1 + R_2 = 100 \text{ k}\Omega$$


$$R_1 + 4R_1 = 100 \text{ k}\Omega$$

$$R_1 = 20 \text{ k}\Omega$$

$$\text{and } R_2 = 4R_1 = 80 \text{ k}\Omega$$

2.14

Gain is 26 dB

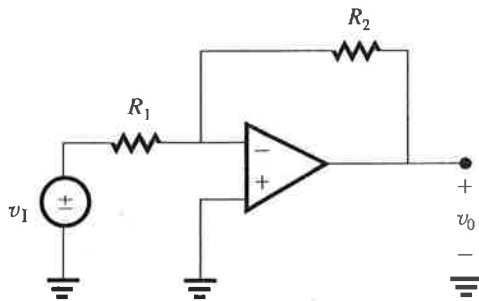

$$26 \text{ dB} = 20 \log |G|$$

$$G = 10^{26/20} = 19.95$$

$$\therefore \frac{v_o}{v_i} = -19.95 \text{ V/V} = -\frac{R_2}{R_1}$$


$$\Rightarrow R_2 = 19.95 R_1 \leq 1 \text{ M}\Omega$$

For largest possible input resistance choose  $R_2 = 1 \text{ M}\Omega$

$$R_1 = \frac{1 \text{ M}\Omega}{19.95} \approx 50.1 \text{ k}\Omega$$

$$R_{in} = R_1 = 50.1 \text{ k}\Omega$$

2.15

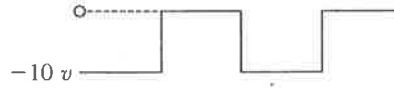

$$G = \frac{v_o}{v_i} = \frac{-R_2}{R_1} = \frac{-100}{10} = -10$$

$$v_{low} = 10 \text{ V}, v_{high} = 0, v_{avg} = -5 \text{ V}$$

2.16

$$\frac{v_o}{v_i} = \frac{10 \text{ k}}{1 \text{ k}} = -10 \text{ V/V}$$


$$v_o = -10 v_i$$

$$= -10 \times (0.5)$$

$$= -5 \text{ V/V}$$

In the figure
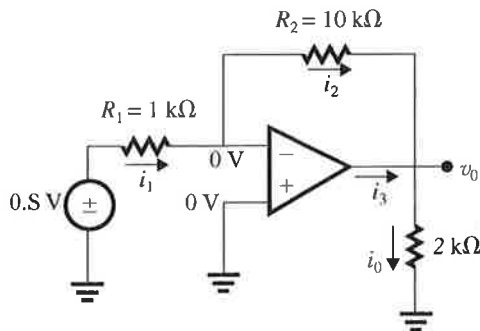
$$i_o = \frac{v_o}{2 \text{ k}\Omega} = \frac{-5}{2 \text{ k}\Omega} = -2.5 \text{ mA}$$



$$i_1 = i_2 = \frac{0 - (v_o)}{10 \text{ k}\Omega} = \frac{0 - (-5)}{10 \text{ k}\Omega}$$

$$= +0.5 \text{ mA}$$

$$i_3 = i_o - i_2 = -2.5 - 0.5$$

$$= -3 \text{ mA}$$

This additional current is supplied by the op amp.

2.17

$$|\text{Gain}| = \frac{R_2}{R_1} = \frac{R_2 \left(1 + \frac{X}{100}\right)}{R_1 \left(1 + \frac{X}{100}\right)} \approx \frac{R_2}{R_1} \left(1 \pm \frac{2X}{100}\right)$$

So  $2X$  is the tolerance on the closed loop gain  $G$

$$G = -100 \frac{\text{V}}{\text{V}} \text{ and } X = 1$$

$$\text{Gain variation } -102 < G < -98$$