

```
1) >> [n,w0]=buttord(2*pi*3000, 2*pi*8000, 3, 50, 's')
```

n = 6 \leftarrow 6th order filter

w0 = 1.9258e+04

```
>> [b,a]=butter(6,1,'s')
```

b = 0 0 0 0 0 0 1.0000

a = 1.0000 3.8637 7.4641 9.1416 7.4641 3.8637 1.0000

```
>> [sos,g]=tf2sos(b,a)
```

sos =

Stage	0	0	1.0000	1.0000	1.9319	1.0000
	0	0	1.0000	1.0000	0.5176	1.0000
	0	0	1.0000	1.0000	1.4142	1.0000


g = 1.0000

```
>> q=1./sos(:,5)
```

q =
0.5176 = Q₁
1.9319 = Q₂
0.7071 = Q₃

$$H(s) = \underbrace{\frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q_1}s + \omega_0^2}}_{\text{STAGE 1}} \cdot \underbrace{\frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q_2}s + \omega_0^2}}_{\text{STAGE 2}} \cdot \underbrace{\frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q_3}s + \omega_0^2}}_{\text{STAGE 3}}$$

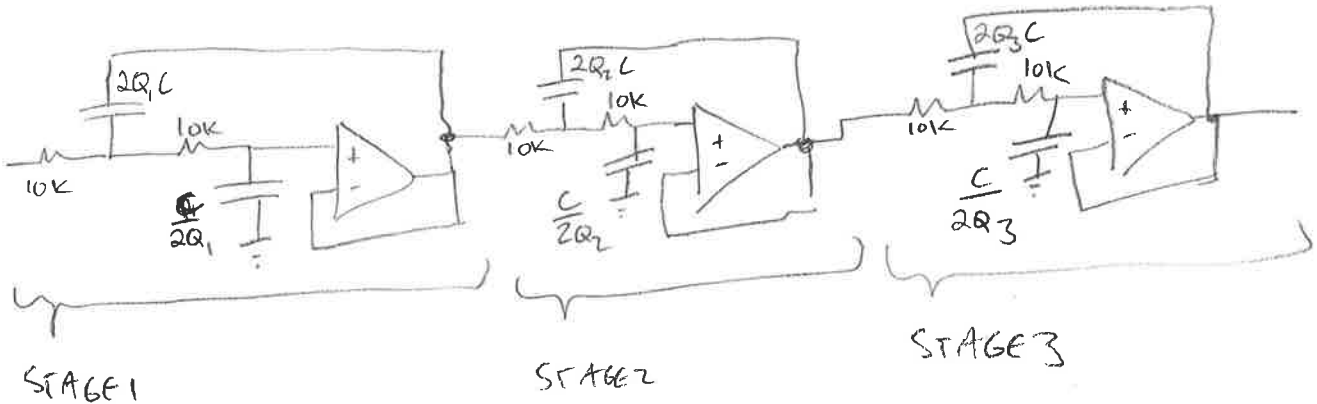2) $\omega_0 = \frac{1}{RC} = 2\pi \cdot 3000$ $R = 10k$ $C = 5.3nF = 5300pF$



3) $K=1$ Replace R_1 by $\frac{1}{sC_\alpha} = \frac{1}{sC}$ Replace R_2 by $\frac{1}{sC_\beta} = \frac{1}{sC}$ Replace $\frac{1}{sC_1}$ by R_α
 $R_\alpha = \frac{1}{sR_\alpha}$ $C_2 = \frac{1}{sR_\beta}$

$$H(s) = \frac{s^2 C^2 R_\alpha R_\beta}{s^2 + [sCR_\alpha + s^2 CR_\alpha]s + s^4 C^2 R_\alpha R_\beta} = \frac{s^2}{s^2 + [\frac{1}{CR_\beta} + \frac{1}{CR_\alpha}]s + \frac{1}{R_\alpha R_\beta C^2}}$$


$R_\alpha = \frac{R}{2Q}$
 $R_\beta = 2RQ$

$$H(s) = \frac{s^2}{s^2 + [\frac{\omega_0}{Q}]s + \omega_0^2}$$


$$R_1 = 680 \Omega \quad R_2 = 2k + 5k = 7k \quad C = 0.01 \mu F$$

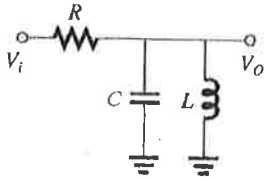4) $f = \frac{1.44}{(R_1 + 2R_2)C} = 9.81 kHz \rightarrow$ (very close to the 10kHz Band pass center frequency.)

$$D.C. = \frac{0.64(R_1 + R_2)k}{0.64(R_2 + 2R_2)k} = 0.52 \rightarrow \text{close to square wave.}$$



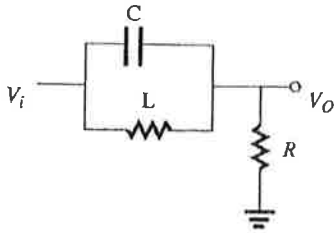\Rightarrow INTERCHANGE V_i & gnd to get:



5) 16.62
for fig 16.18(d)

$$T(S) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = R\sqrt{\frac{C}{L}}$$

For ω_0

$$\frac{\partial \omega_0}{\partial L} = \frac{\partial (LC)^{-1/2}}{\partial L} = -\frac{1}{2} L^{-3/2} C^{-1/2} = -\frac{\omega_0}{2L}$$

$$\frac{\partial \omega_0}{\partial C} = -\frac{\omega_0}{2C}$$

$$\frac{\partial \omega_0}{\partial R} = 0$$

$$\therefore S_L^{\omega_0} = \frac{\partial \omega_0}{\partial L} \frac{L}{\omega_0} = -1/2$$

$$S_C^{\omega_0} = \frac{\partial \omega_0}{\partial C} \times \frac{C}{\omega_0} = -1/2$$

$$S_R^{\omega_0} = \frac{\partial \omega_0}{\partial R} \frac{R}{\omega_0} = 0$$

For Q

$$\frac{\partial Q}{\partial L} = \frac{R\sqrt{C}}{L\sqrt{L}} \left(-\frac{1}{2}\right) = -\frac{Q}{2L}$$

$$\frac{\partial Q}{\partial C} = \frac{1}{2} \frac{R}{\sqrt{LC}} = \frac{1R\sqrt{C}}{2C\sqrt{L}} = \frac{Q}{2C}$$

$$\frac{\partial Q}{\partial R} = \sqrt{C/L} = \frac{R}{R} \sqrt{C/L} = Q/R$$

$$S_L^Q = -\frac{Q}{2C} \times \frac{L}{Q} = -\frac{1}{2}$$

$$S_C^Q = \frac{Q}{2C} \times \frac{C}{Q} = \frac{1}{2}$$

$$S_R^Q = -\frac{Q}{R} \cdot \frac{R}{Q} = -1$$

16.63

$$y = uv$$

$$\begin{aligned} S_x^y &= \frac{\partial(uv)}{\partial x} \frac{x}{uv} \\ &= v \frac{\partial u}{\partial x} \frac{x}{uv} + u \frac{\partial v}{\partial x} \frac{x}{uv} \\ &= \frac{\partial u}{\partial x} \frac{x}{u} + \frac{\partial v}{\partial x} \frac{x}{v} \\ &= S_x^u + S_x^v \end{aligned}$$

Part (b) $y = u/v$

$$\begin{aligned} S_x^y &= \frac{\partial y}{\partial x} \cdot \frac{x}{y} + \frac{\partial(u/v)}{\partial x} \frac{xv}{u} \\ &= \frac{1}{v} \frac{\partial u}{\partial x} \frac{xv}{u} + \frac{-u}{v^2} \frac{\partial v}{\partial x} \cdot \frac{xv}{u} \\ &= \frac{\partial u}{\partial x} \frac{x}{u} - \frac{\partial v}{\partial x} \frac{x}{v} \\ &= S_x^u - S_x^v \end{aligned}$$

Part (c) $y = ku$

$$\begin{aligned} S_x^y &= \frac{\partial u}{\partial x} \cdot \frac{x}{y} + \frac{\partial(ku)}{\partial x} \frac{x}{ku} \\ &= k \frac{\partial u}{\partial x} \frac{x}{ku} \\ &= \frac{\partial u}{\partial x} \frac{x}{u} \\ &= S_x^u \end{aligned}$$

Part (d) $y = u^n$

$$\begin{aligned} S_x^y &= \frac{\partial y}{\partial x} \cdot \frac{x}{y} + \frac{\partial(u^n)}{\partial x} \frac{x}{u^n} \\ &= nu^{n-1} \frac{\partial u}{\partial x} \cdot \frac{x}{u^n} \\ &= n \frac{\partial u}{\partial x} \cdot \frac{x}{u^n} = n S_x^u \end{aligned}$$


Part (e) $y = f_1(u) \quad u = f_2(x)$

$$\begin{aligned} S_x^y &= \frac{\partial y}{\partial x} \frac{x}{y} \times \frac{\partial f_1(u)}{\partial x} \frac{x}{f_1(u)} \\ &= \frac{\partial f_1(u)}{\partial x} \frac{\partial u}{\partial x} \frac{x}{f_1(u)} \\ &= \frac{\partial f_1}{\partial u} \cdot \frac{\partial f_2}{\partial x} \cdot \frac{x}{f_1} \cdot \frac{u}{u} \end{aligned}$$

But $u = f_2$

$$\begin{aligned} \therefore S_x^y &= \frac{\partial f_1}{\partial u} \cdot \frac{\partial f_2}{\partial x} \cdot \frac{x}{f_1} \cdot \frac{u}{f_2} \\ &= \frac{\partial f_1}{\partial u} \cdot \frac{u}{f_1} \cdot \frac{\partial f_2}{\partial x} \frac{x}{f_2} \\ &= S_u^{f_1} \cdot S_x^{f_2} \end{aligned}$$

17.18

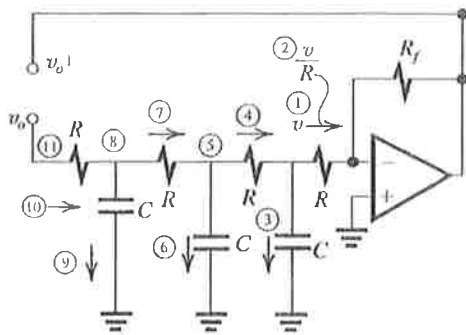

(3) $i = scv$
 (4) $scv = v/R$
 (5) $v + (SCv + \frac{v}{R})R = 2v + SCRv$
 (6) $2SCv + S^2C^2Rv$
 (7) $= (6) + (4) = 3SCv + S^2C^2Rv + \frac{v}{R}$
 (8) $2v + SCRv + v + 3SCRv + S^2C^2R^2v$
 $= 3v + 4SCRv + S^2C^2R^2v$
 (9) $3SCv + 4S^2C^2Rv + S^3C^3R^2v$
 (10) $= (7) + (9)$
 $= 6SCv + 5S^2C^2Rv + \frac{v}{R} + S^3C^3R^2v$
 (11) $= (8) + (10) \times R$
 $v_o = 4v + 10SCRv + 6S^2C^2R^2v + S^3C^3R^3v$
 $L(s) = \frac{v_o}{v} = \frac{vR_f/R}{v(S^3C^3R^3 + 6S^2C^2R^2 + 10SCR + 4)}$
 $= \frac{R_f/R}{S^3C^3R^3 + 6S^2C^2R^2 + 10SCR + 4}$
 $L(j\omega) = \frac{R_f/R}{(4 - 6\omega^2C^2R^2) + j(10\omega CR + \omega^3C^3R^3)}$

$L(j\omega)$ is purely real if

$10\omega_o CR = \omega_o^3 C^3 R^3$
 $\omega_o = \frac{1}{\sqrt{10}} \frac{1}{RC}$

Given $R = 10 \text{ k}\Omega$, $f_o = 10 \text{ kHz}$

$C = \frac{1}{\sqrt{10} \times 10^4 \times 2\pi 10^4}$
 $= 0.503 \text{ nF}$

Now,

$|L(j\omega_o)| = \frac{R_f/R}{4 - 6\omega_o^2 R^2 C^2}$ sub for ω_o

$= \frac{R_f/R}{4 - 6 \frac{1}{10R^2C^2} R^2 C^2}$


$= \frac{R_f/R}{4 - 6/10} \geq 1$

$\therefore R_f/R \geq 3.4$

$R_f \geq 34 \text{ k}\Omega$

17.19

for 2nd indicator

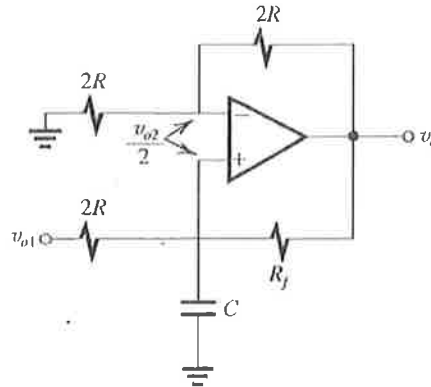

From the voltage divider around the upper branch:

$v_+ = v_- = \frac{1}{2} v_{o2}$

$\sum I = 0$ at the input

$\frac{1}{2} \frac{v_{o2} - v_{o1}}{2R} + SC \frac{v_{o2}}{2} + \frac{v_{o2} - v_{o2}}{R_f} = 0$

$\frac{v_{o2} - 2v_{o1}}{2R} + SCv_{o2} - \frac{v_{o2}}{R_f} = 0 \quad R_f = \frac{2R}{H\Delta}$

$v_{o2} \left(\frac{1}{2} + SC - \frac{H\Delta}{2R} \right) = \frac{v_{o1}}{R}$

$v_{o2} \left(SCR - \frac{\Delta}{2} \right) = v_{o1}$

$\therefore \frac{v_{o2}}{v_{o1}} = \frac{1}{SCR - \Delta/2}$

Now: $\frac{v_{o1}}{v_x} = \frac{-1}{SCR}$

$\therefore L(S) = \frac{-1/SCR}{SCR - \Delta/2}$

Characteristic equation $L(s) = 1$

$\therefore S^2 C^2 R^2 - \frac{SCR\Delta}{2} + 1 = 0$

\therefore Poles are

~~55 problem on last page~~

$$Q = \frac{1}{(2 - R_2/R_1)}$$

for $Q = \infty$ ~ poles on $j\omega$ axis

$$\sim R_2/R_1 = 2$$

for poles in R.H.P $R_2/R_1 > 2$

17.12

From Fig (17.5) assuming resistance of limiting network is very low

At positive peak

$$v_o = \left(\frac{1 + 20.3 \text{ K}}{10 \text{ K}}\right) v_o = 3.03 v_I \quad (1)$$

$$v_o - \left[\frac{R_5}{R_5 + R_6} \cdot (v_o - (-15))\right] - 0.7 = v_I \quad (2)$$

Now for $10V_{p-p}$ out

$$\hat{v}_o = 5 \text{ V}$$

$$\hat{v}_I = \frac{5}{3.03} = 1.65 \text{ V}$$

using (2) $R_5 = 1 \text{ k}\Omega$

$$5 - \left(\frac{1}{1 + R_6} \cdot (V_o + 15)\right) - 0.7 = 1.65$$

$$\frac{20}{1 + R_6} = 2.65$$

$$R_6 = \frac{20}{2.65} - 1$$

$$R_6 = 6.5 \text{ k}\Omega = R_3$$

If $R_3 = R_6 = \infty$ from (2)


$$v_o - \left(\frac{1}{1 + \infty} (V_o + 15)\right) - 0.7 = \frac{v_o}{3.03}$$

$$v_o - 0.7 = \frac{v_o}{3.3}$$

$$v_o = 1.04 \text{ V}$$

\therefore oppoutput is $2 v_o = 2.08 V_{p-p}$.

17.13

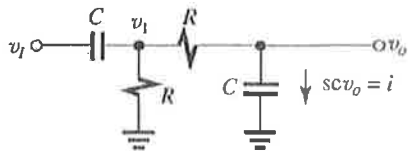

$$\frac{v_1 - v_o}{R} = SC v_o \Rightarrow v_1 - v_o(1 + SCR)$$

ΣI at v_1

$$\frac{v_1}{R} + SC(v_1 - v_o) + SC v_o = 0$$

$$v_o(1 + SCR) + SCR(v_o + v_o SCR) - SCR v_1 +$$

$$SCR v_o = 0$$

$$v_o(1 + SCR + SCR + S^2 C^2 R^2 + SCR) = SCR v_1$$

$$\beta(s) \triangleq \frac{v_o}{v_1} = \frac{SCR}{S^2 C^2 R^2 + 3SCR + 1}$$

$$= \frac{1}{3 + SCR + 1/(SCR)}$$

From Fig(17.3) $A = 1 + R_2/R_1$

$$\beta(j\omega) = \frac{1}{3 + j\left(\omega CR - \frac{1}{\omega CR}\right)}$$

Zero phase when $\omega CR = \frac{1}{\omega CR}$

$$\omega = \frac{1}{CR}$$


$$|\beta(W = 1/RC)| = \frac{1}{3}$$

for oscillations $1 + R_2/R_1 \geq 3 \Rightarrow \frac{R_2}{R_1} \geq 2$

$$L(s) = A\beta = \frac{1 + R_2/R_1}{3 + SCR + SCR}$$

$$L(jw) = \frac{1 + R_2/R_1}{3 + j\left(WCR - \frac{1}{WCR}\right)}$$

17.14

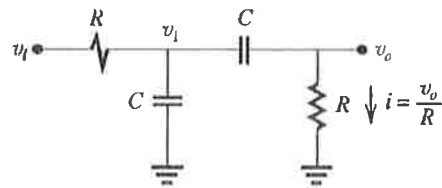

$$SC(v_1 - v_o) = \frac{v_o}{R}$$

$$v_1 = v_o \left(1 + \frac{1}{SRC}\right)$$

ΣI at v_1 :

$$\frac{-v_1 + v_1}{R} + SC v_1 + \frac{v_o}{R} = 0$$

\leftarrow SUB FOR v_1 and mult by $\frac{1}{SC}$

$$\frac{1}{SCR}[-v + v_o(1 + SCR)] + v_o \left(1 + \frac{1}{SCR}\right) +$$

$$\frac{v_o}{SCR} = 0$$

$$v_o \left[\frac{1}{SCR} + 1 + \frac{1}{SCR} + \frac{1}{S^2 C^2 R^2} + \frac{1}{SCR}\right]$$

$$= \frac{v_1}{SCR}$$

Problem F, Solution


a) The DC voltage across the inductor and resistor is 12 V, so the DC current = $12\text{V}/2\Omega = 6\text{A}$.



$I_{DC} = 6\text{A}$ (Assume this is constant over one period; this is equivalent to taking only the first term of the Taylor Series).

When $V_{\text{motor}} = 24\text{V}$: $V_{\text{inductor}} = 24 - V_{\text{resistor}} = 24 - 6\text{A} \cdot 2\Omega = 12\text{V}$ $L \frac{di}{dt} = V_{\text{inductor}} = 12$; $\frac{di}{dt} = \frac{V_{\text{inductor}}}{L} = 6000\text{A/s}$

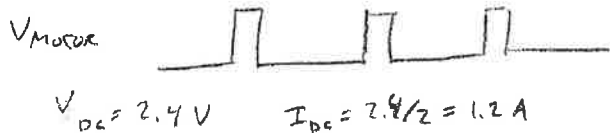One half period = $0.5/12800 = 39\mu\text{s} = 0.039\text{ms}$. ripple = $di = \frac{V_{\text{inductor}}}{L} dt = 6000\text{A/s} \cdot 0.039\text{ms} = 0.23\text{A}$



When $V_{\text{motor}} = 24\text{V}$ $V_{\text{inductor}} = 24 - V_{\text{resistor}} = 24 - 1.2\text{A} \cdot 2\Omega = 21.6\text{V}$ $L \frac{di}{dt} = V_{\text{inductor}} = 21.6$; $\frac{di}{dt} = \frac{V_{\text{inductor}}}{L} = 10800\text{A/s}$

Time high = $0.1/12800 = 7.8\mu\text{s}$ ripple = $di = \frac{V_{\text{inductor}}}{L} dt = 10800\text{A/s} \cdot 7.8\mu\text{s} = 0.084\text{A}$ (so... ripple is lower than with 50% duty cycle).

Check answer – ripple should be the same magnitude but opposite direction when $V_{\text{motor}} = 0$ (current is dropping).

When $V_{\text{motor}} = 0\text{V}$ $V_{\text{inductor}} = 0 - V_{\text{resistor}} = 0 - 1.2\text{A} \cdot 2\Omega = -2.4\text{V}$ $L \frac{di}{dt} = V_{\text{inductor}} = -2.4$; $\frac{di}{dt} = \frac{V_{\text{inductor}}}{L} = -1200\text{A/s}$

Time low = $0.1/12800 = 7.8\mu\text{s}$ ripple = $di = \frac{V_{\text{inductor}}}{L} dt = -1200\text{A/s} \cdot 7.8\mu\text{s} = -0.084\text{A}$ (This verifies original answer).

d) $I_{DC} = 1\text{A} = (V_{\text{batt}}/2 - E_b)/2\Omega = 1\text{A}$

$V_{\text{inductor}} = 24 - E_b - V_{\text{resistor}} = 24 - 10 - 1\text{A} \cdot 2\Omega = 12\text{V}$ $L \frac{di}{dt} = V_{\text{inductor}} = 12$; $\frac{di}{dt} = \frac{V_{\text{inductor}}}{L} = 6000\text{A/s}$

One half period = $0.5/12800 = 39\mu\text{s} = 0.039\text{ms}$. ripple = $di = \frac{V_{\text{inductor}}}{L} dt = 6000\text{A/s} \cdot 0.039\text{ms} = 0.23\text{A}$

So... the ripple is the same amount, but a much larger amount as a percent of the average current.

Problem G, Solution

- a)** Cutoff frequency: $\omega_0 = 1/(R \cdot C) = 4.17 \text{E}3 \text{ rad/sec}$, $f_0 = 660 \text{ Hz}$. Note: $660 \text{ Hz} \ll 12.8 \text{ kHz}$ (the pwm frequency)
- b)** Low pass filter, we only get DC component ($660 \text{ Hz} \ll 12.8 \text{ kHz}$). So $v_- = 0.5 \text{ volts}$.
- c)** By the same argument: $v_- = 0.1 \text{ volts}$.
- d)** $v_+ = 5.2 \cdot 240 / (20240) = 0.0617 \text{ V}$
- e)** $v_- =$ average of the voltage across J_1 . Therefore, $v_- = 0.0617 = 10 \text{ A} \cdot R_{J_1}$ $R_{J_1} = 0.00617 \Omega$
- f)** The voltage at v_+ is small, and therefore susceptible to noise. The capacitor forms a lowpass filter ($f_0 = 1/2 \cdot \pi \cdot C \cdot (10 \text{ k} \parallel (10 \text{ k} + 240)) \approx 300 \text{ Hz}$) that will attenuate noise on the supply (5.2V) from affecting the voltage on v_+ .