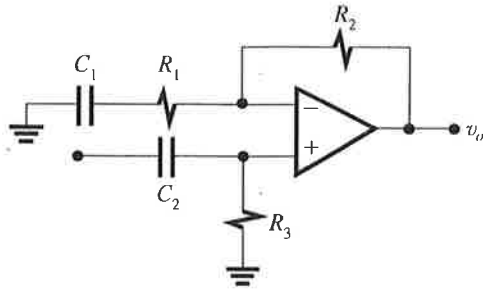


2.100



$$R_2 = R_3 = 100 \text{ k}\Omega$$

$$1 + \frac{R_2}{R_1} = 200$$

$$R_1 = \frac{100 \text{ k}}{199} = 502 \Omega$$

$$\frac{1}{R_1 C_1} = 2\pi \times 100 \Rightarrow C_1 = \frac{1}{500 \times 2\pi \times 100} = 3.18 \mu\text{F}$$

$$\frac{1}{R_3 C_2} = 2\pi \times 10 \Rightarrow C_2 = \frac{1}{100 \text{ K} \times 2\pi \times 10} = 0.16 \mu\text{F}$$

2.101


$$v_o = 4 \text{ mV}$$

The output component due to \$v_{os}\$ is

$$v_{o1} = v_{os} \left(1 + \frac{1 \text{ M}\Omega}{10 \text{ k}\Omega} \right) = 101 v_{os} = 101 \times 4 \text{ mV} = 404 \text{ mV}$$

The output component due to input bias current \$I_B\$ is:

$$I_{B1} = I_B + \frac{I_{OS}}{2}$$

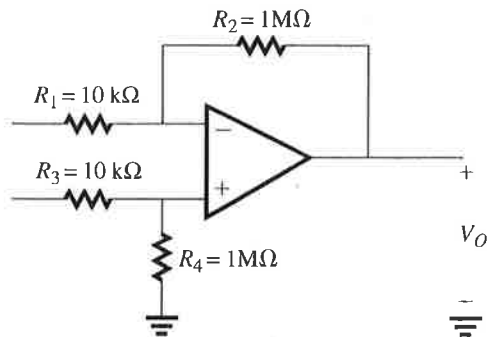

$$= \left(0.5 + \frac{0.1}{2} \right) \mu\text{A}$$

$$= 0.55 \mu\text{A}$$

$$I_{B2} = I_B - \frac{I_{OS}}{2}$$

$$= \left(0.5 - \frac{0.1}{2} \right)$$

$$= 0.45 \mu\text{A}$$

$$v_+ = -I_{B2} \times (10 \text{ k}\Omega \parallel 1 \text{ M}\Omega) = -0.45 \mu\text{A} \times 9.9 \text{ k}\Omega = -4.46 \text{ mV}$$

$$v_{o2} = v_+ + \left[1 \text{ M}\Omega \times \left(I_{B1} + \frac{v_+}{10 \text{ k}\Omega} \right) \right]$$


$$= -4.46 + 1 \text{ M}\Omega \times \left(0.55 \mu\text{A} + \frac{-4.46 \text{ mV}}{10 \text{ k}\Omega} \right)$$

$$= 99.5 \text{ mV}$$

The worst case dc offset Voltage at the output is

$$(99.5 + 404) \text{ mV} = 503.5 \text{ mV}$$

2.102

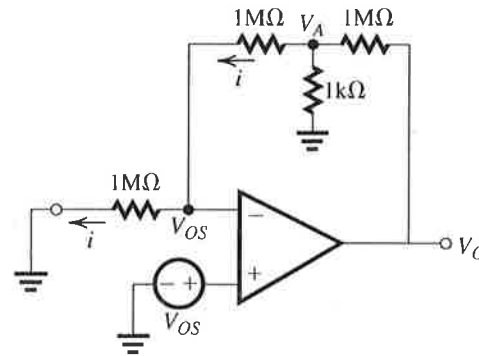

$$v_- = v_+ = v_{os}$$

$$V_A = 2v_{os} = 8 \text{ mV}$$

$$i = \frac{V_{OS}}{1 \text{ M}\Omega} = V_{OS} (\text{in } \mu\text{A})$$

$$V_o = V_A + 1 \text{ M}\Omega \times \left(i + \frac{V_A}{1 \text{ k}} \right)$$


$$= 2V_{os} + 1 \text{ M}\Omega \times \left(\frac{V_{OS}}{1 \text{ M}} + \frac{2V_{OS}}{1 \text{ k}} \right)$$

$$= 2003 V_{os}$$

$$= 2003 \times 4 \text{ mV}$$

$$\cong 8 \text{ V}$$

For capacitively coupled input

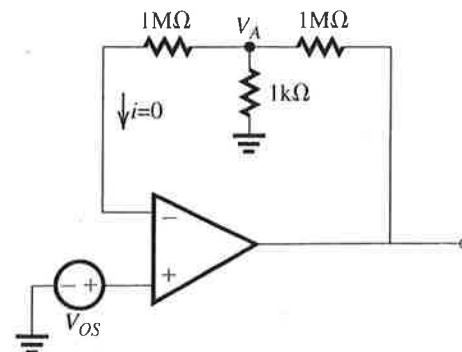

$$V_+ = V_- = V_{OS}$$


$$V_A = V_{OS} \therefore i = 0$$

$$V_O = V_A + 1 \text{ M}\Omega \times \frac{V_{OS}}{1 \text{ k}\Omega} = V_{OS} + 1000 V_{OS}$$

$$= 1001 V_{OS}$$

$$= 1001 \times 4 \text{ mV} = 4.004 \text{ V}$$

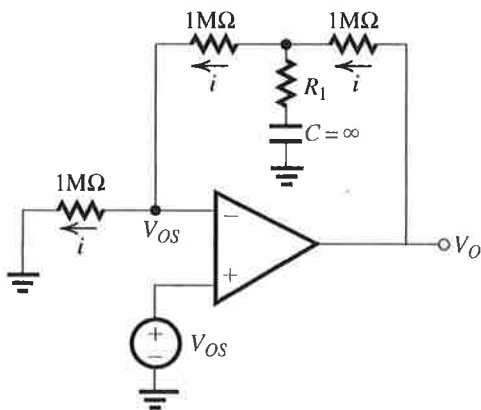A large capacitor placed in series with 1 kΩ resistor



$$V_+ = V_- = V_{OS}$$

No dc current flows through R_1 , C branch

$$\therefore V_O = V_A + V_{OS}$$

$$= 2V_{OS} + V_{OS}$$

$$= 3V_{OS}$$


$$= 3 \times 4 \text{ mV}$$

$$= 12 \text{ mV}$$

2.103

At 0°C, we expect
 $\pm 10 \times 25 \times 1000 \mu = \pm 250 \text{ mV}$
 At 75°C, we expect
 $\pm 10 \times 50 \times 1000 \mu = \pm 500 \text{ mV}$
 We expect these quantities to have opposite polarities.

2.104

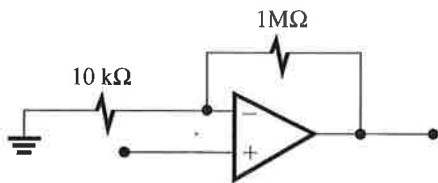

$$100 = 1 + \frac{R_2}{R_1} \Rightarrow R_1 = 10.1 \text{ k}\Omega$$

a) $V_O = 100 \times 10^{-9} \times 1 \times 10^6 = 0.1 \text{ V}$

b) Largest output offset is:
 $V_O = 1 \text{ mV} \times 100 + 0.1 \text{ V} = 200 \text{ mV} = 0.2 \text{ V}$
 c) For bias current compensation we connect a resistor R_3 in series with the positive input terminal of the op-amp, with: $R_3 = R_1 \parallel R_2$

$$I_{OS} = \frac{100}{10} = 10 \text{ nA}$$


$$R_3 = 10 \text{ k}\Omega \parallel 1 \text{ M}\Omega = 10 \text{ k}\Omega$$

The offset current alone result in an output offset voltage of


$$I_{OS} \times R_2 = 10 \times 10^{-9} \times 1 \times 10^6 = 10 \text{ mV}$$

d) $V_O = 100 \text{ mV} + 10 \text{ mV} = 110 \text{ mV}$

2.105

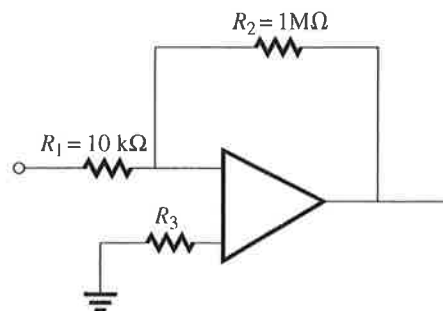

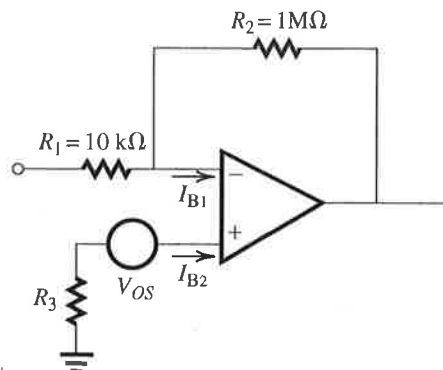See equation 2.39
 $R_3 = R_1 \parallel R_2 = 10 \text{ k}\Omega \parallel 1 \text{ M}\Omega = 9.9 \text{ k}\Omega$
 From equation 2.40
 $V_O = I_{OS} R_2$ and $V_O = 0.21 \text{ V}$



If $V_{OS} = 1 \text{ mV}$

$$V_+ = -I_{B2} R_3 \pm V_{OS}$$

$$I_{B1} = \frac{I_{B2} R_3 \pm V_{OS}}{R_1} + \frac{I_{B3} R_3 \pm V_{OS}}{R_2}$$

$$= I_{B2} R_3 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \pm V_{OS} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

But $\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_3}$


$$I_{B1} = I_{B2} \pm \frac{V_{OS}}{R_3}$$

$$(I_{B1} - I_{B2}) = \pm \frac{V_{OS}}{R_3} = \pm \frac{1 \text{ mV}}{9.9 \text{ k}\Omega} = \pm 0.1 \mu\text{A}$$

so the offset current is $\pm 0.1 \mu\text{A}$


2.106

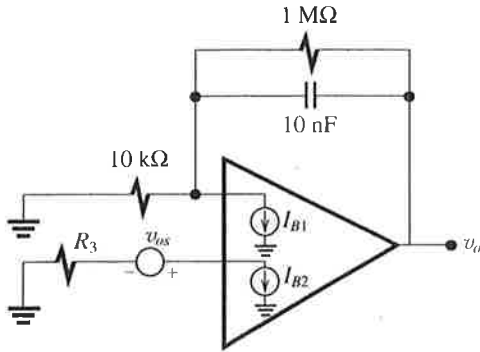a) To compensate for the effect of dc bias current I_B , we can consider the following model



Similar to the discussion leading to equation (2.46) we have:
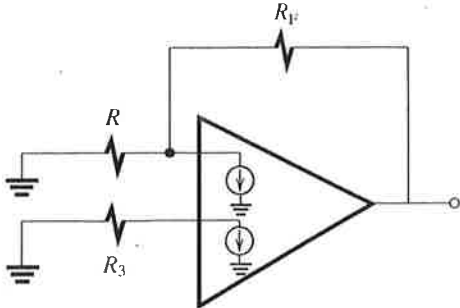
$$R_3 = R \parallel R_F = 10 \text{ k}\Omega \parallel 1 \text{ M}\Omega \Rightarrow R_3 = 9.9 \text{ k}\Omega$$



b) As discussed in Section 2.8.2 the dc output voltage of the integrator when the input is grounded is:

$$V_O = V_{OS} \left(1 + \frac{R_F}{R} \right) + I_{DS} R_F$$

$$V_O = 3 \text{ mV} \left(1 + \frac{1 \text{ M}\Omega}{10 \text{ k}\Omega} \right) + 10 \text{ nA} \times 1 \text{ M}\Omega$$

$$= 0.303 \text{ V} + 0.01 \text{ V}$$

$$V_O = 0.313 \text{ V}$$

2.107

eq.2.28:

$$w_t = A_O w_b$$

$$\Rightarrow f_t = A_O f_b$$

A_O	$f_b(\text{Hz})$	$f_t(\text{Hz})$
10^5	10^2	10^7
10^6	1	10^6
10^5	10^3	10^8
10^7	10^{-1}	10^6
2×10^5	10	2×10^6

2.108

Eq. 2.25:

$$A = \frac{A_O}{1 + jw/w_b} \Rightarrow |A| = \frac{|A_O|}{\sqrt{1 + \left(\frac{f}{f_b}\right)^2}}$$

$$A_O = 80 \text{ dB}, A = 40 \text{ dB @ } f = 100 \text{ kHz}$$

$$20 \log \sqrt{1 + \left(\frac{f}{f_b}\right)^2} = 20 \log \frac{|A_O|}{|A|} = 20 \log A_O - 20 \log A$$

$$= 86 - 40 = 46 \text{ dB}$$


$$1 + \left(\frac{100 \text{ kHz}}{f_b}\right)^2 = (199.5)^2 \Rightarrow f_b = 0.501 \text{ kHz}$$

$$f_b = 501 \text{ Hz}$$

$$f_t = A_O f_b = 1.995 \times 10^4 \times 501$$

$$= \overbrace{9.998 \text{ MHz}}^{86 \text{ dB}} \approx 10 \text{ MHz}$$

2.109

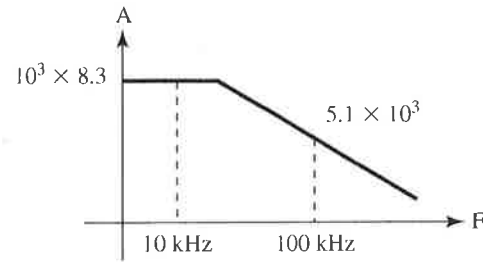

$$A_O = 8.3 \times 10^3 \text{ V/V}$$

$$\text{Eq. 2.25: } A = \frac{A_O}{1 + j\frac{f}{f_b}}$$

$$f_t = A_O f_b$$

$$c) 1 + \frac{R_2}{R_1} = 2 \text{ V/V}, f_{3\text{db}} = 10 \text{ kHz}$$

$$f_i = 10 \text{ MHz} \times 2 = 20 \text{ MHz}$$

$$d) -\frac{R_2}{R_1} = -2 \text{ V/V}, f_{3\text{db}} = 10 \text{ kHz}$$

$$f_i = 10 \text{ MHz}(1 + 2) = 30 \text{ MHz}$$

$$e) -\frac{R_2}{R_1} = -1000 \text{ V/V}, f_{3\text{db}} = 20 \text{ kHz}$$

$$f_i = 20 \text{ kHz}(1 + 100) = 20.02 \text{ MHz}$$

$$f) 1 + \frac{R_2}{R_1} = 1 \text{ V/V}, f_{3\text{db}} = 1 \text{ MHz}$$

$$f_i = 1 \text{ M} \times 1 = 1 \text{ MHz}$$

$$g) -\frac{R_2}{R_1} = -1, f_{3\text{db}} = 1 \text{ MHz}$$

$$f_i = 1 \text{ M}(1 + 1) = 2 \text{ MHz}$$

2.114

$$\text{Gain} = 1 + \frac{R_2}{R_1} = 96 \text{ V/V}$$

$$f_{3\text{db}} = 8 \text{ kHz}$$

$$f_i = 96 \times 8 = 768 \text{ kHz}$$

$$\text{for } f_{3\text{db}} = 24 \text{ kHz}$$

$$\text{Gain} = \frac{768}{24} = 32 \text{ V/V}$$

2.115

$$f_{3\text{db}} = f_i = 1 \text{ MHz}$$

$$|G| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3\text{db}}}\right)^2}} = \frac{1}{\sqrt{1 + f^2}} f_{\text{in}} \text{ MHz}$$

$$|G| = 0.99 \Rightarrow f = 0.142 \text{ MHz}$$

The follower behaves like a low-pass STC circuit

$$\text{with a time constant } \tau = \frac{1}{2\pi \times 10^6} = \frac{1}{2\pi} \mu\text{s}$$

$$t_r = 2.20 = 0.35 \mu\text{s} \text{ (Refer to Appendix F)}$$

2.116

$$1 + \frac{R_2}{R_1} = 10 \text{ V/V}, R_1 = 1 \text{ k}\Omega, R_2 = 9 \text{ k}\Omega$$

If we consider 5τ the time that it takes for the output voltage to reach 99% of its final value, then: $5\tau = 100 \text{ ns} \Rightarrow \tau = 20 \text{ ns}$

$$\tau = \frac{1}{\omega_{3\text{db}}} \Rightarrow \omega_{3\text{db}} = 50 \times 10^6 \Rightarrow f_{3\text{db}} = 7.96 \text{ MHz}$$

$$f_i = \left(1 + \frac{R_2}{R_1}\right) f_{3\text{db}} = 10 \times 7.96 = 79.6 \text{ MHz}$$

2.117

a) Assume two identical stages, each with a gain

$$\text{function: } G = \frac{G_o}{1 + j\frac{\omega}{\omega_1}} = \frac{G_o}{1 + jf/f_1}$$

$$G = \frac{G_o}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$

$$\text{overall gain of the cascade is } \frac{G_o^2}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$

The gain will drop by 3db when:

$$1 + \left(\frac{f_{3\text{db}}}{f_1}\right)^2 = \sqrt{2}, \text{ Note } 3\text{db} = 20\log\sqrt{2}$$

$$f_{3\text{db}} = f_1 \sqrt{\sqrt{2} - 1}$$

$$b) 40 \text{ db} = 20 \log G_o \Rightarrow G_o = 100 = 1 + \frac{R_2}{R_1}$$

$$f_{3\text{db}} = \frac{f_i}{1 + \frac{R_2}{R_1}} = \frac{1 \text{ MHz}}{100} = 10 \text{ kHz}$$

c) Each stage should have 20db gain or

$$1 + \frac{R_2}{R_1} = 10 \text{ and therefore a 3db frequency of:}$$

$$f_1 = \frac{10^6}{10} = 10^5 \text{ Hz.}$$

$$\text{The overall } f_{3\text{db}} = 10^5 \sqrt{\sqrt{2} - 1} = 64.35 \text{ kHz}$$

which is 6 time greater than the bandwidth achieved using single op amp.

(case b above)

2.118

$f_i = 100 \times 5 = 500 \text{ MHz}$ if single op-amp is used.

with op-amp that has only $f_i = 40 \text{ MHz}$, the possible closed 100 p gain at 5 MHz is:

$$|A| = \frac{40}{5} = 8 \text{ V/V}$$

To obtain an overall gain of 100, three such amplifier cascaded, would be required. Now, if each of the 3 stages, has a low-frequency (d) closed loop gain K, then its 3-db frequency will $\frac{40}{k} \text{ MHz}$.

$$v_p = \frac{2}{100} = 0.02 \text{ V} = 20 \text{ mV}$$

$$c) R_L = ?, i_{\text{umax}} = 20 \text{ mA} = \frac{10 \text{ V}}{R_{L\text{min}}} + \frac{10 \text{ V}}{100 \text{ K}}$$

$$20 - 0.1 = \frac{10}{R_{L\text{min}}} \Rightarrow R_{L\text{min}} = 502 \Omega$$

2.123




Op Amp slew rate = $10 \text{ V}/\mu\text{s}$

For the input pulse to rise 5 V , it will take

$$\frac{5}{10} = 0.5 \mu\text{s}$$

\therefore The minimum pulse width = $W = 0.5 \mu\text{s}$

The output will be a triangular with $10 \text{ V}/\mu\text{s}$ slew rate

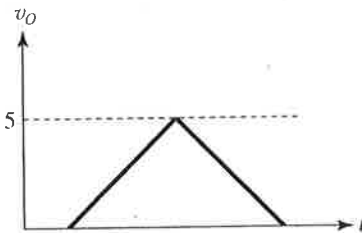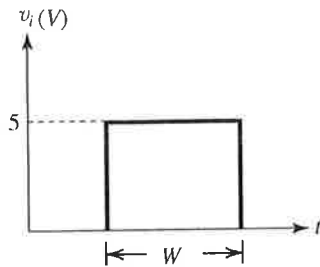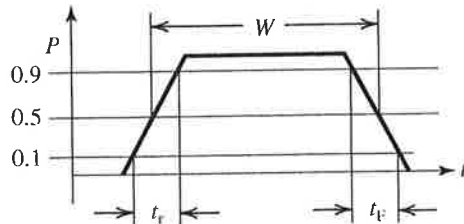**2.124**

$$W = 2 \mu\text{s}$$

$$t_r + t_f = 0.2 W = 0.4 \mu\text{s}$$

$$t_r = t_f = 0.2 \mu\text{s}$$

$$\text{SR} = \frac{(0.9 - 0.1)V}{t_r} = \frac{0.8 \times 10}{0.2} = 40 \text{ V}/\mu\text{s}$$

2.125

$$\text{Slope of the triangle wave} = \frac{20 \text{ V}}{T/2} = \text{SR}$$

$$\text{Thus } \frac{20}{T} \times 2 = 10 \text{ V}/\mu\text{s}$$

$$\Rightarrow T = 4 \mu\text{s} \text{ or } f = \frac{1}{T} = 250 \text{ kHz}$$

For a sine wave $v_o = v_o \sin(2\pi \times 250 \times 10^3 t)$

$$\left. \frac{dv_o}{dt} \right|_{\text{max}} = 2\pi \times 250 \times 10^3 \hat{v}_o = \text{SR}$$

$$\Rightarrow \hat{v}_o = \frac{10 \times 10^6}{2\pi \times 10^3 \times 250} = 6.37 \text{ V}$$

2.126

$$v_o = 10 \sin \omega t \Rightarrow \frac{dv_o}{dt} = 10\omega \cos \omega t \Rightarrow \left. \frac{dv_o}{dt} \right|_{\text{max}} = 10\omega$$

The highest frequency at which this output is possible is that for which:

$$\left. \frac{dv_o}{dt} \right|_{\text{max}} = \text{SR} \Rightarrow 10\omega_{\text{max}} = 60 \times 10^6 \Rightarrow \omega_{\text{max}} = 6 \times 10^5$$

$$\Rightarrow f_{\text{max}} = 45.5 \text{ kHz}$$

2.127

$$a) v_i = 0.5, v_o = 10 \times 0.5 = 5 \text{ V}$$

Output distortion will be due to slew-Rate limitation and will occur at the frequency for which

$$\left. \frac{dv_o}{dt} \right|_{\text{max}} = \text{SR}$$

$$\omega_{\text{max}} \times 5 = \frac{1}{10^{-6}} = 2 \times 10^5 \text{ rad/s} \Rightarrow f_{\text{max}} = 31.8 \text{ kHz}$$

b) The output will distort at the value of V_i that

$$\text{results in } \left. \frac{dv_o}{dt} \right|_{\text{max}} = \text{SR.}$$

$$v_o = 10 v_i \sin 2\pi \times 20 \times 10^3$$

$$\left. \frac{dv_o}{dt} \right|_{\text{max}} = 10 v_i \times 2\pi \times 20 \times 10^3$$

$$\text{Thus } v_i = \frac{1/10^{-6}}{10 \times 2\pi \times 20 \times 10^3} = 0.795 \text{ V}$$

$$c) v_i = 50 \text{ mV} \quad v_o = 500 \text{ mV} = 0.5 \text{ V}$$

Slew rate begins at the frequency for which $\omega \times 0.5 = \text{SR}$

which gives $\omega_i = \frac{1/10^{-6}}{0.5} = 2 \times 10^6$ rad/s or

$f = 318.3$ kHz. However the small signal 3 dB frequency is

$$f_{3dB} = \frac{f_i}{1 + \frac{R_2}{R_1}} = \frac{2 \times 10^6}{10} = 200 \text{ kHz}$$

Thus the useful frequency range is limited at 200 kHz.

d) for $f = 5$ kHz, the slew Rate limitation occurs at the value of v_i given by

$$\begin{aligned} \omega_i \times 10 v_i &= \text{SR} \Rightarrow v_i = \frac{1/10^{-6}}{2\pi \times 5 \times 10^3 \times 10} \\ &= 3.18 \text{ V} \end{aligned}$$

Such an input voltage, however would ideally result in an output of 31.8V which exceeds V_{omax} .

Thus $V_{imax} = \frac{V_{omax}}{10} = 1 \text{ V peak}$.