

2.28

From example 2.2

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

Here $R_1 = R_2 = R_4 = 1 \text{ M}\Omega$

$$\therefore \frac{v_o}{v_i} = -\left(1 + 1 + \frac{1}{R_3} \right) = -\left(2 + \frac{1 \text{ M}}{R_3} \right)$$

$$\frac{v_o}{v_i} + 2 = -\frac{1 \text{ M}\Omega}{R_3}$$

$$R_3 = -\frac{1 \text{ M}}{\left(\frac{v_o}{v_i} + 2 \right)}$$

a. $\frac{v_o}{v_i} = -200 \frac{\text{V}}{\text{V}}$

$$R_3 = -\frac{1 \text{ M}}{(-200 + 2)} = 5.05 \text{ k}\Omega$$

b. $\frac{v_o}{v_i} = -20 \frac{\text{V}}{\text{V}}$

$$R_3 = -\frac{1 \text{ M}}{(-20 + 2)} = 55.6 \text{ k}\Omega$$

c. $\frac{v_o}{v_i} = -2 \frac{\text{V}}{\text{V}}$ $R_3 = -\frac{1 \text{ M}\Omega}{(-2 + 2)} = \infty$

2.29

$$R_2 / R_1 = 1000, R_2 = 100 \text{ k}\Omega \Rightarrow R_1 = 1000 \Omega$$

a) $R_m = R_1 = 100 \Omega$

b) $\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right) = -1000$


If $R_2 = R_1 = R_4 = 100 \text{ K} \Rightarrow R_3 = \frac{100 \text{ K}}{1000 - 2} \approx 100 \Omega$

$R_m = R_1 = 100 \text{ k}\Omega$

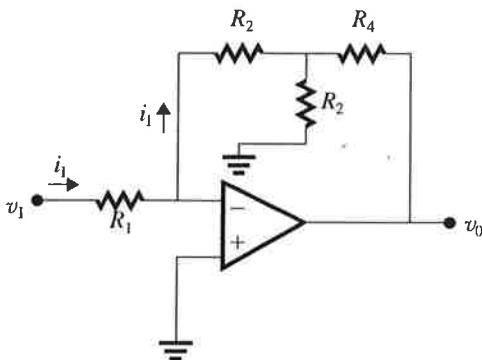2.30

$$i_i = \frac{v_i}{R_1}, v_x = -i_i R_2 = -\frac{v_i}{R_1} R_2$$

So $\frac{v_x}{v_i} = -\frac{R_2}{R_1}$ or $\frac{v_i}{v_x} = -\frac{R_1}{R_2}$



$$v_x = v_o \frac{(R_2 \parallel R_3)}{(R_2 \parallel R_3) + R_4}$$

$$= v_o \frac{R_2 R_3}{R_2 R_3 + R_2 R_4 + R_3 R_4}$$

$$\frac{v_o}{v_x} = \frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_2 R_3}$$

$$= 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2}$$

$$\frac{v_o}{v_i} = \frac{v_o / v_x}{v_i / v_x} = \frac{1 + \frac{R_4}{R_3} + \frac{R_4}{R_2}}{-\frac{R_1}{R_2}}$$

$$= -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_3} + \frac{R_4}{R_2} \right)$$

2.31

a) $R_1 = R$

$$R_2 = (R \parallel R) + \frac{R}{2} = \frac{R}{2} + \frac{R}{2} = R$$

$$R_3 = (R_2 \parallel R) + \frac{R}{2} = (R \parallel R) + \frac{R}{2} = R$$

$$R_4 = (R_3 \parallel R) + \frac{R}{2} = (R \parallel R) + \frac{R}{2} = R$$

b) $v = RI = RI_1 \Rightarrow I_1 = I$


$$I_{12} = I + I = 2I \Rightarrow v_1 + 2I \times \frac{R}{2} = RI_2$$

$$RI + RI = RI_2 \Rightarrow I_2 = 2I$$

$$I_{13} = I_2 + I_{12} = 4I \Rightarrow v_2 + 4I \times \frac{R}{2} = RI_3$$

$$R \times 2I + 4I \times \frac{R}{2} = RI_3 \Rightarrow I_3 = 4I,$$

$$I_4 = -(4I + 4I) I_4 = 8I$$

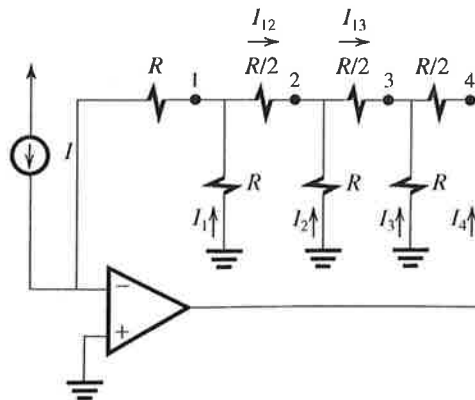


c) $v_1 = I_1 R = -IR$

$$v_2 = -I_2 R = -2IR$$

$$v_3 = -I_3 R = -4IR$$

$$v_4 = -I_3 R + I_4 \frac{R}{2} = -4IR + 8I \frac{R}{2} = -8IR$$

Short-circuit R_3 :

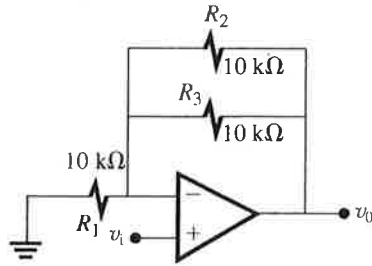

$$\frac{v_o}{v_i} = 1$$

2.46

$v_+ = v_- = v_o = R \times i$, $i = 100 \mu\text{A}$ when $v = 10\text{V}$

$$\Rightarrow R = \frac{10}{0.1 \text{ mA}} = 100 \text{ k}\Omega$$

As indicated, i only depends on R and v and the meter resistance does not affect i .

2.47

Refer to the circuit in P 2.47:

a) Using superposition, we first set

$v_{p1} = v_{p2} \dots = 0$. The output voltage that

results in response to $v_{N1}, v_{N2}, \dots, v_{Nn}$ is:

$$v_{ON} = -\left[\frac{R_F}{R_{N1}} v_{N1} + \frac{R_F}{R_{N2}} v_{N2} + \dots + \frac{R_F}{R_{Nn}} v_{Nn} \right]$$


Then we set $v_{N1} = v_{N2} = \dots = 0$, then:

$$R_N = R_{N1} \parallel R_{N2} \parallel R_{N3} \parallel \dots \parallel R_{Nn}$$

The circuit simplifies to:

$$v_{op} = \left(1 + \frac{R_F}{R_N} \right) \times$$
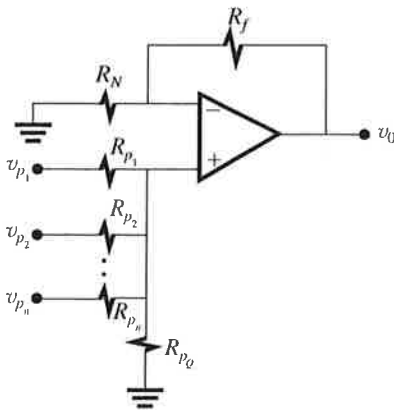
$$\left(v_{p1} \frac{1/R_{p1}}{\frac{1}{R_{p1}} + \frac{1}{R_{p2}} + \frac{1}{R_{pn}}} + v_{p2} \frac{1/R_{p2}}{\frac{1}{R_{p1}} + \dots + \frac{1}{R_{pn}}} \right)$$



$$\dots v_{pn} \frac{1/R_{pn}}{1/R_{p1} + \dots + \frac{1}{R_{pn}}}$$

$$v_{op} = \left(1 + \frac{R_F}{R_N} \right) \left(v_{p1} \frac{R_p}{R_{p1}} + v_{p2} \frac{R_p}{R_{p2}} + \dots + \frac{R_p}{R_{pn}} v_{pn} \right)$$

where:

$$R_p = R_{p1} \parallel R_{p2} \parallel \dots \parallel R_{pn}$$

when all inputs are present:

$$v_o = v_{ON} + v_{OP}$$

$$= -\left(\frac{R_F}{R_{N1}} v_{N1} + \frac{R_F}{R_{N2}} v_{N2} + \dots \right) +$$

$$\left(1 + \frac{R_F}{R_N} \right) \left(\frac{R_p}{R_{p1}} v_{N1} + \frac{R_p}{R_{p2}} v_{N2} + \dots \right)$$

b) $v_o = -2v_{n1} + v_{r1} + 2v_{r2}$


$$\frac{R_F}{R_{N1}} = 2, R_{N1} = 10 \text{ k}\Omega \Rightarrow R_F = 20 \text{ k}\Omega$$

$$\left(1 + \frac{R_F}{R_N} \right) \left(\frac{R_p}{R_{p1}} \right) = 1 \Rightarrow 3 \frac{R_p}{R_{p1}} = 1 \Rightarrow R_{p2} = \frac{R_{p1}}{2}$$

$$\left(1 + \frac{R_F}{R_N} \right) \left(\frac{R_p}{R_{p2}} \right) = 2 \Rightarrow 3 \frac{R_p}{R_{p2}} = 2 \Rightarrow R_{p2} = \frac{R_{p1}}{2}$$

where $R_p = \frac{R_{p1} \times R_{p2}}{R_{p1} + R_{p2}}$ (ignoring R_{p0})

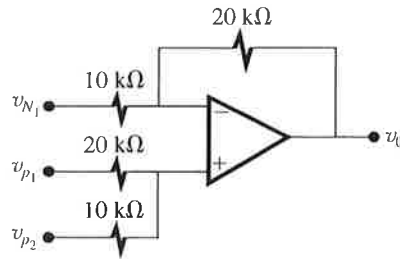Note that if the results from the last 2 constraints differ, we would use an additional resistor connected from the positive input to ground. (R_{p0})



2.48

$$v_o = v_{11} + 3v_{12} - 2(v_{13} + 3v_{14})$$

Refer to P2.47

$$\frac{R_F}{R_{N3}} = 2 \text{ if } R_{N3} = 10 \text{ k}\Omega \Rightarrow R_F = 20 \text{ k}\Omega$$




$$\frac{R_F}{R_{N4}} = 6 \Rightarrow R_{N4} = \frac{20}{6} = 3.3 \text{ k}\Omega$$

$$R_N = R_{N3} \parallel R_{N4} = 10 \text{ K} \parallel 3.3 \text{ k} = 2.48 \text{ k}\Omega$$

$$\left(1 + \frac{R_F}{R_N} \right) \frac{R_p}{R_o} = 1 \Rightarrow \left(1 + \frac{20}{2.48} \right) \frac{R_p}{R_{p1}}$$

$$= 1 \Rightarrow 9.06 R_p = R_{p1}$$
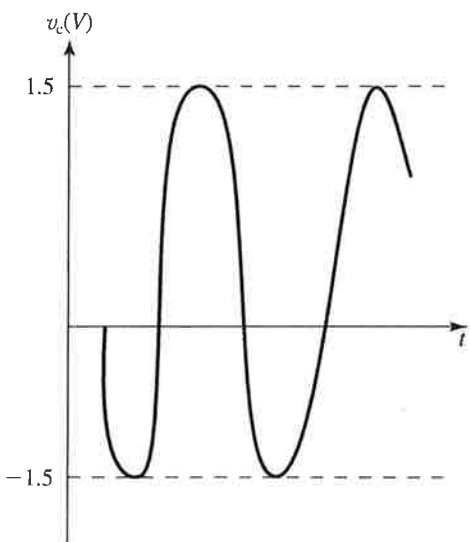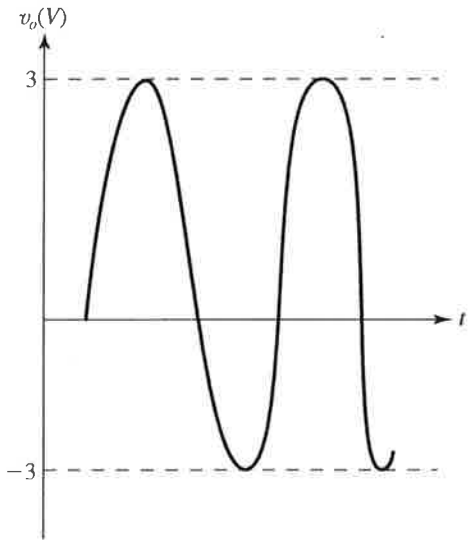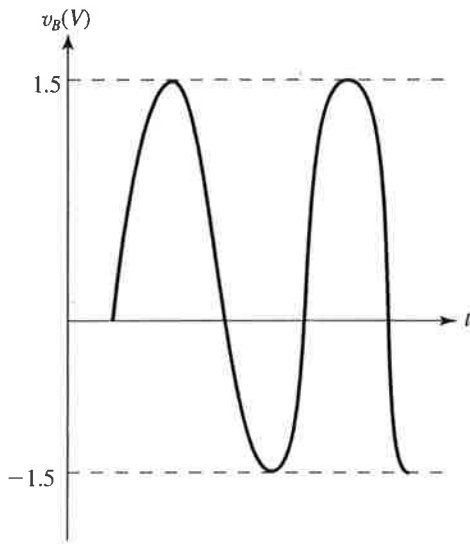
$$R_p = R_{p1} \parallel R_{p2} \parallel R_{p3} \Rightarrow R_p$$




c) v_B and v_C can be ± 14 V or 28 V P-P.

$-28 \leq v_o \leq 28$ or 56 VP-P.

$$v_{\text{rms}} = 19.8 \text{ V} = \frac{28}{\sqrt{2}}$$

2.78

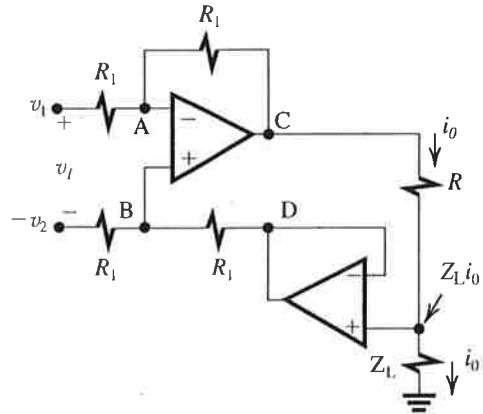

Refer to Fig. P.2.78.a:

Since the inputs of the op-amp do not draw any current, v_1 appears across R_1

$$i_o = \frac{v_1}{R}$$

Fig. P2.78.B

$$v_D = Z_L i_o$$

we use superposition:

$$v_1 = v_1 - v_2$$

$$v_1 \text{ only: } V_B = \frac{V_O}{2} = \frac{z_L i_{o1}}{2}$$

$$\frac{v_1 - \frac{z_L i_{o1}}{2}}{R_1} = \frac{\frac{z_L i_{o1}}{2} - i_{o1}(z_L + R)}{R_1}$$

$$\Rightarrow v_1 = i_{o1} R \Rightarrow i_{o1} = \frac{v_1}{R}$$

Now if only $(-v_2)$ is applied:

$$v_B = \frac{-v_2 + z_L i_{o2}}{2}, v_A = \frac{i_{o2} \times (R + z_L)}{2}$$

$$v_A = v_B \Rightarrow -v_2 + z_L i_{o2} = i_{o2} R + i_{o2} z_L$$

$$-v_2 = i_{o2} R \Rightarrow i_{o2} = \frac{-v_2}{R}$$


The total current due to both sources is:

$$i_o = i_{o1} + i_{o2} = \frac{v_1}{R} - \frac{v_2}{R} = \frac{v_1}{R}$$

The circuit in Figure P2.78(a) has ideally infinite input resistance, and it requires that both terminals of Z_L be available, while the other circuit has finite input resistance with one side of Z_L grounded.

see next page.

2.78 b)

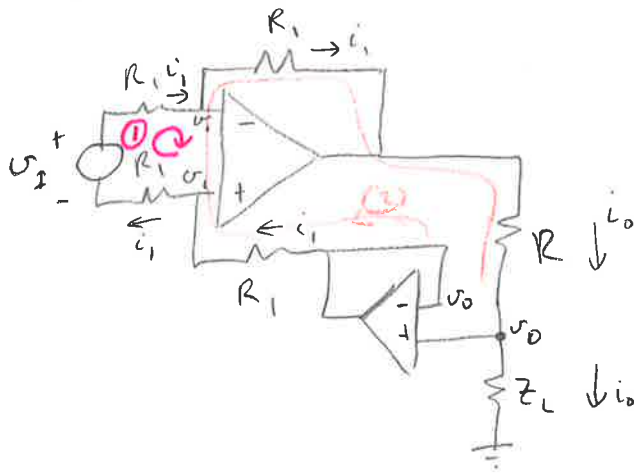

Equal currents + voltages are marked

KVL around loop 1

$$-i_1 R_1 + v_I - i_1 R_1 = 0$$

so $i_1 = \frac{v_I}{2R_1}$

KVL around loop 2

$$-i_1 R_1 - i_1 R_1 - i_o R = 0$$

$$-\frac{v_I}{2R_1} R_1 - \frac{v_I}{2R_1} R_1 - i_o R = 0$$

so $i_o = -\frac{v_I}{R}$

2.91

$RC = 10^{-3} \text{ s}$ when

$C = 10 \text{ mF} \Rightarrow R = 100 \text{ k}\Omega$

$\frac{v_o}{v_i} = -sRC, \frac{v_o}{v_i}(j\omega) = -j\omega RC$

$\phi = -90^\circ$ always

$\left| \frac{v_o}{v_i} \right| = 1 \Rightarrow \omega = \frac{1}{\text{unity } RC} = 1 \text{ krad/s}$

Gain is 10 times the unity gain, when = the frequency is 10 times the unity gain frequency. Similarly for $\omega = \frac{1}{10}$ krad/s, gain is 0.1 V/V. (for

$\omega = 10 \text{ krad/s}$, gain = 10 V/V)


for high frequency C is short circuited,

$\frac{v_o}{v_i} = \frac{-R}{R_1} = -100 \Rightarrow R_1 = 1 \text{ k}\Omega$

$\frac{v_o}{v_i} = \frac{-RCs}{R_1Cs + 1} = \frac{-10^{-3}s}{10^{-5}s + 1}$

$\Rightarrow \omega_{3db} = 100 \text{ krad/s}$ or

$f_{3db} = 15.9 \text{ kHz}$

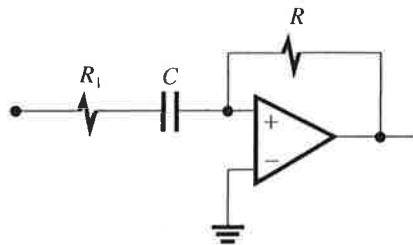


for unity gain:

$|10^{-3}s| = |10^{-5}s + 1| \Rightarrow \omega_H = 1.01 \text{ krad/s}$

if $\omega = 10.1 \text{ krad/s}$: $\left| \frac{v_o}{v_i} \right| = \frac{10.1}{1.01} = 10$,

$\phi = -95.77^\circ$


2.92

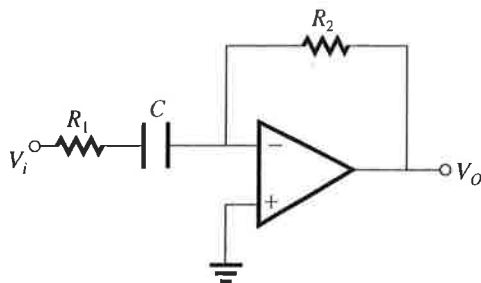

Let $Z_1 = R_1 + \frac{1}{sC}$, $Z_2 = R_2$

Gain = $\frac{v_o}{v_i} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1 + \frac{1}{sC}}$

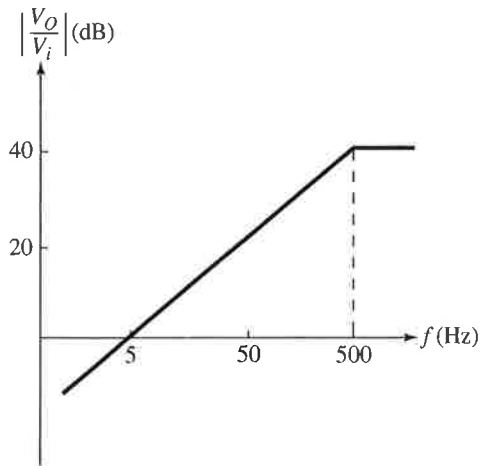$= \frac{-(R_2/R_1)s}{s + \frac{1}{R_1C}}$



This is the transfer function of a single time constant high pass filter having High frequency gain

$= (R_2/R_1)$ and 3dB frequency at $\omega_o = \frac{1}{R_1C}$.

At high frequency the input impedance

approaches R_1 as $20 \frac{1}{j\omega C}$ becomes very small

Select $R_1 = 10 \text{ k}\Omega$

Gain = 40 dB = 100 V/V

For a gain of 100, $\frac{R_2}{R_1} = 100$

and $R_1 = 10 \text{ k}\Omega$

$\therefore R_2 = 10 \text{ k}\Omega \times 100$

$= 1 \text{ M}\Omega$

For a 3dB frequency of 500 Hz

$\frac{1}{R_1C} = 2\pi \times 500$

$C = \frac{1}{2\pi \times 500 \times R_1} = 32 \text{ nF}$

From the Bode-plot the gain $\frac{v_o}{v_i}$ reduces to unity

at 5 Hz

2.93

Refer to the circuit in fig P 2.126:

$\frac{v_o}{v_i} = -\frac{Z_2}{Z_1} = -\frac{1}{Z_1 Y_2} = -\frac{1}{\left(R_1 + \frac{1}{sC_1}\right)\left(\frac{1}{R_2} + sC_2\right)}$

$\frac{v_o}{v_i} = -\frac{R_2/R_1}{\left(1 + \frac{1}{R_1C_1s}\right)\left(1 + sR_2C_2\right)}$

$$\frac{v_o(j\omega)}{v_i} = \frac{-R_2/R_1}{\left(1 + \frac{1}{j\omega R_1 C_1}\right)(1 + j\omega R_2 C_2)}$$

$$= \frac{-R_2/R_1}{\left(1 + \frac{\omega_1}{j\omega}\right)\left(1 + j\frac{\omega}{\omega_2}\right)}$$

where $\omega_1 = \frac{1}{R_1 C_1}$, $\omega_2 = \frac{1}{R_2 C_2}$

a) for $\omega = \omega_1 \ll \omega_2$

$$\frac{v_o(j\omega)}{v_i} \approx \frac{-R_2/R_1}{\left(1 + \frac{\omega}{j\omega_1}\right)} \approx \frac{-R_2 R_1}{\omega_1 / j\omega} \approx -j \frac{R_2}{R_1} \omega$$


b) for $\omega_1 \ll \omega \ll \omega_2$

$$\frac{v_o(j\omega)}{v_i} \approx -\frac{R_2}{R_1}$$

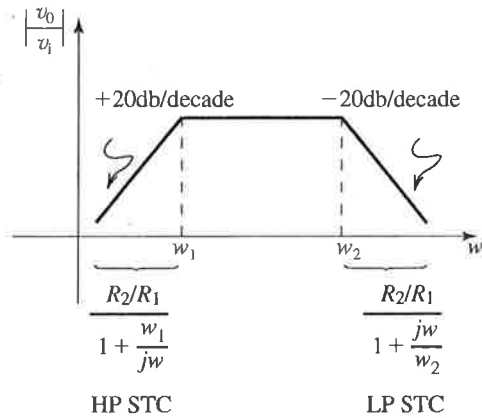c) for $\omega \gg \omega_2$ and $\omega_2 \gg \omega_1$:

$$\frac{v_o(j\omega)}{v_i} \approx \frac{-R_2 R_1}{1 + j\omega/\omega_2} \approx \frac{-R_2 R_1}{j\omega/\omega_2} = j \left(\frac{R_2}{R_1}\right) \left(\frac{\omega_2}{\omega}\right)$$

from the results of a), b) and c) we can draw the Bode-plot:



Design: $\frac{R_2}{R_1} = 1000$ (60 dB gain in the mid-frequency range)

R_{in} for $\omega \gg \omega_1$

$$= R_1 = 1 \text{ k}\Omega \Rightarrow R_2 = 1 \text{ M}\Omega$$

$$f_1 = 100 \text{ Hz} \Rightarrow \omega_1 = 2\pi \times 100 = \frac{1}{R_1 C_1}$$


$$\Rightarrow C_1 = 1.59 \text{ }\mu\text{F}$$

$$f_2 = 10 \text{ Hz} \Rightarrow \omega_2 = 2\pi \times 10 \times 10^3 = \frac{1}{R_2 C_2}$$

$$\Rightarrow C_2 = 15.9 \text{ pF}$$

2.94

Inverting configuration

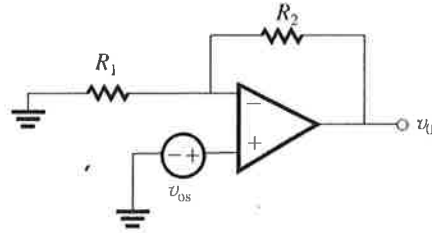

$$v_o = v_{OS} \left(1 + \frac{R_2}{R_1}\right)$$

$$-0.4 = v_{OS} \left(1 + \frac{100}{1}\right)$$

$$v_{OS} \approx 4 \text{ mV}$$

2.95

$$v_{OS} = \pm 2 \text{ mV}$$

$$v_o = 0.01 \sin \omega t \times 200 + v_{OS} \times 200$$

$$= 2 \sin \omega t \pm 0.4 \text{ V}$$

2.96

Input offset voltage = 5 mV

Output dc offset voltage =

$$5 \text{ mV} \times \text{closed loop gain}$$

$$= 5 \text{ mV} \times 1000$$

$$= 5 \text{ V}$$


The maximum amplifier of an input sinusoid that results in an output peak amplifier of $13 - 5 = 8 \text{ V}$ is given by:

$$v_i = \frac{8}{1000} = 8 \text{ mV}$$

If amplifier is capacitively coupled then


$$v_{i \text{ max}} = \frac{13}{1000} = 13 \text{ mV}$$

2.97

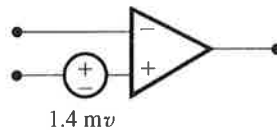


$$v_{OS} = \frac{1.4}{100} = 1.4 \text{ mV}$$

2.98

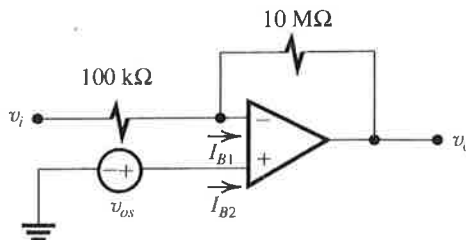

4.1

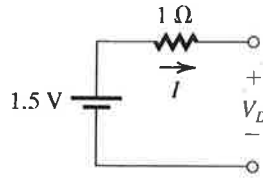

The diode can be reverse-biased and thus no current would flow, or forward-biased where current would flow.

- (a) Reverse biased $I = 0A$ $V_D = 1.5V$
- (b) Forward biased $I = 1.5A$ $V_D = 0V$

4.2

(a) Diode is conducting and thus has a 0V drop across it. Consequently

$$V = -5V$$

$$I = \frac{5 - (-5)}{10 \text{ k}\Omega} = 0.1 \text{ mA}$$

(b) Diode is cut off.

$$V = 5V \quad I = 0A$$

(c) Diode is conducting

$$V = 5V$$


$$I = \frac{5 - (-5)}{10 \text{ k}\Omega} = 0.1 \text{ mA}$$

(d) Diode is cut off.


$$V = -5V \quad I = 0A$$

4.3

(a)

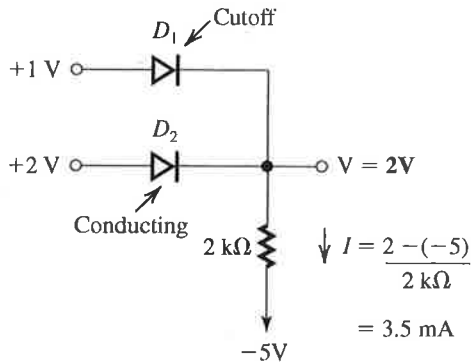


(b)

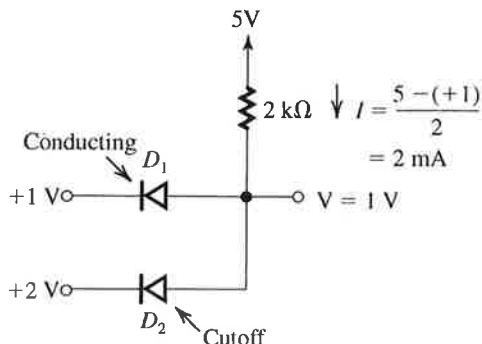

4.4


(a)

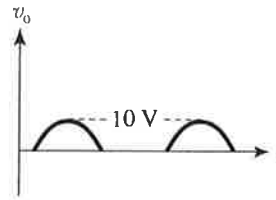

$$V_{p+} = 10V \quad V_{p-} = 0V$$

$$f = 1 \text{ kHz}$$


(b)

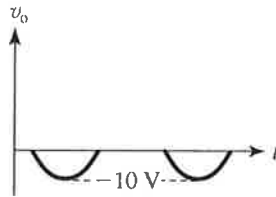

$$V_{p+} = 0V \quad V_{p-} = -10V$$

$$f = 1 \text{ kHz}$$


(c)

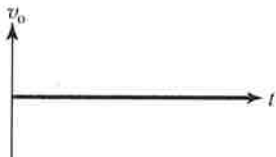

$$v_o = 0V$$

Neither D_1 nor D_2 conducts so there is no output.


(d)

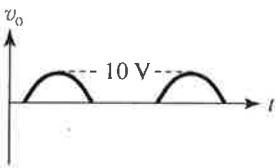

$$V_{p+} = 10V \quad V_{p-} = 0V \quad f = 1 \text{ kHz}$$

Both D_1 and D_2 conduct when $V_I > 0$

(e)

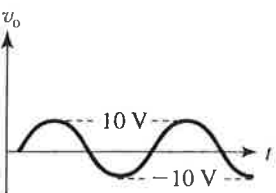

$$i_{B(\text{avg})} = \frac{\pi - 2 \arcsin(3/10)}{2\pi} \cdot 60 \text{ mA} = 24.2 \text{ mA}$$

For peak V_i reduced by 10%

$$i_{B(\text{peak})} = 60 \text{ mA}$$

$$i_{B(\text{avg})} = \frac{\pi - 2 \arcsin(3/9)}{2\pi} \cdot 60 \text{ mA} = 23.5 \text{ mA}$$

4.6

	A	B	x	y
	0	0	0	0
	0	1	0	1
	1	0	0	1
	1	1	1	1

$$x = A B \quad y = A + B$$

x and y are the same for

$$A = B$$

x and y are opposite if $A \neq B$

4.7

The case for the highest current in a single diode is when only one input is high:

$$V_y = 5 \text{ V}$$

$$\frac{V_y}{R} \leq 0.2 \text{ mA} \Rightarrow R \geq 25 \text{ k}\Omega$$

4.8


The maximum input current occurs when one input is low and the other two are high.

$$\frac{5 - 0}{R} \leq 0.1 \text{ mA}$$


$$R \geq 50 \text{ k}\Omega$$

4.9

(a)

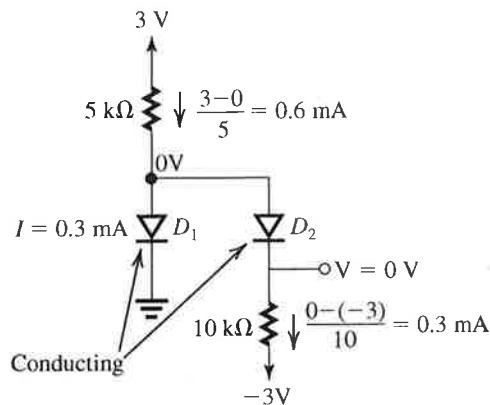


(b)

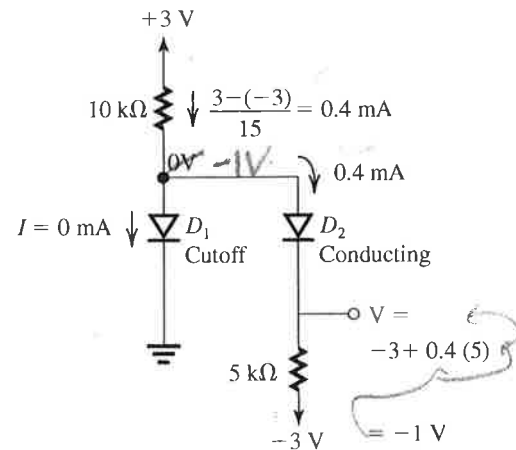

4.10


(a)

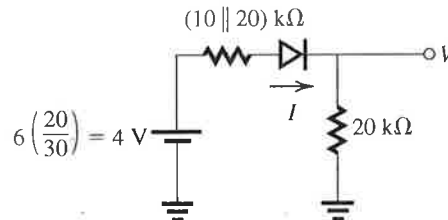

$$I = \frac{4}{(10 \parallel 20) + 20} = 0.15 \text{ mA}$$

$$V = \frac{20}{(10 \parallel 20) + 20} \times 4 = 3 \text{ V}$$

(b)

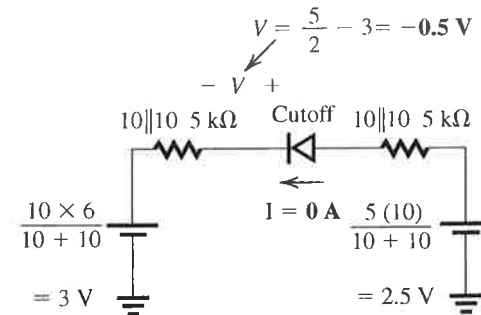


4.11

$$R \geq \frac{120\sqrt{2}}{50} \geq 3.4 \text{ k}\Omega$$

The largest reverse voltage appearing across the diode is equal to the peak input voltage

$$120\sqrt{2} = 169.7 \text{ V}$$

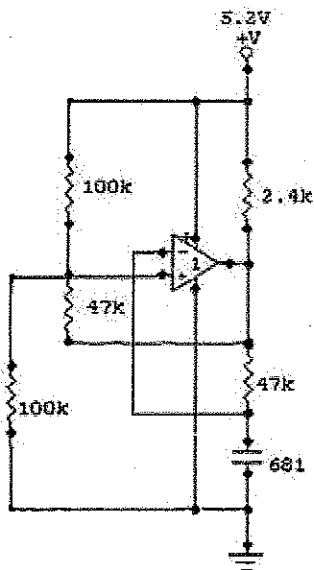


This is relaxation oscillator, similar to lab

$$V_{+, H1} = 5.2 \cdot \frac{100}{100 + 100 + 50} = 3.9V$$

approx $47k \approx 50k$
 $47 + 2.4k \approx 50k$

$$V_{+, L0} = 5.2 \cdot \frac{100 + 50}{100 + 100 + 100} = 1.3$$
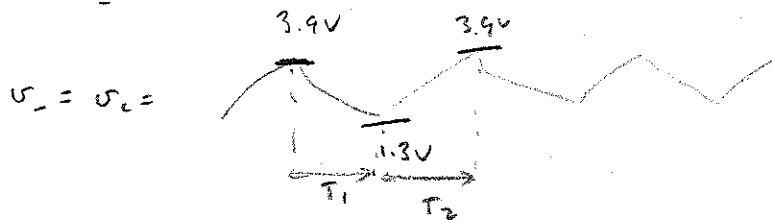
$$\text{let } \tau = 680 \text{ pF} \cdot 50k \approx .034 \text{ m sec}$$



$$V(t) = V(\infty) + (V(0) - V(\infty))e^{-t/\tau}$$

$$\frac{V(t) - V(\infty)}{V(0) - V(\infty)} = e^{-t/\tau}$$

$$t = \tau \ln \left(\frac{V(\infty) - V(t)}{V(\infty) - V(0)} \right)$$

$$T_1 = .034 \text{ ms} \cdot \ln \left(\frac{3.9 - 0}{1.3 - 0} \right) = .037 \text{ ms}$$

$$T_2 = .034 \cdot \ln \left(\frac{1.3 - 5}{3.9 - 5} \right) = .041 \text{ ms}$$

$$f_{\text{freq}} = \frac{1}{.037 + .041} = 12.8 \text{ kHz}$$

So ... we get approx a 12.8 kHz triangle wave generator from 1.3V to 3.9V

