

STRING OF LED'S


D1 + C1 FORM A RECTIFIER/FILTER
TO GET A DC LEVEL.

THE IDEA SEEMS TO BE TO
LIGHT UP MORE LED'S AS THE INPUT
VOLTAGE INCREASES.

HOWEVER, THE VOLTAGE AT
A NODE OF D2 IS ALMOST CONSTANT
(2 DIODE DROPS) SO ~~D3-D4-D24~~ WILL
PROBABLY NEVER TURN ON (OR ONLY BARELY)

D28 WILL CERTAINLY NEVER LIGHT.

WEEK 3

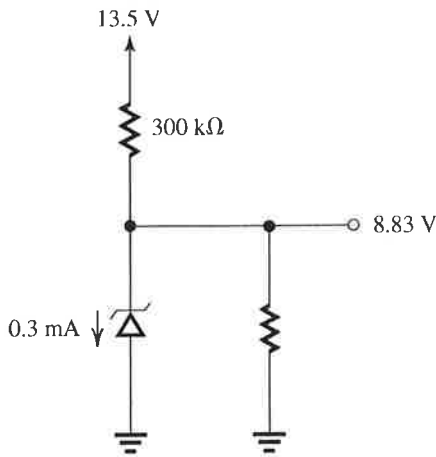

Lowest output voltage = 8.83 V

$$\text{Line Regulation} = \frac{r_z}{R + r_z} = \frac{30}{300 + 30}$$

$$= 90 \frac{\text{mV}}{\text{V}}$$

$$\text{Load Regulation} = -(r_z \parallel R) = -29.1 \frac{\text{mV}}{\text{mA}}$$


4.64

(a) $V_{ZT} = V_{ZO} + r_z I_{ZT}$

$$10 = V_{ZO} + 7(0.025)$$

$$\Rightarrow V_{ZO} = 9.825 \text{ V}$$

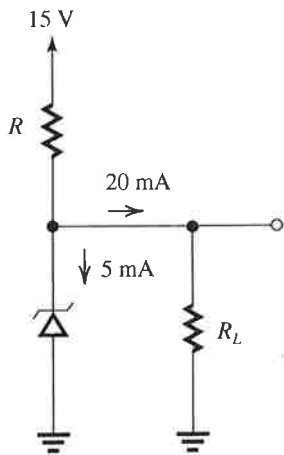(b) The minimum zener current of 5 mA occurs when $I_L = 20 \text{ mA}$ and V_S is at its minimum of $20(1 - 0.25) = 15 \text{ V}$. see the circuit below:



$$R \leq \frac{15 - (V_{ZO} + r_z I_Z)}{20 + 5}$$

$$\leq \frac{15 - (9.825 + 7(0.005))}{25}$$

$$\leq 205.6 \Omega.$$

\therefore use $R = 205 \Omega$

(c) Line regulation = $\frac{7}{205 + 7} = 33 \frac{\text{mV}}{\text{V}}$

$\pm 25\%$ change in $v_S \equiv \pm 5 \text{ V}$

V_O changes by $\pm 5 \times 33 = \pm 165 \text{ mV}$

corresponding to $\frac{\pm 165}{10} \times 100 = \pm 1.65\%$

(d) Load Regulation = $-(r_z \parallel R)$

$$= -(7 \parallel 205) = -6.77 \Omega$$

or -6.77 V/A


$$\Delta V_O = -6.77 \times 20 \text{ mA} = -135.4 \text{ mV}$$

corresponding to $-\frac{0.1354}{10} \times 100 = -1.35\%$

(e) The maximum zener current occurs at no load $\equiv I_L = 0$ and the supply at

$$20 + \frac{1}{4}(20) = 25 \text{ V}.$$

$$V_Z = V_{ZO} + r_z I_Z$$

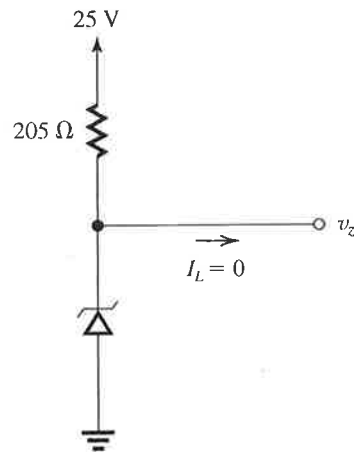

$$= 9.825 + 7 \times \frac{25 - V_Z}{205}$$


$$205 V_Z = 205(9.825) + 7(25) - 7V_Z$$

$$\Rightarrow V_Z = 10.326 \text{ V}$$

$$P_Z = 10.326 \times \left(\frac{25 - 10.326}{205} \right)$$

$$= 739.4 \text{ mW}$$

Alternate circuit to calculate V_Z

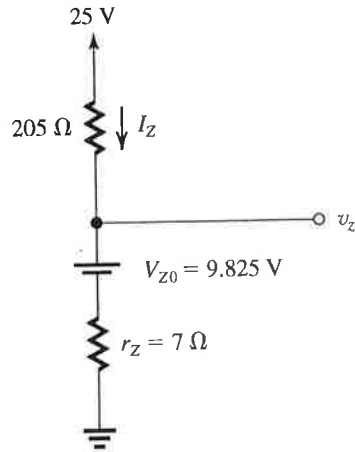

$$I_Z = \frac{25 - V_{Z0}}{205 + 7}$$

$$= \frac{25 - 9.825}{205 + 7}$$

$$= 71.6 \text{ mA}$$


$$V_Z = V_{Z0} + I_Z r_Z$$

$$= 9.825 + 0.0716 \times 7$$


$$= 10.326 \text{ V}$$

as above!


4.65

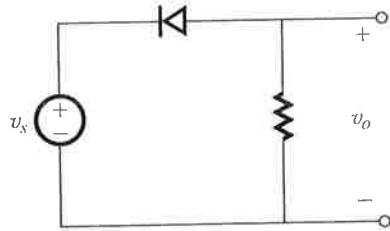


using the constant voltage drop model:

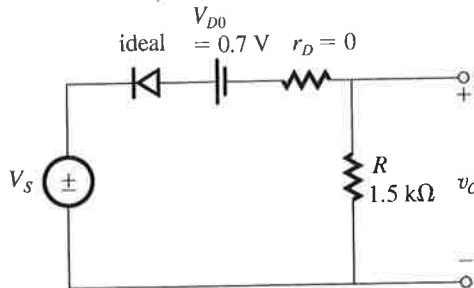

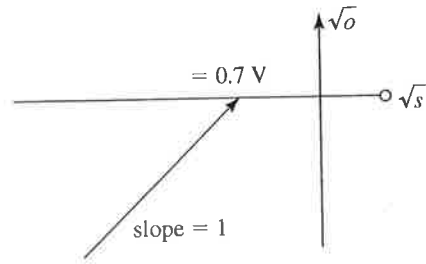(a) $v_o = v_s + 0.7 \text{ V}$, For $v_s \leq -0.7 \text{ V}$
 $v_o = 0$, for $v_s \geq -0.7 \text{ V}$



(b)

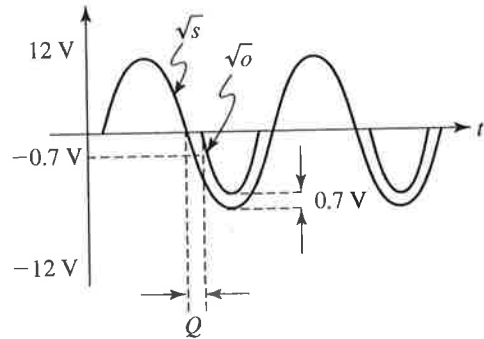

(c) The diode conducts at an angle

$$\theta = \sin^{-1}\left(\frac{0.7}{12}\right) = 3.34^\circ \text{ \& stops}$$

at $\pi - \theta = 176.65^\circ$
 Thus the conduction angle is $\pi - 2\theta$
 $= 173.31^\circ$ or 3.025 rad.

$$v_{o, \text{avg}} = \frac{-1}{2\pi} \int_{\theta}^{\pi - \theta} (12 \sin \phi - 0.7) d\phi$$

$$= \frac{-1}{2\pi} [-12 \cos \phi - 0.7\phi]_{\theta}^{\pi - \theta}$$

$$= \frac{-1}{2\pi} [12 \times 2 \cos \theta - 0.7(\pi - 2\theta)]$$

$$= -4.572 \text{ V}$$

(d) Peak current in diode is:

$$\frac{12 - 0.7}{1.5 \times 10^3} = 2.53 \text{ mA}$$

(e) PIV occurs when v_s is at its the peak and

$$v_o = 0.$$

$$\text{PIV} = 12 \text{ V}$$

(b) For $v_{o,avg} = 100 \text{ V}$

$$V_s = \frac{\pi}{2} \times 101.4 = 159.3 \text{ V}$$

$$\text{Turns Ratio} = \frac{120\sqrt{2}}{159.3} = 1.065 \text{ to } 1$$

4.72

Refer to Fig. 4.23

For $2V_{D0} \ll V_s$

$$V_{o,avg} = \frac{2}{\pi} V_s - 2V_{D0} = \frac{2}{\pi} V_s - 1.4$$

(a) For $V_{o,avg} = 10 \text{ V}$

$$10 \text{ V} = \frac{2}{\pi} \cdot V_s - 1.4$$

$$\therefore V_s = 11.4 \left(\frac{\pi}{2} \right) = 17.9 \text{ V}$$

$$\text{Turns ratio} = \frac{120\sqrt{2}}{17.9} = 9.5 \text{ to } 1$$

(b) For $V_{o,avg} = 100 \text{ V}$

$$100 \text{ V} = \frac{2}{\pi} \cdot V_s - 1.4$$

$$\Rightarrow V_s = 101.4 \left(\frac{\pi}{2} \right) = 159 \text{ V}$$

$$\text{Turns ratio} = \frac{120\sqrt{2}}{159} = 1.07 \text{ to } 1$$

4.73

$$120\sqrt{2} \pm 10\% : 24\sqrt{2} \pm 10\%$$

$$\Rightarrow \text{turns Ratio} = 5:1$$

$$v_s = \frac{24\sqrt{2}}{2} \pm 10\%$$

$$\text{PIV} = 2V_{s|\text{max}} - V_{D0}$$




$$= 2 \times \frac{24\sqrt{2}}{2} \times 1.1 - 0.7$$

$$= 36.6 \text{ V}$$

using a factor of 1.5 for safety we select a diode having a PIV rating of 55 V

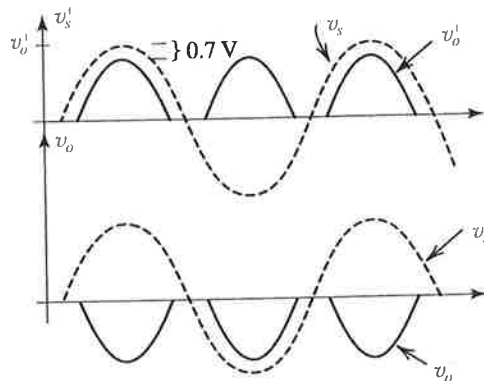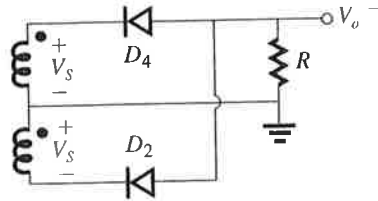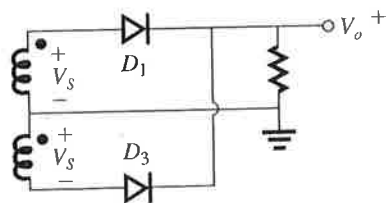4.74

The circuit is a full wave rectifier with centre tapped secondary winding. The circuit can be analyzed by looking at v_o^+ and v_o^- separately.



$$v_{o,avg} = \frac{1}{2\pi} \int (V_s \sin \phi - 0.7) d\phi = 15$$

$$= \frac{2V_s}{\pi} - 0.7 = 15$$

assumed $V_s \gg 0.7 \text{ V}$

$$V_s = \frac{15 + 0.7}{2} \pi = 24.66 \text{ V}$$

Thus voltage across secondary winding

$$= 2V_s = 49.32 \text{ V}$$

Looking at D_4

$$\text{PIV} = V_s - V_o^-$$

$$= V_s + (V_s - 0.7)$$


$$= 2V_s - 0.7$$


$$= 48.6 \text{ V}$$

If choosing a diode, allow a safety margin of

$$1.5\text{PIV} = 73 \text{ V}$$

4.75

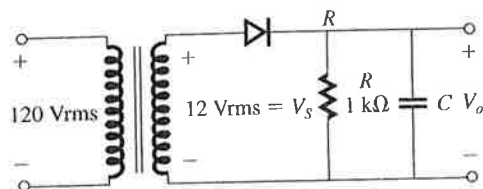

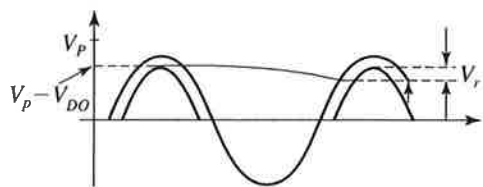

$$(i) v_r \cong (V_P - V_{DO}) \frac{T}{CR} \text{ Eq. (4.28)}$$

$$0.1(V_P - V_{DO}) = (V_P - V_{DO}) \frac{T}{CR}$$

$$C = \frac{1}{0.1 \times 60 \times 10^3} = 166.7 \mu\text{F}$$

(ii) for

$$v_r = 0.01(V_P - V_{DO}) = \frac{(V_P - V_{DO})T}{CR}$$

(a)

$$\begin{aligned} (i) v_{O, \text{avg}} &= V_P - V_{DO} - \frac{1}{2}V_r \\ &= 12\sqrt{2} - 0.7 - \frac{1}{2}(12\sqrt{2} - 0.7)0.1 \\ &= (12\sqrt{2} - 0.7)\left(1 - \frac{0.1}{2}\right) \\ &= 15.5 \text{ V} \end{aligned}$$

$$\begin{aligned} (ii) v_{O, \text{avg}} &= (12\sqrt{2} - 0.7)\left(1 - \frac{0.01}{2}\right) \\ &= 16.19 \text{ V} \end{aligned}$$

(b)

i) using eq (4.30) we have the conduction angle =

$$\begin{aligned} \omega\Delta t &\cong \sqrt{2V_r I (V_P - V_{DO})} \\ &= \sqrt{\frac{2 \times 0.1(V_P - 0.7)}{(V_P - 0.7)}} \\ &= \sqrt{0.2} \\ &= 0.447 \text{ rad} \end{aligned}$$

\(\therefore\) Fraction of cycle for

$$\begin{aligned} \text{conduction} &= \frac{0.447}{2\pi} \times 100 \\ &= 7.1\% \end{aligned}$$

$$(ii) \omega\Delta t \cong \sqrt{2 \times 0.01 \frac{(V_P - 0.7)}{V_P - 0.7}} = 0.141 \text{ rad}$$

$$\text{Fraction of cycle} = \frac{0.141}{2\pi} \times 100 = 2.25\%$$

(c)(i) use eq (4.31)

$$\begin{aligned} i_{D, \text{avg}} &= I_L \left(1 + \pi \sqrt{\frac{2(V_P - V_{DO})}{V_r}}\right) \\ &= \frac{V_{O, \text{avg}}}{R} \left(1 + \pi \sqrt{\frac{2(V_P - V_{DO})}{0.1(V_P - V_{DO})}}\right) \\ &= \frac{15.5}{10^3} \left(1 + \pi \sqrt{\frac{2}{0.1}}\right) \\ &= 233 \text{ mA} \end{aligned}$$

$$\begin{aligned} (ii) i_{D, \text{avg}} &= \frac{16.19}{10^3} (1 + \pi \sqrt{200}) \\ &= 735 \text{ mA} \end{aligned}$$

$$\text{NB next user } I_L \cong V_P/R = \frac{V_P - V_{DO}}{R}$$

$$\text{but here are used } i_{D, \text{avg}} = \frac{V_P - V_{DO} - \frac{1}{2}V_r}{R}$$

which is more accurate.

$$\begin{aligned} (d) (i) i_{D, \text{peak}} &= I_L \left(1 + 2\pi \sqrt{\frac{2(V_P - V_{DO})}{V_r}}\right) \\ &= \frac{15.42}{10^3} \left(1 + 2\pi \sqrt{\frac{2}{0.1}}\right) \\ &= 449 \text{ mA} \end{aligned}$$

$$\begin{aligned} (ii) i_{D, \text{peak}} &= \frac{16.19}{10^3} \left(1 + 2\pi \sqrt{\frac{2}{0.01}}\right) \\ &= 1455 \text{ mA} \end{aligned}$$

4.76

$$(i) v_r = 0.1(V_P - V_{DO}) = \frac{(V_P - V_{DO})}{2fCR}$$

The factor of 2 accounts for discharge occurring only half of the period $T/2 = \frac{1}{2f}$

$$C = \frac{1}{(2fR)0.1} = \frac{1}{2(60)10^3 \times 0.1} = 83.3 \mu\text{F}$$

$$(ii) C = \frac{1}{2(60)10^3 \times 0.01} = 833 \mu\text{F}$$

$$(a) i) V_O = V_P - V_{DO} - \frac{1}{2}v_r$$

$$= (V_P - V_{DO})\left(1 - \frac{0.1}{2}\right)$$

$$= (16.27)\left(1 - \frac{0.1}{2}\right)$$

$$= 15.5 \text{ V}$$

$$(ii) V_O = (16.27)\left(1 - \frac{0.01}{2}\right) = 16.19 \text{ V}$$

(b)

$$(i) \text{ Fraction of cycle} = \frac{2\omega\Delta t}{2\pi} \times 100$$

$$= \sqrt{\frac{2V_r/(V_p - V_{DO})}{\pi}} \times 100$$

$$= \frac{1}{\pi} \sqrt{2(0.1)} \times 100 = 14.2\%$$

$$(ii) \text{ Fraction of Cycle} = \frac{2\sqrt{2(0.01)}}{2\pi} \times 100$$

$$= 4.5\%$$

(c) use eq (4.34)

$$(i) i_{D, \text{avg}} = I_L \left(1 + \pi \sqrt{\frac{V_p - V_{DO}}{2V_r}} \right)$$

$$= \frac{15.5}{1} \left(1 + \pi \sqrt{\frac{1}{2(0.1)}} \right) = 124.4 \text{ mA}$$

$$(ii) i_{D, \text{avg}} = \frac{16.19}{1} \left(1 + \pi \frac{1}{\sqrt{2(0.01)}} \right) = 376 \text{ mA}$$

(d) use eq(4.35)

$$(i) \hat{i}_D = I_L \left(1 + 2\pi \frac{1}{\sqrt{2(0.1)}} \right) = 233 \text{ mA}$$

$$(ii) \hat{i}_D = I_L \left(1 + 2\pi \frac{1}{\sqrt{0.02}} \right) = 735 \text{ mA}$$

4.77

$$1) v_r = 0.1(V_p - V_{DO} \times 2) = \frac{V_p 2V_{DO}}{2fCR}$$

$$\text{discharge occurs only over } \frac{1}{2} T = \frac{1}{2f}$$

$$C = \frac{(V_p - 2V_{DO})}{(V_p - 2V_{DO})} \frac{1}{2(0.1)fR} = 83.3 \mu\text{F}$$

$$(ii) C = \frac{1}{2(0.01)fR} = 833 \mu\text{F}$$

$$(b) (i) \text{ Fraction of cycle} = \frac{2\omega\Delta t}{2\pi} \times 100$$

$$= \sqrt{\frac{2(0.1)}{\pi}} \times 100 = 14.2\%$$

(ii) Fraction of cycle

$$= \sqrt{\frac{2(0.01)}{\pi}} \times 100 = 4.5\%$$


$$(c) (i) i_{D, \text{avg}} = \frac{14.79}{1} \left(1 + \pi \sqrt{\frac{1}{0.2}} \right) = 119 \text{ mA}$$

$$(ii) i_{D, \text{avg}} = \frac{15.49}{1} (1 + \pi/\sqrt{0.02}) = 356 \text{ mA}$$

$$(d) (i) \hat{i}_D = \frac{14.79}{1} \left(1 + 2\pi \sqrt{\frac{1}{0.2}} \right) = 223 \text{ mA}$$

$$(ii) \hat{i}_D = \frac{15.49}{1} \left(1 + 2\pi \sqrt{\frac{1}{0.02}} \right) = 704 \text{ mA}$$

4.78

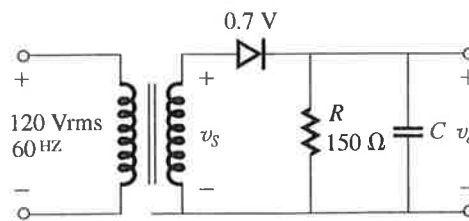

$$v_{O, \text{peak}} = V_p - V_{DO} = 16$$


$$V_p = 16.7 \text{ V}$$

$$V_{\text{rms}} = \frac{16.7}{\sqrt{2}} = 11.8$$

$$(b) V_r = (V_p - V_{DO}) \frac{T}{CR} \text{ Eq (4.28)}$$

$$2 = \frac{16}{60 \times C \times 150}$$

$$C = 889 \mu\text{F}$$

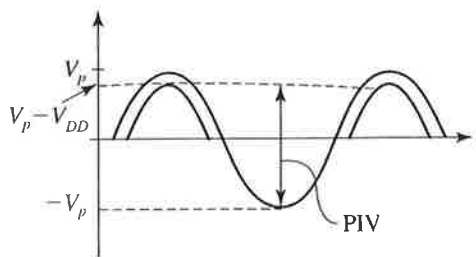

$$\text{PIV} = V_p - V_{DO} - V_r/2 + V_p$$

$$= V_{O, \text{avg}} + V_p$$

$$= 15 + 16.7$$

$$= 31.7 \text{ V}$$

$$\text{For a 50\% safety margin PIV} = 1.5 \times 31.7$$

$$= 47.6 \text{ V}$$

$$(d) i_{D, \text{avg}} = I_L \left(1 + \pi \sqrt{\frac{2(V_p - V_{DO})}{V_r}} \right)$$

$$\text{using } I_L = \frac{v_{O, \text{avg}}}{R} = \frac{15}{R} \text{ we have}$$



$$i_{D, \text{avg}} = \frac{15}{150} \left(1 + \pi \sqrt{\frac{2(16)}{2}} \right)$$

$$= 1.36 \text{ A}$$




$$(e) i_{D, \text{peak}} = I_L \left(1 + 2\pi \sqrt{\frac{2(V_p - V_{DO})}{V_r}} \right)$$

$$= \frac{15}{150} \left(1 + 2\pi \sqrt{\frac{2(16)}{2}} \right)$$


$$= 2.61 \text{ A}$$

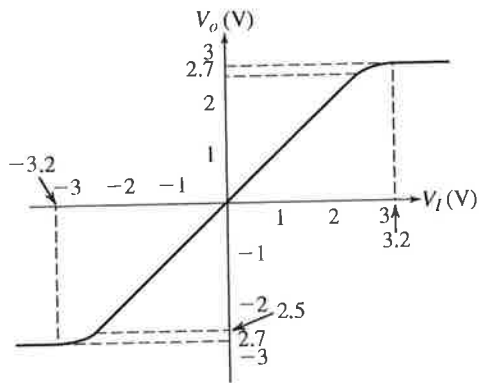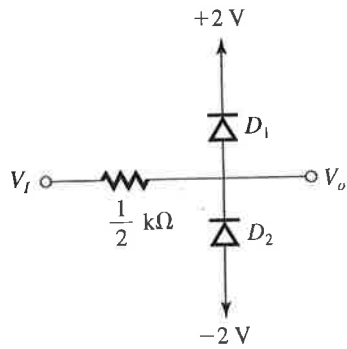


4.87

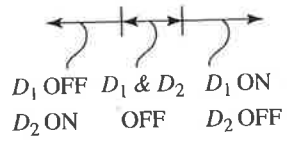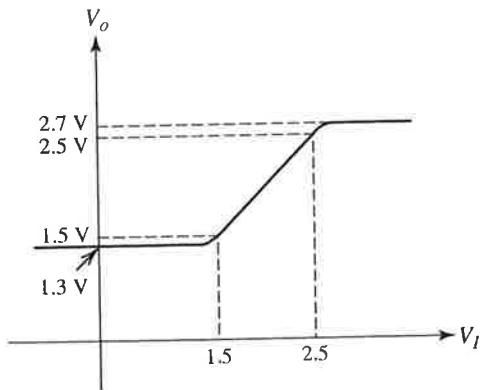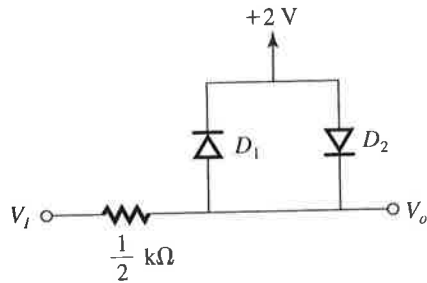


4.88

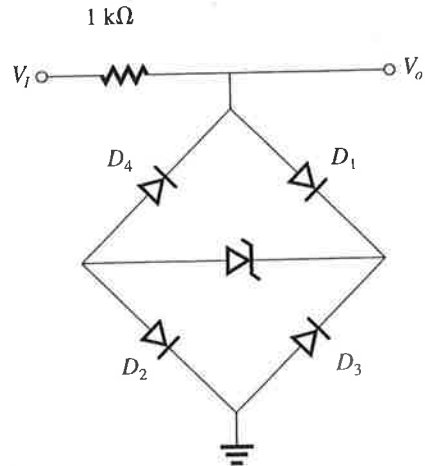

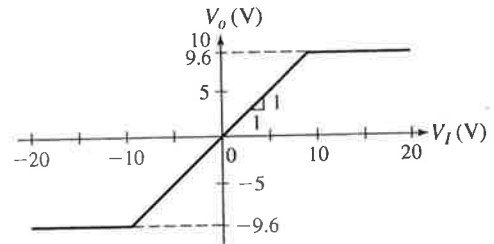Each diode has 0.7 V drop when conducting
The Zener has 8.2 V drop when conducting. So the limiter thresholds are
 $\pm(2 \times 0.7 + 8.2) = \pm 9.6$ V



4.89

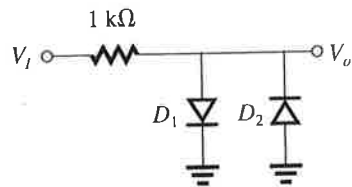

Diodes have 0.7 V drop at 1 mA current


\therefore For diode D_1

$$\frac{i_D}{1 \text{ mA}} = e^{(v_O - 0.7)/V_T}$$

$$i_D = 1 \times 10^{-3} e^{(v_O - 0.7)/V_T}$$

Solution: Problem B) What does the portion of the circuit shown below do? Assume a 1W zener (19mA max), so that we want at least 1.9mA flowing through the zener at all times. You also know that the resistor can dissipate a maximum of 1W before overheating.

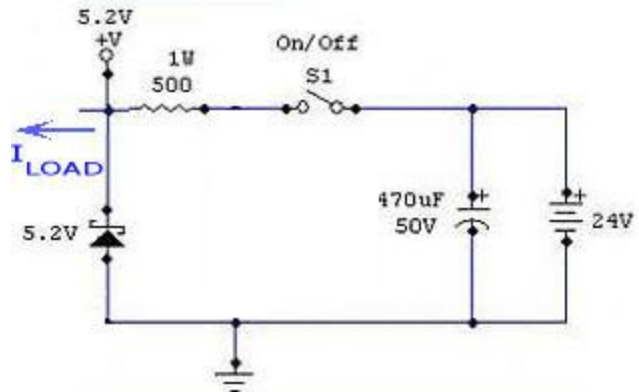This circuit creates a lower voltage (5.2V) regulated power supply from the much higher voltage (24V) battery – also battery voltages change with load, so the 24V is only nominal.



1. How much current goes through the Zener when $I_{LOAD}=0$?

$$I_{500\Omega} = \frac{24 - 5.2}{500} = 37.6\text{mA}$$

$$I_{Zener} + I_{Load} = I_{500\Omega}$$

$$I_{Zener, \text{no load}} = I_{500\Omega} = 37.6\text{mA}$$

Note – this would destroy the zener, so some current must be flowing in load.

2. What is the maximum value for I_{LOAD} before the power supplies fails?

$$I_{Zener, \text{min}} + I_{Load, \text{max}} = I_{500\Omega} = 37.6\text{mA}$$

$$I_{Load, \text{max}} = I_{500\Omega} - I_{Zener, \text{min}} = 37.6\text{mA} - 1.9\text{mA} = 35.7\text{mA}$$

3. For this maximum current compare the power dissipated in the load ("useful power") to the power dissipated in the 500Ω resistor ("wasted power") and calculate the efficiency, $\eta = \text{useful power} / \text{total power}$.

$$P_{Load, \text{max}} = I_{Load, \text{max}} \cdot 5.2\text{V} = 35.7\text{mA} \cdot 5.2\text{V} = 186\text{mW}$$

$$P_{500\Omega} = I_{500\Omega} \cdot 24 - 5.2 = 37.6\text{mA} \cdot 18.8\text{V} = 707\text{mW}$$

$$P_{Zener} = I_{Zener, \text{min}} \cdot 5.2\text{V} = 1.9\text{mA} \cdot 5.2\text{V} = 10\text{mW}$$

$$\eta = \frac{P_{Load, \text{max}}}{P_{Load, \text{max}} + P_{500\Omega} + P_{Zener}} = \frac{186}{186 + 707 + 10}$$

$$= \frac{186}{903} = 0.206 \approx 21\%$$

Note that this is the maximum efficiency. If the load current drops, so does the efficiency.

Also – it is OK if you didn't include P_{Zener} . I didn't include it in the original problem statement (but it doesn't change the answer much).