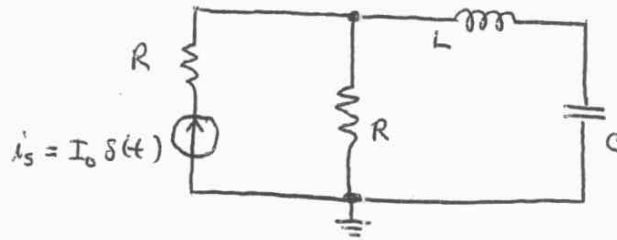


EXAM 3, part 2
CLOSED BOOK, CLOSED NOTES, CLOSED MOUTHS

Due at 5PM on Friday, December 6, 2002

1. Find the impulse response of the circuit below. Let $R = L = C = 1$ (with appropriate units). The source is a current $i_s(t) = I_0 \delta(t)$. Find $v_c(t)$ for $t > 0$. Please also explain which other element(s) will experience the impulse in current passing through it/them.


$$i_L(0^-) = i_C(0^+) = 0$$



EXAM 3, part 2

2. Find the complete response of the circuit shown below. A switch closes at time $t = 0$ to connect the source $v_s(t) = V_0\sqrt{2} * \cos(t)$. Let $R = L = C = 1$ (with appropriate units).

$$i_L(0^-) = v_C(0^-) = 0$$

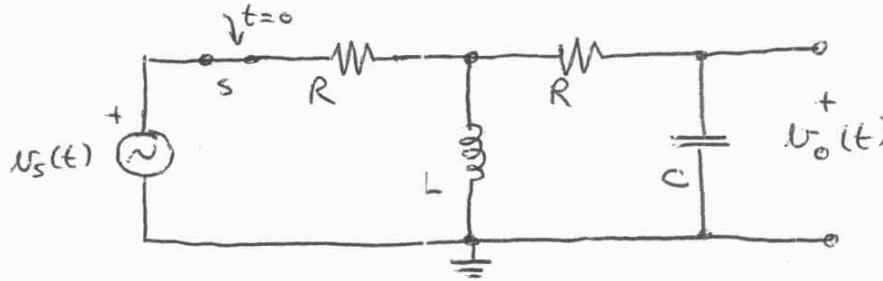


EXAM 3, part 2
CLOSED BOOK, CLOSED NOTES, CLOSED MOUTHS

Due at 5PM on Friday, December 6, 2002

1. Find the impulse response of the circuit below. Let $R = L = C = 1$ (with appropriate units). The source is a current $i_s(t) = I_0 \delta(t)$. Find $v_c(t)$ for $t > 0$. Please also explain which other element(s) will experience the impulse in current passing through it/them.

$$i_L(0^-) = i_C(0^-) = 0$$

R in series w/ source is irrelevant.

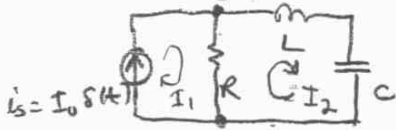

$$-R(I_2 - I_0 \delta(t)) - L \frac{dI_2}{dt} - \frac{1}{C} \int I_2 dt = 0$$

$$\frac{dI_2}{dt} + \frac{R}{L} I_2 + \frac{1}{LC} \int I_2 dt = \frac{RI_0}{L} \delta(t)$$

$$\text{let } I_2 = \frac{dq_2}{dt}$$

$$\frac{d^2 q_2}{dt^2} + \frac{R}{L} \frac{dq_2}{dt} + \frac{1}{LC} q_2 = \frac{RI_0}{L} \delta(t) \quad (*)$$

$$\text{Natural: } s^2 + \frac{R}{L}s + \frac{1}{LC} = s^2 + s + 1 = 0 \Rightarrow s = -\frac{1}{2} \pm \sqrt{\frac{1}{4} - 1} = -\frac{1}{2} \pm j \frac{\sqrt{3}}{2}$$

$$\text{IC: } \left(\int \neq dt \right) \frac{dq_2}{dt} \Big|_{t=0^+} + \frac{R}{L} q_2(0^+) = \frac{RI_0}{L} \Rightarrow q_2(0^+) = 0$$

$$\frac{dq_2}{dt} \Big|_{t=0^+} = \frac{RI_0}{L}$$

$$v_c = \frac{q_2}{C} = A e^{-t/2} \cos\left(\frac{\sqrt{3}}{2}t + \phi\right)$$


$$v_c(0^+) = q_2(0^+) = 0 = A \cos \phi \Rightarrow \phi = -\pi/2$$

$$\frac{dv_c}{dt} \Big|_{t=0^+} = \frac{dq_2}{dt} \Big|_{t=0^+} = \frac{RI_0}{L} = I_0 = -\frac{A}{2} \cos \phi - \frac{A\sqrt{3}}{2} \sin \phi \Rightarrow A = \frac{2I_0}{\sqrt{3}}$$

$$v_c(t) = \frac{2I_0}{\sqrt{3}} e^{-t/2} \cos\left(\frac{\sqrt{3}}{2}t - \pi/2\right) u(t) \text{ V}$$

EXAM 3, part 2

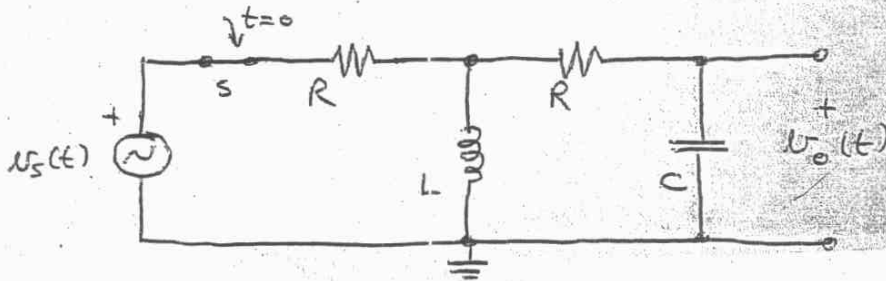2. Find the complete response of the circuit shown below. A switch closes at time $t = 0$ to connect the source $v_s(t) = V_0\sqrt{2} \cos(t)$. Let $R = L = C = 1$ (with appropriate units). $i_L(0^-) = v_C(0^-) = 0$



$$Z(s) = \frac{\left(\frac{SLR}{SL+R} + R \right) / sC}{\frac{SLR}{SL+R} + R + \frac{1}{sC}} = \frac{2s+1}{2s^2+2s+1}$$

$$s^2 + s + \frac{1}{2} = 0 \Rightarrow s = -\frac{1}{2} \pm \sqrt{\frac{1}{4} - \frac{1}{2}} = -\frac{1}{2} \pm j\frac{1}{2}$$

$$v_{cn} = A e^{-t/2} \cos\left(\frac{t}{2} + \phi\right)$$

Forced: $v_C = \frac{Z_C}{R + Z_C} v_L = \frac{Z_C}{R + Z_C} \frac{Z_{RLC}}{R + Z_{RLC}} v_s$ $Z_{RLC} = \frac{s(R + \frac{1}{sC})}{sL + R + \frac{1}{sC}} = \frac{s(s+1)}{s^2+s+1}$

$$= \frac{1/sC}{R + 1/sC} \frac{s(s+1)}{1 + \frac{s(s+1)}{s^2+s+1}} v_s = \frac{1}{s+1} \frac{s(s+1)}{s^2+s+1 + s(s+1)} = \frac{s}{2s^2+2s+1} v_s$$

Let $s \rightarrow j\omega$ ($\omega = 1$) $\frac{v_C}{v_s} = \frac{j}{1-2+j^2} = \frac{1 \angle 90^\circ}{\sqrt{5} \angle 116.56^\circ} = 0.447 \angle -26.56^\circ$

$$v_{cf} = 0.447\sqrt{2} \cos(t - 26.56^\circ)$$

$$v_C = v_{cn} + v_{cf} = A e^{-t/2} \cos\left(\frac{t}{2} + \phi\right) + 0.447\sqrt{2} \cos(t - 26.56^\circ)$$

$$v_C(0^+) = 0 \Rightarrow A \cos \phi + 0.447\sqrt{2} \cos(-26.56^\circ) = 0$$

$$\frac{dv_C}{dt} \Big|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{V_0\sqrt{2}}{2RC} = \frac{V_0\sqrt{2}}{2} = -\frac{1}{2}A \sin \phi - \frac{1}{2} \cdot 0.447\sqrt{2} \sin(-26.56^\circ)$$

2 eq, 2 unk. \Rightarrow solve.