

1. In the circuit below, $R_1 = R_2 = L = C = 1$ (with appropriate MKS units). The capacitor has an initial voltage of $V_0 = 1$ V, and the inductor has an initial current of $I_0 = 1$ A. (25 points)

a. Fill in the table below for the initial voltages and currents at $t = 0^+$.


$t = 0^+$	v	i
R_1	1 V	1 A
R_2	1 V	1 A
L	-2 V	1 A
C	1 V	0 A

What are the initial values of $\frac{dv_C}{dt}$ and $\frac{di_L}{dt}$ at $t = 0^+$?

$$\left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = 0 \text{ V/s}$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L} = -2 \text{ A/s}$$

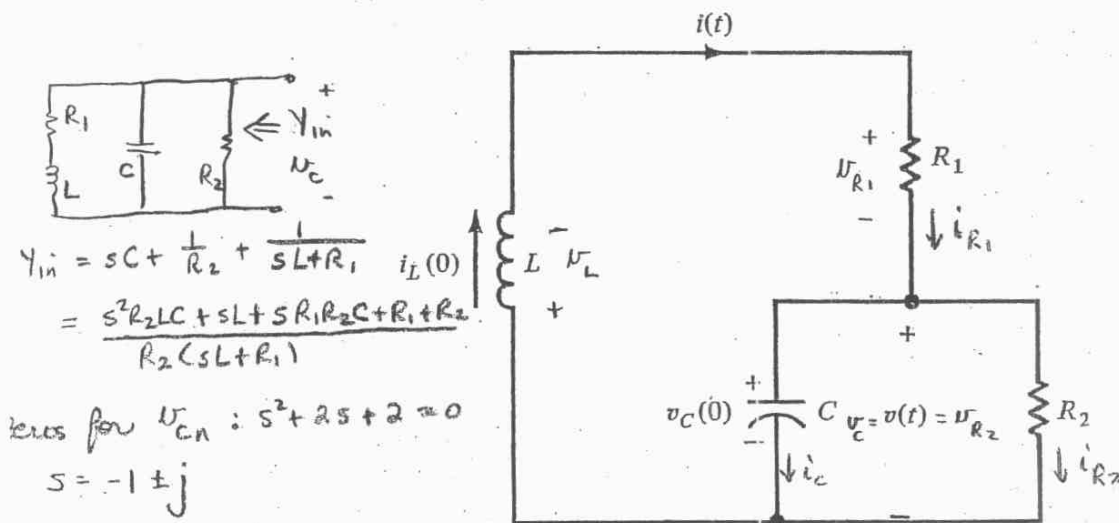b. Find the voltage $v_C(t)$ across the capacitor (natural response) for $t \geq 0$.



$$Y_{in} = sC + \frac{1}{R_2} + \frac{1}{sL + R_1}$$

$$= \frac{s^2 R_2 LC + sL + sR_1 R_2 C + R_1 + R_2}{R_2 (sL + R_1)}$$

zeros for v_{Cn} : $s^2 + 2s + 2 = 0$

$$s = -1 \pm j$$


$$v_{Cn} = A e^{-t} \cos(t + \phi) \text{ V } t \geq 0$$

$$v_{Cn}(0) = 1 = A \cos \phi \quad \text{using } \Rightarrow A = \frac{1}{\cos \phi} = \frac{1}{\cos(-\pi/4)} = \sqrt{2}$$

$$\left. \frac{dv_{Cn}}{dt} \right|_{t=0} = 0 = -A \cos \phi - A \sin \phi \Rightarrow \tan \phi = -1 \text{ or } \phi = -\pi/4$$

$$v_{Cn}(t) = \sqrt{2} e^{-t} \cos(t - \pi/4) u(t) \text{ V}$$

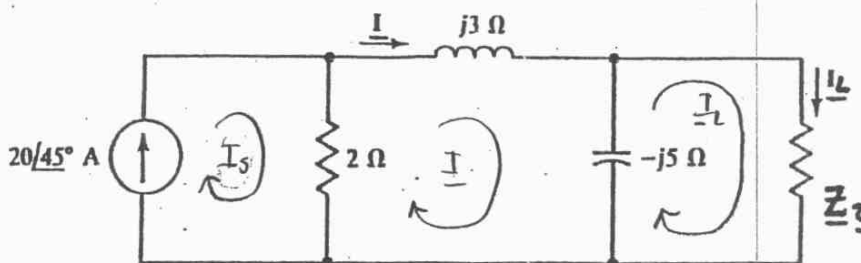2. In the circuit below, find Z_L and I if $I_L = 6.85 \angle -7^\circ$. Is Z a pure resistance, pure inductance, pure capacitance, or combination (specify R and L or R and C)? If Z is an L or a C, please indicate what additional information you would need to know to specify its value. If Z is an R, please provide its value. (25 points)



$$I_s = 20 \angle 45^\circ \quad I_L = 6.85 \angle -7^\circ$$

Middle loop: $\sum v = 0 = j3I - j5(I - I_L) + 2(I - I_s)$

$$(j3 - j5 + 2)I + j5(6.85 \angle -7^\circ) - 40 \angle 45^\circ = 0$$


$$I = \frac{-4.174 - j3.4 + 28.28 + j28.28}{2 - j2} = 8.76 \angle 31.65^\circ$$

By current divider, $\frac{I_L}{I} = \frac{-j5}{Z - j5} = \frac{6.85 \angle -7^\circ}{8.76 \angle 31.65^\circ} = 0.782 \angle -38.65^\circ$


$$Z - j5 = \frac{5 \angle -90^\circ}{0.782 \angle -38.65^\circ} = 6.39 \angle -51.4^\circ$$

$$Z = j5 + 4 - j5 = 4 \Omega$$

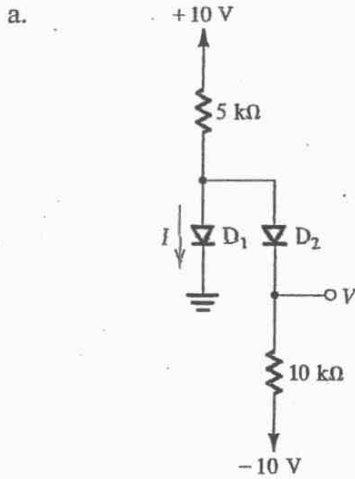
3. Assume all diodes are ideal. In the circuits below, find I and V as indicated. (25 points)



b.

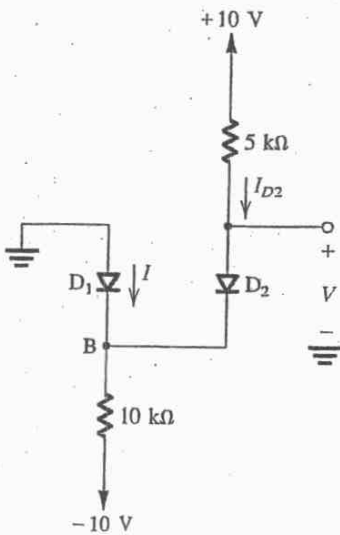

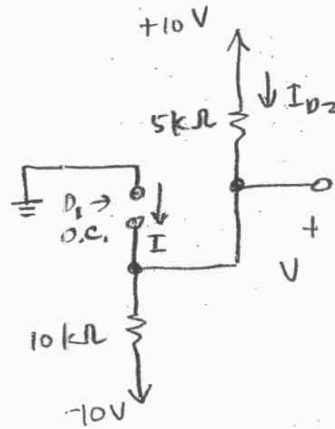Assume D_1 off; D_2 on. Find i, v & check assumptions.



$$I = I_{D1}$$

$$0 - V = V_{D1}$$

$$I_{D2} = \frac{10 - (-10)}{(10 + 5)k} = \frac{4}{3} \text{ mA} ; V_{D2} = 0 \text{ since s.c.}$$

$$V = -10 + 10k(I_{D2}) = -10 + 13.3 = 3.3 \text{ V}$$


$$V_{D1} = 0 - V = 0 - 3.3 = -3.3 \text{ V} \left. \begin{array}{l} \text{consistent w/} \\ D_1 \text{ off} \end{array} \right\}$$

$$I_{D1} = I = 0 \text{ since o.c.}$$

$$I_{D2} = \frac{4}{3} \text{ mA} > 0, V_{D2} = 0 \left. \begin{array}{l} \text{consistent w/} \\ D_2 \text{ on} \end{array} \right\}$$

4. A circuit has one zero at $s = 0.5$, and two poles at $s = 0$ and $s = -1$. (Impedance) (25 points)

a. Plot the pole-zero diagram.

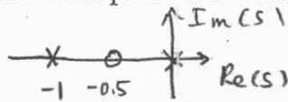

b. Write the forms of the natural current and natural voltage that might occur in this circuit in terms of unknown constant coefficients. $i_n = A e^{-0.5t}$ $v_n = B_1 + B_2 e^{-t}$

c. If you knew that the circuit contained two identical capacitors and one resistor, choose the configuration from those shown below that would have the above impedance function. Specify the values of R and C. What is the physical meaning of the pole at the origin (i.e. which element is responsible for it, and what IC could cause it to be part of the solution)?

$Z(s) = \frac{SRC + 2}{sC}$
single pole X

NO

NO

$Z(s) = \frac{R}{2SRC + 1}$
X no zeros

$Z(s) = \frac{\frac{1}{sC}(R + \frac{1}{sC})}{\frac{2}{sC} + R}$
 $= \frac{SRC + 1}{sC(SRC + 2)}$
Choose $RC = 2$
so $R = 2k\Omega, C = 1mF$

YES

pole @ origin: left C w/ $v_C(0)$ would discharge only half its voltage & then remain @ $v_C(0)/2$

pole @ origin: left C can't discharge $v_C(0)$.

YES

$Z(s) = \frac{R/sC + R + 1/sC}{sC(SRC + 1)}$
Choose $RC = 1$
so $R = 1k\Omega, C = 1mF$

NO

$Z(s) = R + \frac{1}{2sC}$
 $= \frac{SRC + \frac{1}{2}}{sC}$ X single pole

NO

$Z(s) = \frac{R + \frac{1}{sC}}{R + \frac{1}{sC/2}}$
 $= \frac{1}{2} \frac{SRC}{SRC + 2}$ X single pole