

EXAM 1

Each problem is worth 25 points.

1. Find V_0 in the circuit shown below.


$$\sum W = 0 = -6kI_1 - 2k(I_1 + \frac{V_x}{2k}) - V_x \Rightarrow -8kI_1 - 2V_x = 0$$

Loop 1 where $V_x = 6k(I_1 + 2m) = 6kI_1 + 12$; plug into \Rightarrow

$$-8kI_1 - 2(6kI_1 + 12) = 0$$

$$\text{so } I_1 = -\frac{6}{5} \text{ mA}$$







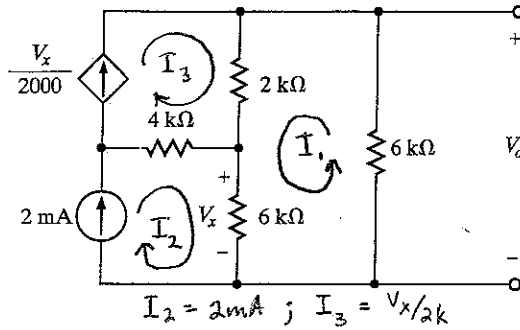
$$\boxed{V_0 = 6kI_1 = -\frac{36}{5} \text{ V}}$$



2. Consider the 8 kΩ resistor in the circuit below to be the load resistor.

a. Find the Thevenin equivalent of the remainder of the circuit (after removing the 8 kΩ resistor). You may use any combination of methods you like to find the Thevenin equivalent.

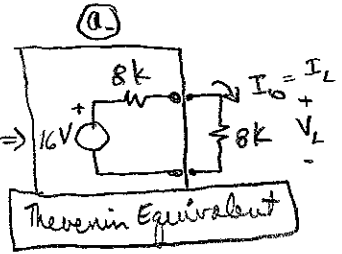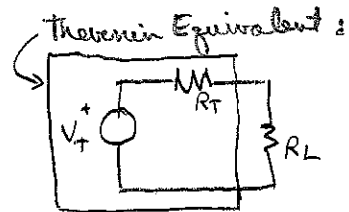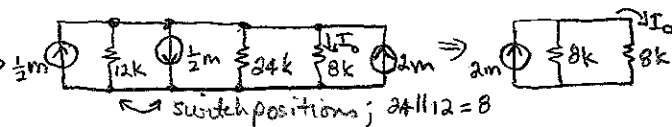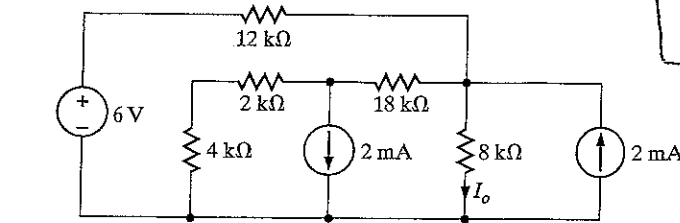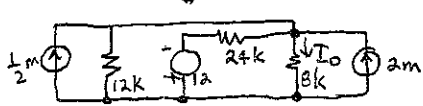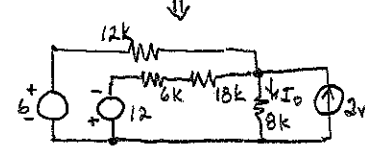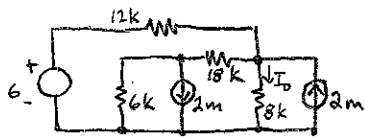b. Find the current I_0 and the power dissipated by the resistor.




b. $I_0 = \frac{V_T}{R_T + R_L} = \frac{16}{16k} = 1 \text{ mA} = I_0$

$P = V_{I_0} = R I_0^2 = 8k(1m)^2 = 8 \text{ mW} = P$

EXAM 1

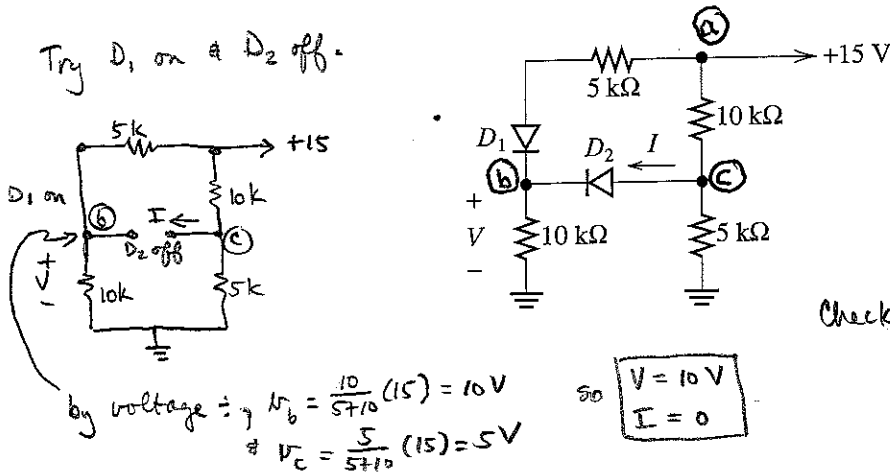3. Find I and V in the circuit shown below.



Check: D_1 has $v > 0$ (\downarrow) ✓
 D_2 has $v < 0$ ($5 - 10 = -5 < 0$) ✓

4. Set up a sufficient number of equations to find i_o in the circuit shown below, but **do not solve** them. The load can be considered to be a resistor connected to ground, and in this circuit, it does not matter what value that resistor has


Note:

$$V_b = V_c$$

$$V_f = V_g$$

$$V_a - V_b = V_{in}$$

$$I_o = \frac{V_e - V_f}{R_f}$$

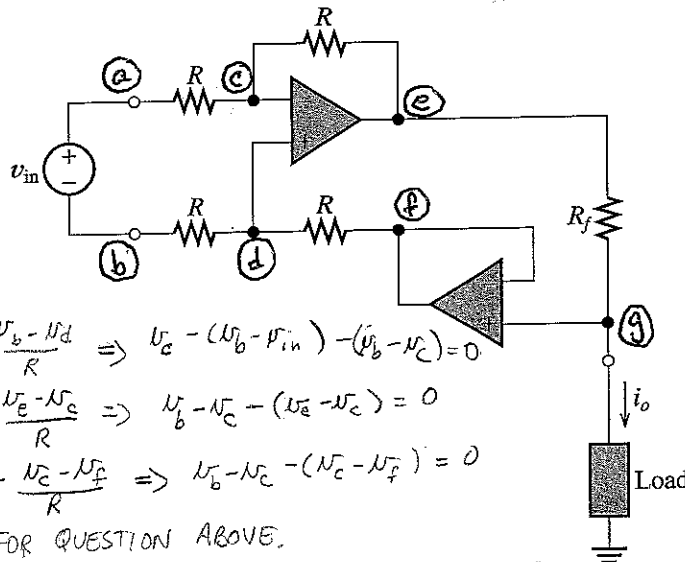

$$\sum I = 0 = \frac{V_c - V_a}{R} - \frac{V_b - V_d}{R} \Rightarrow V_c - (V_b - V_{in}) - (V_b - V_c) = 0$$

$$\sum I = 0 = \frac{V_a - V_c}{R} + \frac{V_e - V_c}{R} \Rightarrow V_b - V_c - (V_e - V_c) = 0$$

$$\sum I = 0 = \frac{V_b - V_c}{R} - \frac{V_c - V_f}{R} \Rightarrow V_b - V_c - (V_c - V_f) = 0$$

⇒ STOP HERE FOR QUESTION ABOVE.

for actual solution,

$$\begin{aligned} V_b - 2V_c + V_e &= -V_{in} \\ V_b - 2V_c + V_f &= 0 \\ -2V_b + 2V_c &= V_{in} \\ V_e - V_f &= R_f I_o \end{aligned}$$

$R_f I_o \Rightarrow V_f = V_e - R_f I_o$
 $V_b - 2V_c + V_e = -R_f I_o$

So $V_b - 2V_c + V_e = -V_{in}$
 $V_b - 2V_c + V_e = -R_f I_o$
 $-2V_b + 2V_c = V_{in}$

⇒ $I_o = -\frac{V_{in}}{R_f}$, so this circuit operates as a current source supplying i_o to the load.