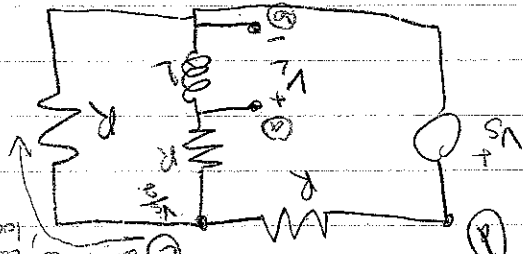


# Exam 2 Review



- Ch. 5 Op Amps
- Ch. 6 L, C (not G, S)
- Ch. 7 first order, homogeneous & particular w/ DC sources
- \* Impedance  $Z(s)$  to find homogeneous response

Remove  $V_S = 0$  S.C.  
 Remove  $I_S = 0$  O.C.

Sequential Switching + Impedance



$V_S \rightarrow$  S.C.

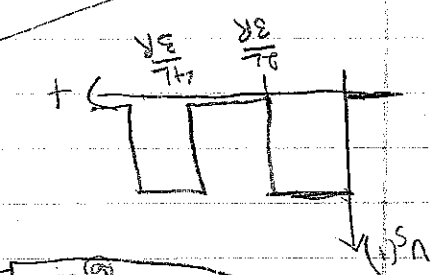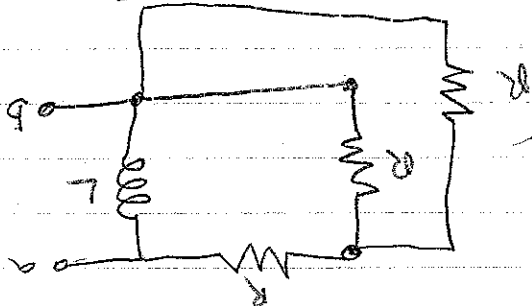

$sL(3R) \leftarrow$  zero used for current  
 $2sL + 3R \leftarrow$  poles used for voltage

$$Z(s) = \frac{sL \left( \frac{2}{3R} \right)}{2sL + 3R} = \frac{sL \frac{2}{3R}}{2sL + 3R}$$

$$s = -\frac{3R}{2L}$$

$$V_L = V_{LH} + V_{LP} = Ae^{-\frac{3R}{2L}t} + 0$$

$$V_L(0^+) = A = \frac{2}{3R} \frac{2L}{3R} + \frac{2}{3R} \frac{2L}{3R}$$

$$0 < t < \frac{2L}{3R}$$

Ch. 5 Op Amps

Ch. 6 L, C (not 6.4, 6.5)

Ch. 7 First Order, Homogeneous & particular w/ dc sources

Sequential switching, impedance  $Z(s)$  to find homogeneous response



Complex numbers

Remove  $V_s$   $V_s=0 \Rightarrow$  short circuit


$I_s$   $I_s=0 \Rightarrow$  open circuit

# Sequential switching + impedance


①

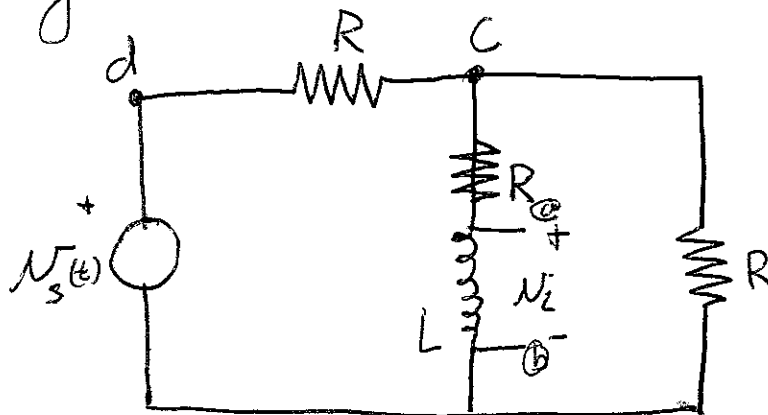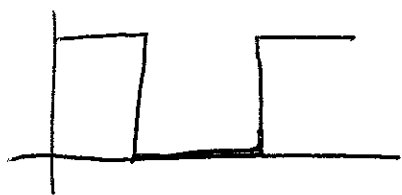

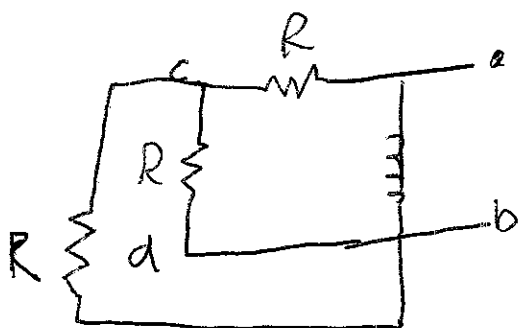Find  $v_L(t)$  if all  $i, v = 0$  (no energy storage) @  $t=0^-$



$\Rightarrow$

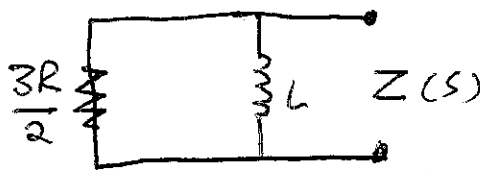

$$Z(s) = \frac{sL \left(\frac{3R}{2}\right)}{sL + \frac{3R}{2}}$$

$$v_L = v_{Lh} + v_{Lp}$$

$$v_{Lh} = A e^{\left(\frac{-3R}{2L}\right)t} + 0$$


For A,  $i = \frac{v_s}{2R}$  (all goes around outside loop; no current  $\rightarrow \frac{1}{2}$ )

$$v_L(0^+) = A = \frac{v_s}{2}$$

$$v_L(t) = \frac{v_s}{2} e^{\left(\frac{-3R}{2L}\right)t} \quad V \quad \left| \quad 0 \leq t \leq \frac{2L}{3R}$$

$$v_L(t) = B e^{\left(\frac{-3R}{2L}\right)\left(t + \frac{2L}{3R}\right)} \quad \frac{2L}{3R} \leq t \leq \frac{4L}{3R}$$

Sketch

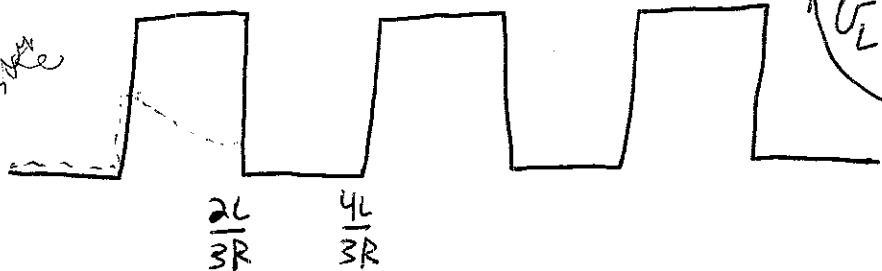

$$v_L(0^+) = B = ?$$

$$\left(-\frac{v_s}{2} e^{-1}\right)$$


$$v_L = L \frac{di}{dt} @ \frac{v_s}{2}$$

$$v_L = \left(\frac{v_s}{2} e^{-1}\right) e^{\left(\frac{-3R}{2L}\right)t}$$

$v_{Lh}$   
 $v_{Lp}$

# Op Amps

5.38  
pg 212

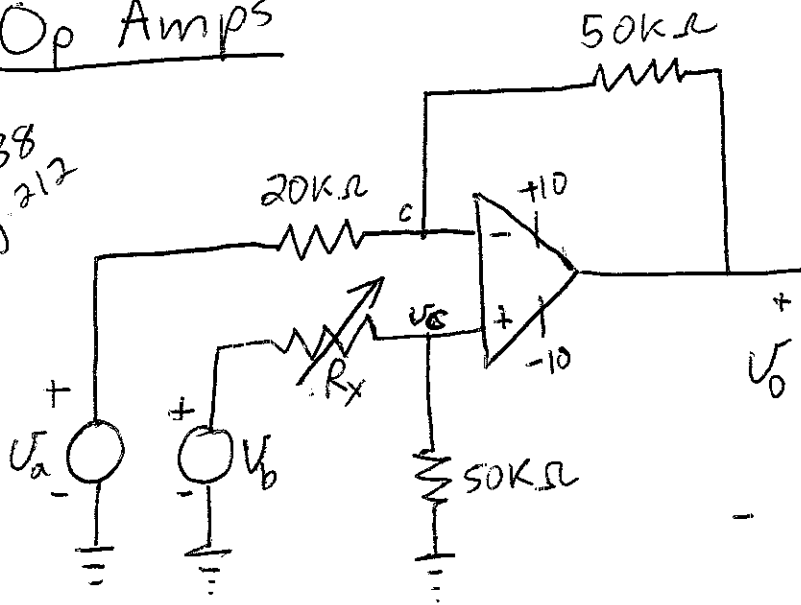

Find  $R_x$  for  $CMRR \geq 1000$  ②

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

$$V_{dm} = V_b - V_a$$

$$V_{cm} = \frac{1}{2} (V_a + V_b)$$

$$V_o = A_{cm} V_{cm} + A_{dm} V_{dm}$$

$$\sum i_c = \left[ \frac{V_a - V_c}{20k} + \frac{V_o - V_c}{50k} = 0 \right] 100 = 5 \left[ V_a - \frac{50k}{50k + R_x} V_b \right] + 2 \left[ V_o - \frac{50k}{50k + R_x} V_b \right] = 0$$

$$V_o = \frac{-5(50k + R_x)V_a + 5(50k)V_b + 2(50k)V_b}{2(50k + R_x)}$$


need  $V_o = A_{cm} V_{cm} + A_{dm} V_{dm}$

use  $\left\{ \begin{array}{l} V_a = \text{fn of } V_{dm} + V_{cm} \\ V_b = \text{fn of } V_{dm} + V_{cm} \end{array} \right\}$  plug into

to obtain
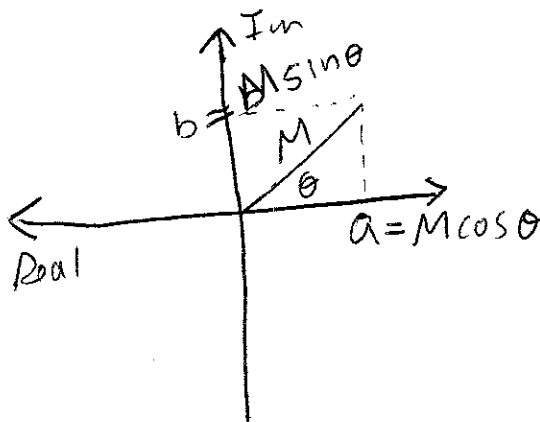
# Complex Numbers

Rect  $a + jb$  Polar  $Me^{j\theta} = M \angle \theta$



Add / Subtract (rect)  
 Multiply / Divide (Polar)  
 Powers / Roots (Polar)

Prefer

Complex Conjugate

$$j \rightarrow -j$$

$$C^* = Me^{-j\theta} = a - jb \quad \left| \quad M = \sqrt{a^2 + b^2} \right.$$

$$C = Me^{j\theta} = a + jb \quad \left| \quad \theta = \tan^{-1}\left(\frac{b}{a}\right) \right.$$

$$(C)(C^*) = \underline{\underline{M^2}} \neq C^2$$

Roots

$$\sqrt{j} \begin{cases} a+jb \\ a=0, b=1 \end{cases} \quad \begin{array}{c} \text{Im} \\ \uparrow \\ j \end{array}$$

$$= e^{-j\pi/2} \rightarrow \sqrt{j} = \sqrt{e^{j\pi/2}} = e^{j\pi/4}, e^{j\pi/4}$$

$$\sqrt[N]{Me^{j\theta}} = M^{1/N} e^{-j\theta/N}, M^{1/N} e^{j(\theta+2\pi)/N}$$

$$\sqrt[3]{1} = \sqrt[3]{1 \angle 0} = \sqrt[3]{1 e^{j0}} = 1 e^{j(0)/3}$$

