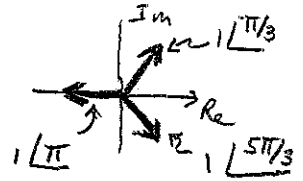



1. a. $\sqrt[3]{\frac{(1+j)^2}{(1-j)^2}} = \sqrt[3]{\frac{2 \angle \pi/3}{2 \angle -\pi/2}} = \sqrt[3]{1 \angle \pi} = \sqrt[3]{1 \angle \frac{\pi}{3}} = \sqrt[3]{1 \angle \frac{\pi+2\pi}{3}} = \sqrt[3]{1 \angle \pi} = 1 \angle \frac{\pi}{3}$



b. Find C if $C^2 - (3-j2)C + (1-j3) = 0$
 $C = \frac{3-j2}{2} \pm \sqrt{\left(\frac{3-j2}{2}\right)^2 - (1-j3)}$
 $C = \frac{3-j2}{2} \pm \sqrt{\frac{3-j6}{2}}$

let $C = a+jb \Rightarrow (a+jb)^2 - (3-j2)(a+jb) + (1-j3) = 0$
 $a^2 + 2jab - b^2 - 3a + j2a - j3b - 2b + 1 - j3 = 0$
 $\Rightarrow a^2 - b^2 - 3a - 2b + 1 = 0 ; 2ab - 3b + 2a - 3 = 0$

2. Find $i(t)$ if S closes @ $t=0$.

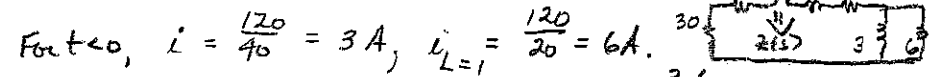

For $t < 0$, $i = \frac{120}{40} = 3A$, $i_{L=1} = \frac{120}{20} = 6A$.
 For homogeneous soln., $Z(s) = 30 + 10 + s + 20 + \frac{3 \cdot 6}{s+6} s = 3s + 60 = 0 \Rightarrow s = -20$

$i_{L=1}(0^-) = i_{L=1}(0^+) = 6A = -i(0^+)$
 $i = i_h + i_p = Ae^{-20t}$; $i(0^+) = -6 = A$
 $\therefore i(t) = \begin{cases} 3A & t < 0 \\ -6e^{-20t} A & t > 0 \end{cases}$

3. At $t=0$, $S: 1 \rightarrow 2$. Find $v_C(t)$.
 $t=0^-: v_C = \frac{R}{R+R}(2V_s) = V_s$ by voltage div.



$t > 0: v_C = v_{Ch} + v_{Cp}$ $v_{Cp} = \frac{R}{R+2R}(-V_s) = -\frac{V_s}{3}$ $v_{Ch}: Y(s) = \frac{1}{R} + \frac{1}{2R} + sC = \frac{2sRC + 1 + 2}{2R}$


for v_{Ch} , use poles of $Z(s) = \text{zeros of } Y(s) \Rightarrow 2sRC + 3 = 0$ or $s = -\frac{3}{2RC}$

$v_C(t) = Ae^{-3t/2RC} + (-\frac{V_s}{3})$; $v_C(0) = V_s = A - \frac{V_s}{3} \Rightarrow A = \frac{4V_s}{3}$
 $\therefore v_C(t) = \frac{V_s}{3} (-4e^{-3t/2RC} + 1) V, t > 0$

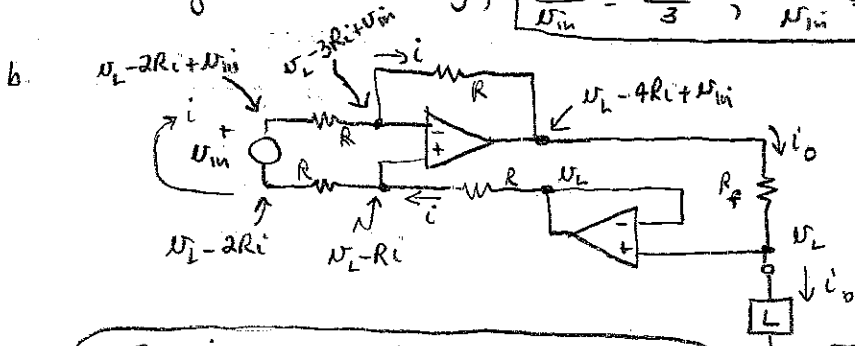4. a. By voltage div., $v_{o1} = \frac{R}{2R} v_{o2} = \frac{v_{o2}}{2}$ (1)

@ inverting input to left op amp, $\sum i = \frac{v_{in} - 0}{R} + \frac{v_{o1} - 0}{4R} + \frac{v_{o2} - 0}{4R} = 0$ (2)

Solving simultaneously, $\frac{v_{o1}}{v_{in}} = -\frac{4}{3}, \frac{v_{o2}}{v_{in}} = -\frac{8}{3}$



Best for left op amp, $v_L - Ri = v_L - 3Ri + v_{in}$

so $i = \frac{v_{in}}{2R}$

$i_o = \frac{(v_L - 4Ri + v_{in}) - v_L}{R_f}$

$= \frac{-4R(\frac{v_{in}}{2R}) + v_{in}}{R_f} = \frac{-v_{in}}{R_f} = i_o'$

\therefore This is a current source, w/ i_o independent of the load.