

Exam 3 Review

- Ch. 8 2nd order RLC Natural, Particular (dc), Complete
- Ch. 9 Sinusoidal Steady State (Particular)
- + Complete (homog + particular)


Not → 9.10, 9.11

Ch 10 RMS

Ch. 14 All

+ Impulse Response

Impulse

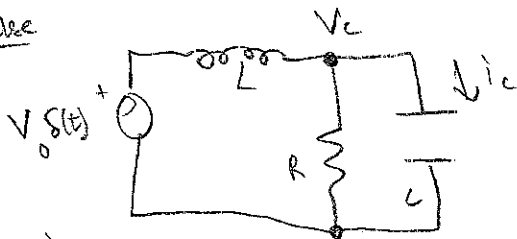


$$u(t) = \int \delta(t) dt$$



$$\delta(t) = \frac{d[u(t)]}{dt}$$



Find i_c

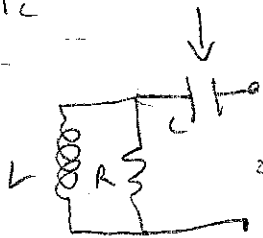

$$Z(s) = \frac{1}{sC} + \frac{sL+R}{sL+R}$$

$$= \frac{s^2 RLC + sL + R}{sC(sL+R)}$$

Use zeros, $R=L=C=1$

$$s^2 + s + 1 = 0$$

$$s = -\frac{1}{2} \pm j \frac{\sqrt{3}}{2}$$

$$i_c = A e^{-\frac{t}{2}} \cos\left(\frac{\sqrt{3}}{2} t + \phi\right)$$

$$s = -\frac{b}{2} \pm \sqrt{\left(\frac{b}{2}\right)^2 - c} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha \pm \sqrt{\omega_0^2 - \alpha^2} \leftarrow \text{resonant}$$


$$= -\alpha \pm j \omega_d \leftarrow \text{driving}$$

$$\sum i = 0 = i_L - i_R - i_C$$

$$0 = \frac{1}{L} \int [V_0 \delta(t) dt - V_C] - \frac{V_C}{R} - C \frac{dV_C}{dt}$$

$$\left. \frac{dV_C}{dt} \right|_{t=0^+} + \frac{1}{RC} V_C \Big|_{t=0^+} + \frac{1}{LC} \int_{-\infty}^{0^+} V_C dt = \frac{1}{LC} \int_{-\infty}^{0^+} V_0 \delta(t) dt = \frac{V_0}{LC} u(t) \left[\text{but @ } t=0^+, u(t)=1 \right]$$

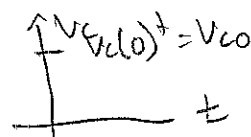want $V_C(0^+) = \begin{cases} V_{C0} \\ 0 \end{cases}$



↑ possible Not possible b/c $\frac{dV_C}{dt}$ would be ∞

$\therefore V_C(0^+) \text{ must } = 0 \quad \therefore \left. \frac{dV_C}{dt} \right|_{t=0^+} = \frac{V_0}{LC}$

$$V_c = B e^{-t/2} \cos\left(\frac{\sqrt{3}}{2}t + \Theta\right) \quad (\text{b/c } i_c \text{ of same form was found})$$

$$V_c(0) = B \cos \Theta = 0 \Rightarrow \Theta = \pm \frac{\pi}{2}$$

$$\left. \frac{dV_c}{dt} \right|_{t=0} = -\frac{B}{2} \cos \Theta - \frac{\sqrt{3}}{2} B \sin \Theta = V_0 \quad (L=C=1)$$

$$\text{b/c } A \cos \omega t + B \sin \omega t = C \cos(\omega t + \phi) \\ = C \cos \phi \cos \omega t - C \sin \phi \sin \omega t$$

$$\Theta = -\frac{\pi}{2}$$


$$\left. \frac{dV_c}{dt} \right|_{t=0} = -\frac{\sqrt{3}}{2} B \sin \Theta = V_0 \quad B = \frac{2V_0}{\sqrt{3}}$$

$$V_c(t) = \frac{2V_0}{\sqrt{3}} e^{-t/2} \cos\left(\frac{\sqrt{3}}{2}t - \frac{\pi}{2}\right) u(t) \quad t > 0$$

$$i_c = C \frac{dV_c}{dt} = \frac{2V_0}{\sqrt{3}} e^{-t/2} \cos\left(\frac{\sqrt{3}}{2}t - \frac{\pi}{2}\right) \delta(t) \Bigg\} = 0$$

$$-\frac{\sqrt{3}}{2} \frac{2V_0}{\sqrt{3}} e^{-t/2} \sin\left(\frac{\sqrt{3}}{2}t - \frac{\pi}{2}\right) u(t) - \frac{1}{2} \frac{2V_0}{\sqrt{3}} e^{-t/2} \cos\left(\frac{\sqrt{3}}{2}t - \frac{\pi}{2}\right) u(t)$$


RMS

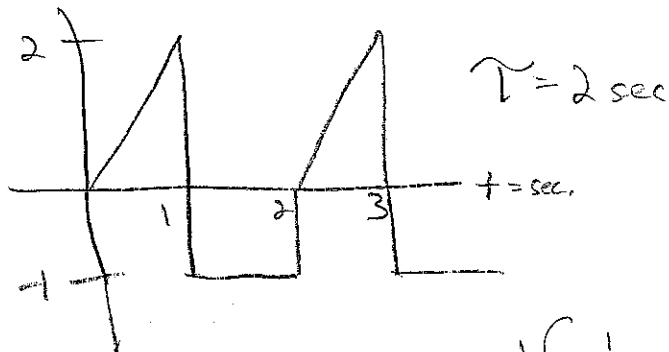

$$V_{RMS}^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{2} \left[\int_0^1 (2t)^2 dt + \int_1^2 (-1)^2 dt \right] = \frac{1}{2} \left[\left(\frac{4}{3}t^3\right)_0^1 + [t]_1^2 \right] \\ = \frac{1}{2} \left(\frac{2}{3} \right) = \frac{2}{6}$$

$$P_{AVG} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{v^2}{R} dt = \frac{V_{RMS}^2}{R}$$

Sinusoidal Steady State

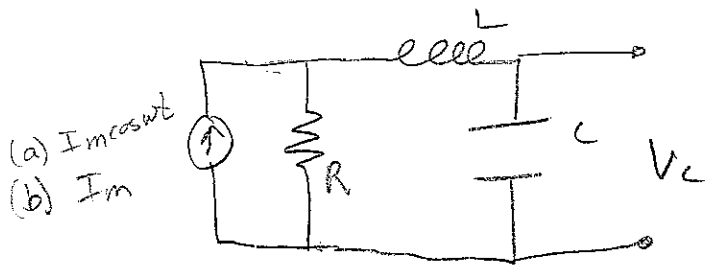

$$Z(s) = \frac{1}{sC} \parallel (R + sL)$$

$$= \frac{\frac{1}{sC}(R + sL)}{sL + R + \frac{1}{sC}}$$

$$= \frac{sL + R}{s^2 LC + sRC + 1}$$

$$s^2 LC + sRC + 1 = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$


$$s^2 + s + 1 = 0 \quad s = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$$

$$= -\alpha \pm j\omega_d$$


$$V_c = V_{ch} + V_{cp}$$

$$V_{ch} = A e^{-\alpha t} \cos(\omega_d t + \phi)$$

V_{cp} :

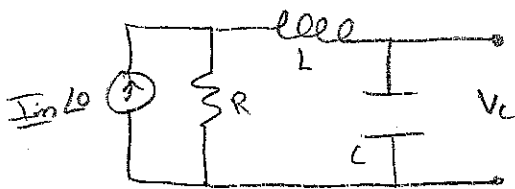

Source transformation + V_c

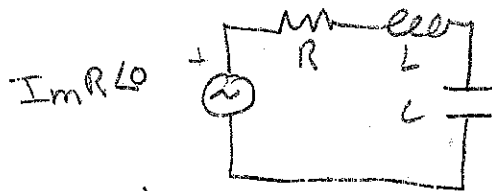

$$V_c = \frac{Z_c}{R + Z_L + Z_c} I_m R L_0 = \left(\frac{-j(\frac{1}{\omega C})}{R + j\omega L + \frac{1}{j\omega C}} \right) I_m R L_0$$

$$R=L=C=\omega=1$$

$$= \frac{1}{\omega C} \angle -\frac{\pi}{2}$$

$$\frac{1}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \angle \tan^{-1} \dots$$

$$= \frac{-j}{1 + j - j} I_m L_0 = \frac{1 \angle -\pi/2}{1} I_m L_0 = I_m \angle -\frac{\pi}{2}$$

$$V_c = I_m \angle -\frac{\pi}{2}$$

$$V_{cp}(t) = I_m \cos(t - \frac{\pi}{2})$$

$$\therefore V_c(t) = A e^{-\alpha t} \cos(\omega_d t + \phi) + I_m \cos(t - \frac{\pi}{2})$$

$$V_c(0^+) = 0 = A \cos \phi + I_m \cos(-\frac{\pi}{2}) \Rightarrow \phi = +\frac{\pi}{2}$$

[b/c $V_c(0) = V_c(0^+) = 0$]
[b/c $i_c(t) = i_L(t)$ and $i_c(0) = 0$]

$$\frac{dV_c}{dt} \Big|_{t=0^+} = \frac{i_c(0^+)}{C} = 0 = -\alpha A \cos \phi - \omega_d A \sin \phi - I_m \sin(-\frac{\pi}{2})$$

$$\therefore V_c(t) = \left\{ \frac{I_m}{\omega_d} e^{-\frac{t}{2}} \cos\left(\frac{\sqrt{3}}{2}t - \frac{\pi}{2}\right) + I_m \cos\left(t - \frac{\pi}{2}\right) \right\} \dots (1) \quad (3)$$

b) $V_{ch} = Ae^{-\alpha t} \cos(\omega t + \phi)$

$V_{cp} = I_m R$ (b/c capacitor $\rightarrow 0 \Omega$)

$V_c = Ae^{-\alpha t} \cos(\omega t + \phi) + I_m R$


$V_c(0^+) = 0 = A \cos \phi + I_m R$

$A = \frac{-I_m R}{\cos \phi}$

$\left. \frac{dV_c}{dt} \right|_{t=0^+} = \frac{c}{l_c(0^+)} = 0 = -\alpha A \cos \phi - \omega A \sin \phi = 0$

then solve

Find Thev. equivalent @ a,b

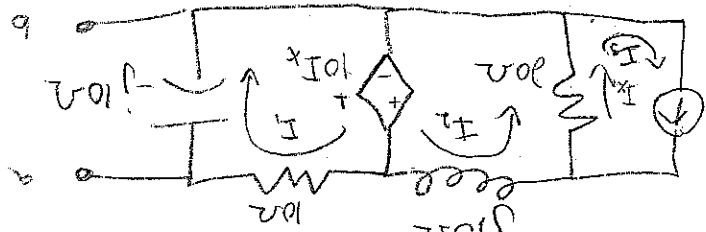

Need V_{oc} , I_{sc}

$R_T = \frac{V_{oc}}{I_{sc}}$

#3 $2V = 10I_x - (j10\Omega)I_2 - (10\Omega)(I_2 + I_3) = 0$

#1 $3V = 10I_x - 10I_1 + (j10)I_1 = 0$

#4 $I_x = I_2 + I_3$

#2 $10(I_1 + (I_2 + I_3)) - j10I_2 - 20(I_2 + I_3) = 0$

so $-10(I_2 + 2(I_2 + I_3)) - j10I_2 = 0$

$I_2(1+j) = -2(I_2 + I_3)$


$I_2 = -I_3$

#4 $I_x = -\sqrt{2} + 2\sqrt{2} = -\sqrt{2} + (2 + j\sqrt{2}) = j\sqrt{2} = \sqrt{2} \angle \frac{\pi}{2} = I_x$

Plug into dependent source & use voltage $V_T = V_{oc} = \left(\frac{-j}{1-j}\right) (10) \sqrt{2} \angle \frac{\pi}{2} = 10 \sqrt{2} \angle \frac{\pi}{4} = 10 \sqrt{2} \angle \frac{\pi}{4}$

Note: we do not get the book's answer

Isc :

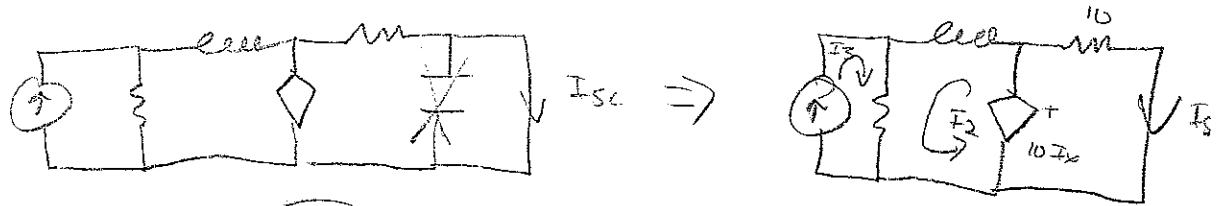

#3 $I_3 = 2 \angle \frac{\pi}{4}$ #2 $10 I_x - j10 I_2 - 10(I_x) = 0$


$I_{sc} = \frac{10 I_x}{10} = I_x$ #1 $I_x = I_2 + I_3 \Rightarrow I_2 = I_x - 2 \angle \frac{\pi}{4}$

#2 $-10 I_x - j10(I_x - 2 \angle \frac{\pi}{4}) = 0 \Rightarrow (1+j) I_x = 2 \angle \frac{\pi}{4} + \frac{\pi}{2} = 2 \angle \frac{3\pi}{4}$
↑ from j

$I_x = \frac{2 \angle \frac{3\pi}{4}}{\sqrt{2} \angle \frac{\pi}{4}} = \sqrt{2} \angle \frac{\pi}{2}$

$Z_T = \frac{V_I}{I_{sc}} = \frac{10 \angle \frac{\pi}{4}}{\sqrt{2} \angle \frac{\pi}{2}} = \frac{10}{\sqrt{2}} \angle -\frac{\pi}{4}$

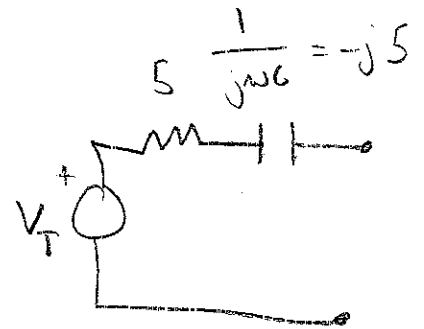$Z_T = \frac{10}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}} \right) = \boxed{5 - j5}$



Surprisingly, we do get the book's answer here, even using the V_T we found that is not in agreement with their value.