

1. Find $i_L(t)$ if S closes @ $t=0$.

Homogeneous: $R \left\{ \begin{array}{c} \text{---} \\ | \\ C \\ | \\ R \\ | \\ L \end{array} \right. z(s) = sL + R + \frac{R/Sc}{R+1/Sc} = \frac{s^2RLC + s(L+R^2C) + 2R}{sRC + 1}$
 $\Rightarrow i_L(t) = A e^{-t} \cos(t + \phi)$

For natural current, use μ ops.
 $R=L=C=1 \Rightarrow s^2 + 2s + 2 = 0$ or
 $s = -1 \pm j1$

Particular: $I_s = \frac{I_m L_0}{1}$; current $\Rightarrow I_L = \frac{Z_{RC}}{Z_{RC} + Z_{RL}} I_s$; $Z_{RC} = \frac{R/j\omega C}{R + j\omega C} = \frac{R}{1 + j\omega RC}$; $Z_{RL} = R + j\omega L$
 $\Rightarrow I_L = \frac{(2 - \omega^2 LC) + j\omega(RC + LR)}{(2 - \omega^2 LC) + j\omega(RC + LR)} I_s$
 $R=L=C=\omega=1 \Rightarrow I_L = \frac{1}{1+j2} I_m L_0 = \frac{I_m}{\sqrt{5}} \angle -\tan^{-1} 2$ or $i_L(t) = \frac{I_m}{\sqrt{5}} \cos(t - \tan^{-1}(2))$

i.c. $i_L(0^+) = i_L(0^-) = 0$ $i_L(0) = 0 = A \cos \phi + \frac{I_m}{\sqrt{5}} \cos(-\tan^{-1} 2) \Rightarrow A = \frac{-I_m \cos(-\tan^{-1}(2))}{\cos \phi}$
 $\frac{di_L}{dt}|_{0^+} = \frac{i_L(0^+)}{L} = 0$ $\frac{di_L}{dt}(0) = 0 = -A \sin \phi - \frac{I_m}{\sqrt{5}} \sin(-\tan^{-1}(2))$
 since $v_C(0^+) = v_C(0^-) = 0 = v_{RL}(0^+)$ $\Rightarrow 0 = \frac{I_m}{\sqrt{5}} \cos(-\tan^{-1}(2)) + \tan \phi \frac{I_m}{\sqrt{5}} \cos(-\tan^{-1}(2)) - \frac{I_m}{\sqrt{5}} \sin(-\tan^{-1}(2))$
 $\neq v_R(0^+) = v_R(0^-) = 0$ $\Rightarrow 0 = 1 + \tan \phi - \tan(-\tan^{-1}(2)) \Rightarrow \tan \phi = -3$ or $\phi = -\tan^{-1}(3)$


so $i_L(t) = A e^{-t} \cos(t + \phi) + \frac{I_m}{\sqrt{5}} \cos(t - \tan^{-1}(2)) u(t)$ Amps; A, ϕ given in above boxes

2. Find i_1 if $v = 10 \cos(100t + \pi/4)$ (ss. soln.) Use KVL.

$10 \angle \pi/4 - 3I_1 - j3(I_1 - I_2) = 0 \Rightarrow (3+j3)I_1 - j3I_2 = 10 \angle \pi/4$
 $-3I_1 - j0.5I_2 - j3(I_2 - I_1) = 0 \Rightarrow (-3+j3)I_1 - jI_2 = 0$
 $\Rightarrow \frac{(3+j3)I_1 - j3I_2 = 10 \angle \pi/4}{(-3+j3)I_1 - jI_2 = 0}$
 $\Rightarrow \frac{(3+j3)I_1 - j3I_2 = 10 \angle \pi/4}{(-6+j12)I_1 = 10 \angle \pi/4}$

$\therefore I_1 = \frac{10 \angle 45^\circ}{\sqrt{180} \angle 16.6^\circ} \Rightarrow i_1(t) = 0.745 \cos(100t - 71.6^\circ) A$

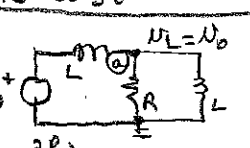3. Note: resistor on left is irrelevant.
 $v_0 = v_L$



$\sum i = 0 = \frac{1}{L} \int (v_0(t) - v_L) dt - \frac{v_L}{R} - \frac{1}{L} \int v_L dt$
 $v_L + \frac{2R}{L} \int v_L dt = \frac{R}{L} v_0 \int \delta t dt$
 i.c.: $v_L(0^+) + 0 = \frac{R}{L} v_0$ (val 5 @ $t=0^+$)

Homogeneous: set source = 0 $\Rightarrow A e^{st} (1 + \frac{2R}{sL}) = 0 \Rightarrow s = -\frac{2R}{L}$
 $\therefore v_0(t) = v_L(t) = \frac{R v_0}{L} e^{-2Rt/L} u(t) V$


4. $Z_{RLC} = \frac{R_L(sL + 1/Sc)}{R_L + sL + 1/Sc} = \frac{R_L(s^2LC + 1)}{s^2LC + sR_LC + 1} \Rightarrow H(s) = \frac{Z_{RLC}}{R + Z_{RLC}} = \frac{R_L(s^2LC + 1)}{R(s^2LC + sR_LC + 1) + R_L(s^2LC + 1)}$

a) $H(j\omega) = \frac{R_L(1 - \omega^2LC)}{(R + R_L)(1 - \omega^2LC) + j\omega R R_L C}$

b) Resonant freq $\omega_0 = \sqrt{1/LC}$

c) $H(j0) = \frac{R_L}{R + R_L}$
 $H(j\omega_0) = 0$
 $H(j\omega) \Big|_{\omega \rightarrow \infty} = \frac{R_L}{R + R_L}$

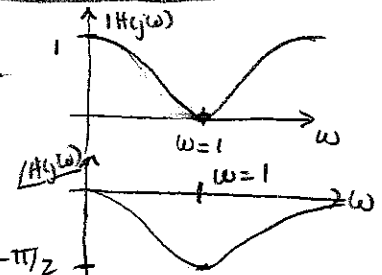d) let $R=L=C=R_L=1$
 $H(j\omega) = \frac{1 - \omega^2}{(1 - \omega^2) + j\omega}$
 $= \frac{1}{1 + j\frac{\omega}{1 - \omega^2}}$



e) denom of $H(j\omega) = 1 + j1$ for cutoff freqs.
 $\Rightarrow \frac{\omega}{1 - \omega^2} = \pm 1 \Rightarrow \omega^2 \pm \omega - 1 = 0$

$\omega_{co} = \frac{-1 \pm \sqrt{1+4}}{2} = \frac{-1 \pm \sqrt{5}}{2}$ Choose $\omega_{co} > 0$
 $\neq \omega_{co} = \frac{1 \pm \sqrt{1+4}}{2} = \frac{1 \pm \sqrt{5}}{2}$

$\Rightarrow \omega_{co} = \frac{1}{2}(-1 + \sqrt{5}), \frac{1}{2}(1 + \sqrt{5})$

f) $Q = \frac{\omega_{co2} - \omega_{co1}}{\omega_0} = \frac{\frac{1}{2}(1 + \sqrt{5}) - \frac{1}{2}(-1 + \sqrt{5})}{1} = 1 = Q$