

# Exam Review

- Ch 1  $V, I$ , Circuit Elements
- Ch 2  $V_s, I_s, KVL, KCL$ , Dependent Sources
- Ch 3 R Circuits
- Ch 4 Analysis Techniques: Node Voltage, Loop Current, Source Transformation, Thevenin & Norton, Max Power transfer
- Ch 5 Op Amp
- Ch 6 L, C (not 6.4, 6.5)
- Ch 7 1<sup>st</sup> order RL & RC Natural response  
 Step  $\rightarrow$  DC driven / complete response
- Ch 8 2<sup>nd</sup> order RLC Natural Response  
 $\rightarrow$  DC driven / complete response
- Ch 9 Sinusoidal Steady State (not 9.11)  
 COMPLETE RESPONSE for sinusoidally driven circuits  
 $\rightarrow$  (not in book, done in class)


- Ch. 15 Active (op amp) filters (not 15.2)
- Appendix B Complex Numbers
- Appendix E Bode Plots

## Not in book:


- Diodes
- Digital Logic
- Duals
- Pole-Zero diagrams
- Impulse
- Finding natural response using  $Z(s)$

## Ch. 14 Frequency Response - Transfer Functions

Active filters

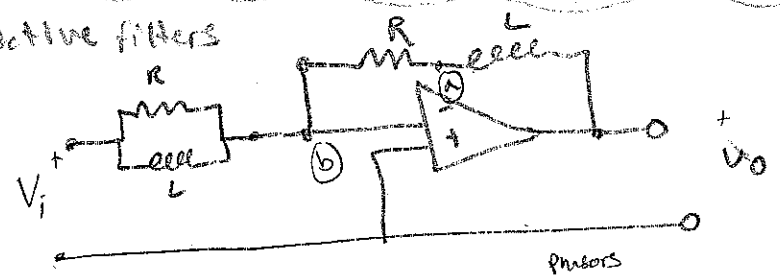

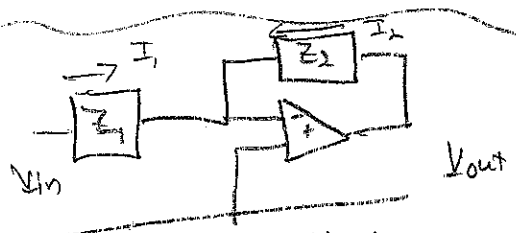$\frac{V_o}{V_i} \Rightarrow$  Frequency Response  $\leftarrow$  Phasors  $Z(j\omega)$   
 $V_o(t) \Rightarrow$  Complete Response as  $f(\text{time})$



$$\frac{V_{in}}{Z_1} + \frac{V_{out}}{Z_2} = 0$$

$$\frac{V_{out}}{V_{in}} = -\frac{Z_2}{Z_1} = \frac{-(R+j\omega L)}{j\omega LR}$$

$$= \frac{-(R+j\omega L)^2}{j\omega LR} = \frac{R^2 - (\omega L)^2 + j\omega LR}{j\omega LR}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{\sqrt{[R^2 - (\omega L)^2]^2 + (2\omega RL)^2}}{\omega RL}$$


$$\angle \frac{V_o}{V_{in}} = \pi + \tan^{-1} \left[ \frac{2\omega LR}{R^2 - (\omega L)^2} \right] - \frac{\pi}{2}$$

$-1 = 180^\circ \rightarrow$

$$\left. \begin{array}{l} \omega L \ll R \\ \text{or} \\ \frac{\omega L}{R} \ll 1 \end{array} \right\} \Rightarrow \frac{V_o}{V_{in}} = \frac{1}{j\omega L/R} = \frac{R}{\omega L} \angle -\frac{\pi}{2}$$

$$\left. \begin{array}{l} \omega L \gg R \\ \frac{\omega L}{R} \gg 1 \end{array} \right\} \Rightarrow \frac{V_o}{V_{in}} = \frac{j\omega L}{R} = \frac{\omega L}{R} \angle \frac{\pi}{2}$$

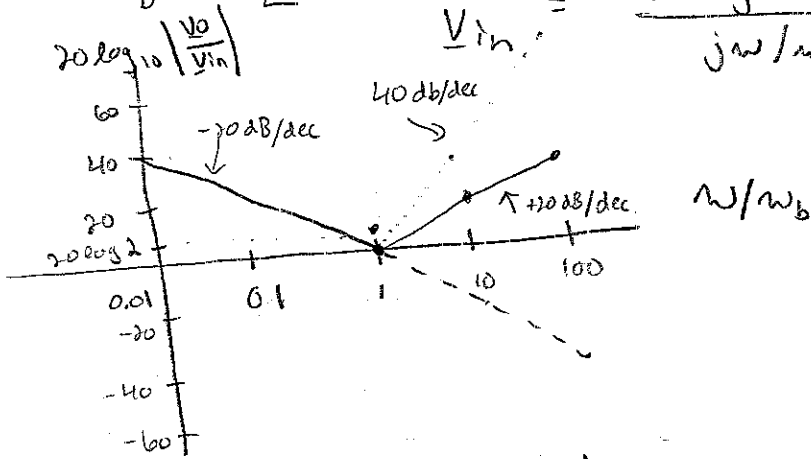
Let  $\omega_b = \frac{R}{L} \Rightarrow \frac{V_o}{V_{in}} = \frac{(1 + j\omega/\omega_b)^2}{j\omega/\omega_b}$



@  $\omega = \omega_b$ ,  $40 \log |\sqrt{2}| - 20 \log 1$   
 $\downarrow \qquad \qquad \downarrow$   
 $20 \log 2 \quad - \quad 0$


$$20 \log \left| \frac{V_o}{V_{in}} \right| = 40 \log \left| 1 + j \frac{\omega}{\omega_b} \right| - 20 \log \left| \frac{\omega}{\omega_b} \right|$$

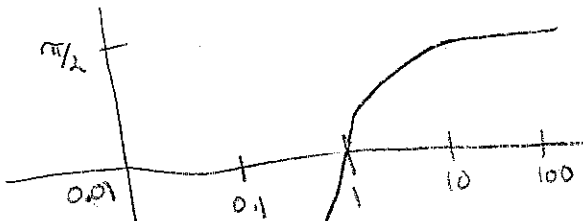$\uparrow$  Kicks in when  $\frac{\omega}{\omega_b} > 1$        $\uparrow$  active at all  $\omega/\omega_b$



$$\left[ \sqrt{2} e^{j\frac{\pi}{4}} \right]^2 = 2 e^{j\frac{\pi}{2}}$$
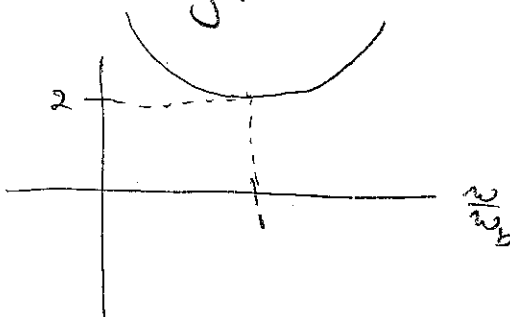
$$\frac{2}{\omega_b} = \frac{(1+j)^2}{j} = \frac{(\sqrt{2} \angle \frac{\pi}{4})^2}{\angle \frac{\pi}{2}} = 2 \angle 0$$



$V_o(t): \sum_b i = 0 = \frac{V_{in}}{R} + \frac{1}{L} \int (V_{in} - 0) dt + \frac{V_a}{R}$


$\sum_a i = 0 = \frac{0 - V_a}{R} + \frac{1}{L} \int (V_{out} - V_a) dt$

$V_a$  - don't need

$$\left. \begin{aligned} \frac{1}{R} \frac{dV_{in}}{dt} + \frac{1}{L} V_{in} + \frac{1}{R} \frac{dV_a}{dt} &= 0 \\ -\frac{1}{R} \frac{dV_a}{dt} + \frac{1}{L} (V_{out} - V_a) &= 0 \end{aligned} \right\} \begin{aligned} + \frac{1}{R} \frac{dV_a}{dt} + \frac{1}{L} V_{in} + \frac{1}{L} (V_{out}) - \frac{1}{L} \left[ -V_{in} - \frac{R}{L} \int V_{in} dt \right] &= 0 \\ \frac{1}{R} \frac{dV_{in}}{dt} + \frac{2}{L} V_{in} + \frac{R}{L^2} \int V_{in} dt &= -\frac{1}{L} V_{out} \\ -\frac{R}{L} V_{out} &= \frac{dV_{in}}{dt} + \frac{2R}{L} V_{in} + \left(\frac{R}{L}\right)^2 \int V_{in} dt \end{aligned}$$

$V_{in} = ac$  or  $dc$  or any signal

If  $V_{in}$  is  $DC$ ,

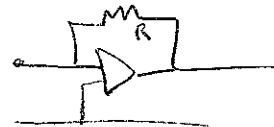


$\frac{V_a}{V_{in}} = \frac{-R}{0}$

$V_{in} = V_m \cos \omega t$

$= -\omega V_m \sin \omega t + \frac{\partial R}{L} V_m \cos \omega t + \left(\frac{R}{L}\right)^2 \frac{V_m}{\omega} \sin \omega t \Big|_{-\infty}^{\infty}$  \* need initial conditions



Diode


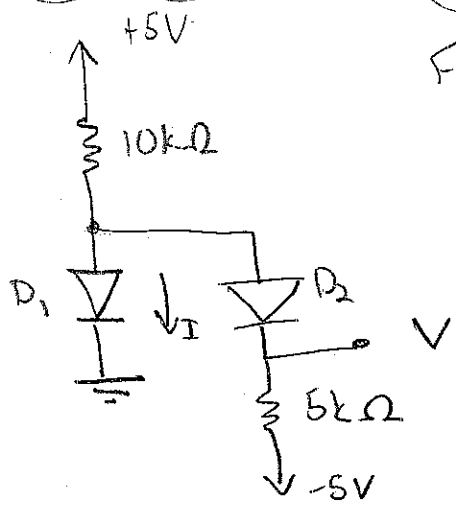


Find  $I, V$

$D_1$  on,  $D_2$  on


$D_1$  off

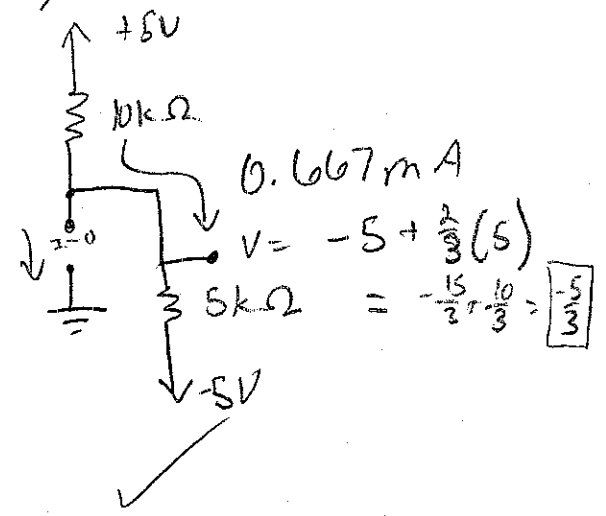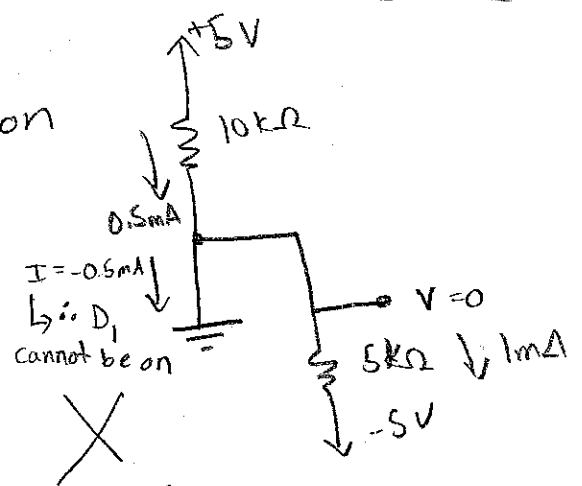

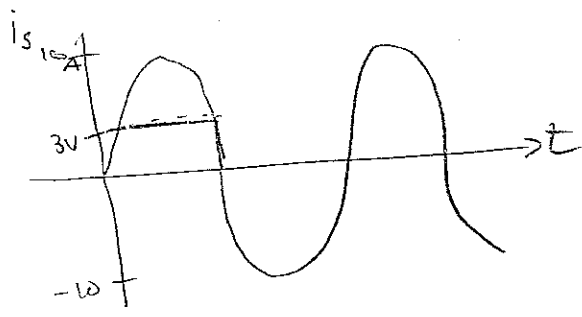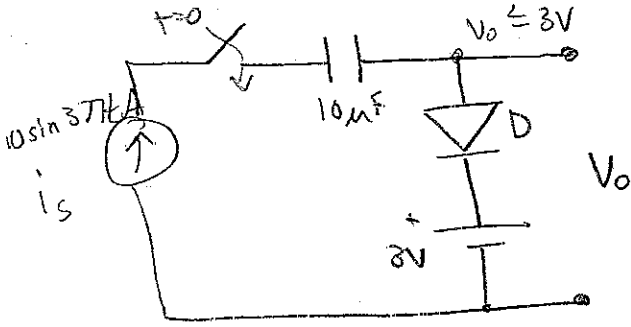

@  $t=0, V_c=0$
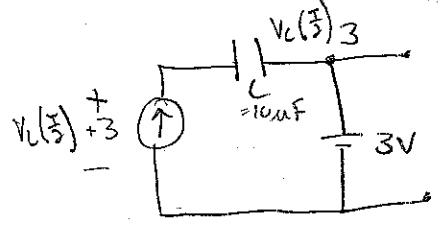
$$V_c(t) = \frac{1}{C} \int i_s dt \quad (\text{for } D \text{ on})$$



$$V_c(t) = -\frac{1}{C} \int_0^{T/2} -\frac{10}{377} \cos 377t \Big|_0^{T/2}$$

$$T = \frac{1}{f} = \frac{2\pi}{\omega} = \frac{2\pi}{2(377)} = \frac{\pi}{2}$$

$$V_c(t) = \frac{10^4}{377C} \left[ \cos 377 \left( \frac{2\pi}{2 \cdot 377} \right) = 1 \right]$$

$$= \frac{20}{377C} = \frac{2(10^4)}{377} \text{ V whenever } i_s \text{ is positive}$$