

Exam 2 Review

Ch. 5 Op Amps

Ch 6 L, C (not 6.4, 6.5)



Ch 7 First order, homogeneous & particular w/DC sources

* Impedance $Z(s)$ to find homogeneous response



Remove V_S $V_S = 0$ S.C.

Remove I_S $I_S = 0$ O.C.


Sequential Switching + impedance

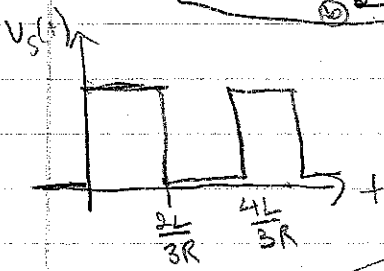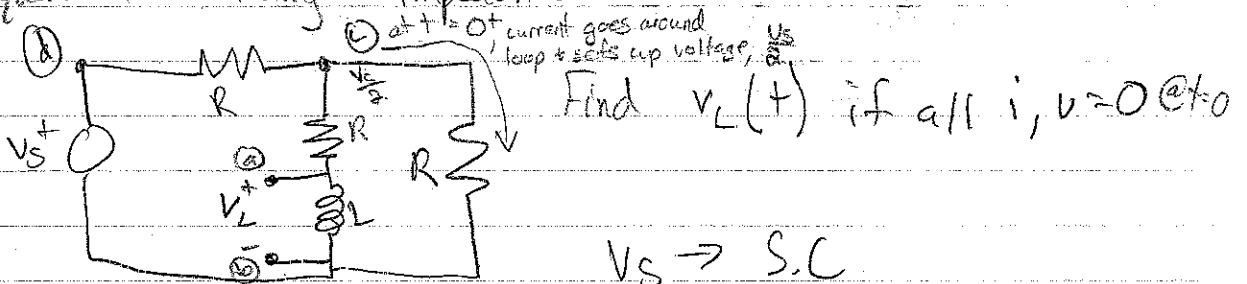

$V_S \rightarrow$ S.C

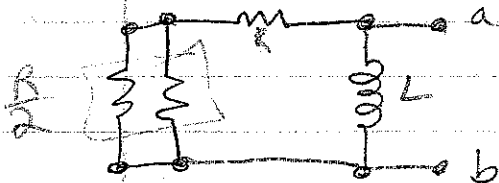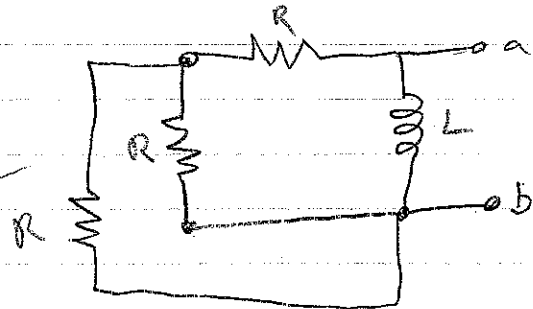

\Rightarrow

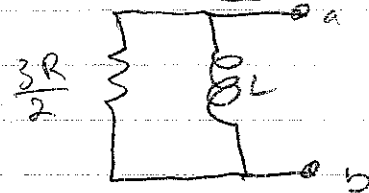

$$Z(s) = \frac{sL \left(\frac{3R}{2} \right)}{sL + \frac{3R}{2}} = \frac{sL(3R)}{2sL + 3R}$$


← zero used for current
← poles used for voltage

$$V_{Lh} = A e^{-\frac{3R}{2L}t}$$

$s = -\frac{3R}{2L}$

$$V_L = V_{Lh} + V_{Lp} = A e^{-\frac{3R}{2L}t} + 0$$

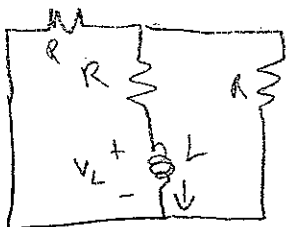$\Rightarrow V_L(0^+) = A = \frac{V_S}{2}$
 $V_L = \frac{V_S}{2} e^{-\frac{3R}{2L}t}$ $0 < t < \frac{2L}{3R}$



$$\frac{2L}{3R} < \frac{L}{3R}$$


$$V_L = B e^{-\frac{3R}{2L}t}$$

(b/c homogeneous doesn't change t in this case, particular is still 0)

$$V_L \left(\frac{2L}{3R} \right) = B = ?$$

$$t = \frac{2L}{3R}$$
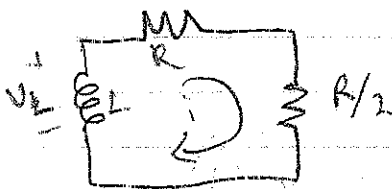
$$V_L = L \frac{di}{dt} @ \frac{2L}{3R}, \quad V_L = \frac{V_S}{2} e^{-1}$$



$$i = -\frac{1}{L} = \frac{V_S}{2} e^{-1} \frac{1}{3R/2}$$

$$V_L = \frac{V_S}{2} e^{-1}$$