

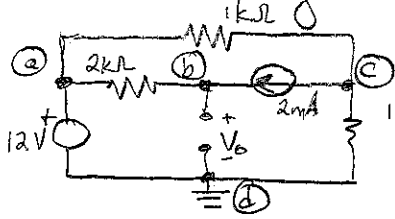


① Find  $V_o$  using Thevenin's Theorem

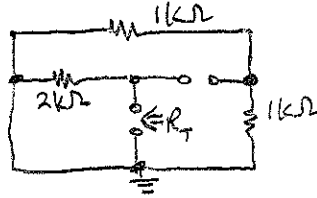

By inspection, the 2mA source forces 2mA through the 2kΩ resistor.
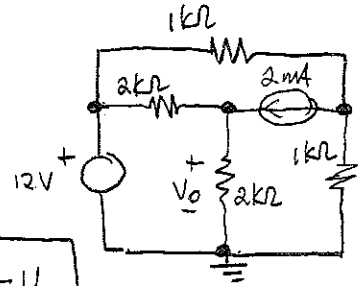
$$V_a = 12V \Rightarrow V_o = 12 + (2k)(2m) = 16V = V_{oc} = U_T$$



The 2 1kΩ resistors are shorted by removing the 12V source  $\Rightarrow$  S.C.  
Thus  $R_T = 2k\Omega$

By voltage divider,  
 $V_o = \frac{R_L}{R_T + R_L} U_T$

$$\Rightarrow V_o = \frac{2}{2+2} (16) = 8V$$

② Find  $i(t)$ .

$Z(s) = sL + R + \frac{1}{sC} = \frac{s^2 LC + sRC + 1}{sC}$  ; use Zeros of  $Z(s) = 0$ .

$$Z(s) = 0 \Rightarrow s^2 + s \frac{R}{L} + \frac{1}{LC} = 0 \Rightarrow s^2 + s \left(\frac{3}{1/3}\right) + \frac{1}{(1/3)(3/8)} = 0$$

$$s^2 + 9s + 8 = 0 \Rightarrow (s+1)(s+8) = 0 \text{ or } s = -1, -8$$


$$i(t) = A_1 e^{-t} + A_2 e^{-8t} \text{ need ICs to find } A_1, A_2$$

$$i(0^+) = i_L(0^+) = i_L(0^-) = V/R = 12/3 = 4A ; \frac{di}{dt} \Big|_{t=0^+} = \frac{V_L(0^+)}{L} \quad V_L(0^+) = -V_R(0^+) - V_C(0^+)$$

$$i(0^+) = A_1 + A_2 = 4$$

$$\frac{di}{dt} \Big|_{t=0^+} = -A_1 - 8A_2 = \frac{-12}{1/3} = -36 \Rightarrow A_1 = -4/7, A_2 = 32/7$$
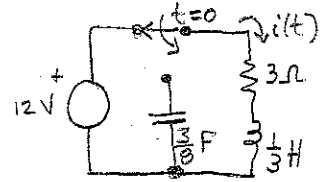
$$\therefore i(t) = \frac{1}{7} (-4e^{-t} + 32e^{-8t}) u(t) \text{ A}$$



$V_C(0^+) = V_C(0^-) = 0$   
 $V_R(0^+) = L(0^+)R = i(0^+)R$   
since  $i = i_L$  instantaneously


$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases} \Rightarrow \text{true for } t > 0$$

③ Find  $V_o$ . Use loop current method. <sup>(a)</sup>  $I_1 = 4$ , <sup>(b)</sup>  $I_2 = 2V_x$

$$(1) 1I_3 + 1I_3 + j1(I_2 + I_3) + 1(I_3 + I_2 - I_1) - j1(I_3 - I_1) = 0$$

$$(2) V_x = -j1(I_1 - I_3) = -j1(4 - I_3) ; \text{ sub in (a), (b) to (1), (2) } \Rightarrow$$
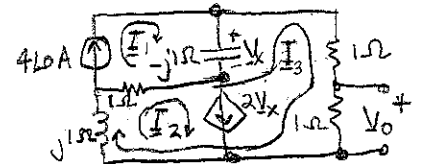
$$\begin{cases} (1) I_3(3) + 2V_x(1+j1) + 4(-1+j1) = 0 \\ (2) V_x = -j1(4 - I_3) \end{cases} \text{ solve simultaneously } \Rightarrow$$



$$I_3 = \frac{4 + j12}{5}$$

$$\Rightarrow V_o = \frac{4}{5} + j\frac{12}{5}$$



④ Sketch magnitude of transfer function  $G_V(j\omega) = \frac{V_o}{V_i}(j\omega)$

Identify type of filter. By voltage divider,

$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}, \text{ where } Z_1 = j\omega L$$


$$Z_2 = \frac{R/j\omega C}{R + j\omega C} = \frac{R}{1 + j\omega RC}$$
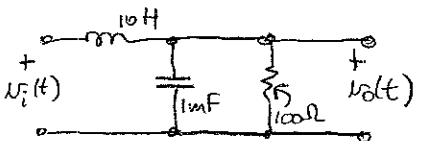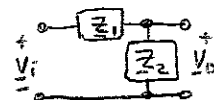
$$\text{so } \frac{V_o}{V_i} = \frac{R}{j\omega L + \frac{R}{1 + j\omega RC}} = \frac{R}{R + j\omega L - \omega^2 RL C} = \frac{100}{100 + j\omega 10 - \omega^2} = \frac{1}{1 + j\frac{\omega}{10} + (j\frac{\omega}{10})^2} = \frac{V_o}{V_i} \text{ LPF}$$



5) Sketch magnitude of transfer function  $G_V(j\omega) = \frac{V_o}{V_i}(j\omega)$ .  
 Identify the type of filter.

$$Z_1 = R_1 || C = \frac{R_1 j\omega C}{R_1 + j\omega C}$$

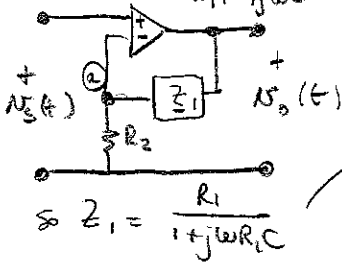

$$\text{so } Z_1 = \frac{R_1}{1 + j\omega R_1 C}$$

$$\sum_i i = 0 = \frac{V_o - V_s}{Z_1} - \frac{V_s}{R_2} \Rightarrow V_o = \left(1 + \frac{Z_1}{R_2}\right) V_s$$

$$\text{so } G_V = \frac{V_o}{V_s} = \frac{R_2 + R_1/(1 + j\omega R_1 C)}{R_2} = \frac{R_1 + R_2 + j\omega R_1 R_2 C}{R_2 + j\omega R_1 R_2 C}$$

Ok:  $\omega \rightarrow 0$  (dc) :  $C \rightarrow \text{o.c.} \Rightarrow$  non-inverting opamp configuration ✓  
 $\omega \rightarrow \infty$  (high freq) :  $C \rightarrow \text{s.c.} ; R_1$  short circuited  $\Rightarrow$  buffer configuration ✓

∴ All-pass filter

