

1.44, 1.53, 1.68,
1.77, 2.42, 2.56

Engineering 72
Electronic Circuit Analysis
Assignment 2 Solutions

LAM
2005

1. (1.44) Amplifier transfer function $v_o = 10 - 5(v_i - 2)^2$ for $2 \leq v_i \leq v_o + 2$ (otherwise saturation)


a. Sketch transfer function

$v_i \leq 2V, v_o = 10V$

Upper limit: $v_i = v_o + 2 : v_o = 10 - 5v_o^2$

or $v_o = 1.32V \Rightarrow v_i = 3.32V$

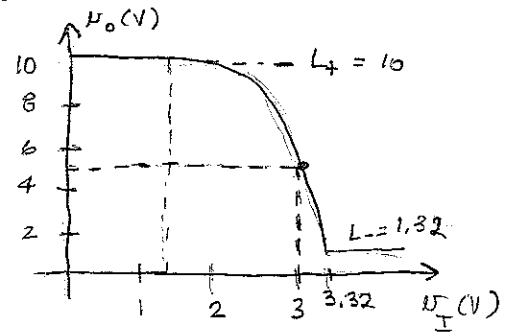Use computer to obtain intermediate values



b. What v_i bias is required for dc $v_o = 5V$?

$5 = 10 - 5(v_i - 2)^2 \Rightarrow v_i - 2 = 1$ or $v_i = 3V$

c. Small signal gain @ bias point = $\frac{\partial v_o}{\partial v_i} \Big|_{v_i=3V} = -5(2)(v_i - 2) = -10V/V$

d. Superimpose a sinusoidal input on dc

$\Rightarrow v_i = v_i + v_i \cos \omega t = 3 + v_i \cos \omega t \Rightarrow v_o = 10 - 5(3 + v_i \cos \omega t - 2)^2$


$v_o = 10 - 5[1 + 2v_i \cos \omega t + v_i^2 \cos^2 \omega t] = 5 - 10v_i \cos \omega t - 5v_i^2 (\frac{1}{2})(1 + \cos 2\omega t)$

$\therefore v_o = \underbrace{(5 - 2.5v_i^2)}_{(dc)} - \underbrace{10v_i \cos \omega t}_{(fundamental)} - \underbrace{2.5v_i^2 \cos 2\omega t}_{(2^{nd} harmonic)}$ 1% distortion $\frac{2.5v_i^2}{10v_i} = 0.01$
 $\Rightarrow v_i = \frac{10(0.01)}{2.5} = 40mV$

2. (1.53) Design voltage amplifier to be driven from signal source w/ 10mV peak amplitude & source $R_s = 10k\Omega$ to supply 3V peak output across $R_L = 1k\Omega$.

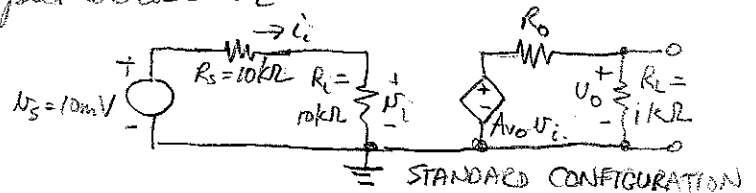a. Voltage gain from source to load?

$\frac{v_o}{v_s} = \frac{3V}{0.01V} = 300V/V$



b. Smallest R_i allowed for i_{peak} from source = 0.1μA :

$\therefore R_i = 90k\Omega$

Current gain: $\frac{i_o}{i_i} = \frac{v_o/R_L}{i_i} = \frac{3mA}{0.1\mu A} = 30(10^6) A/A$

Power gain: $\frac{v_o^2/R_L}{P_s i_i} = \frac{3^2/1k}{(10m)(0.1\mu)} = 9(10^6) W/W$ (includes P_{diss} by source R_s)

c. If peak value of O.C. output voltage $A_{vo}v_i$ is limited to 5V, find R_o max.

$5(\frac{R_L}{R_o + R_L}) = 3 \Rightarrow R_o = \frac{2}{3}R_L = 667\Omega$ (larger $R_o \Rightarrow v_o < 3V$)


d. Given R_i & R_o in b & c, what is O.C. voltage gain $\frac{v_o}{v_i} \Big|_{R_L \rightarrow \infty}$?

$300V/V = (\frac{90}{90+10})A_{vo}(\frac{1}{1+0.667}) \Rightarrow A_{vo} = 556V/V$

e. ↑ R_i to $1(10^6)$; ↓ R_o to $1(10^3)$, find achievable R_i, R_o , & A_{vo} .

$R_i = 100k\Omega, R_o = 100\Omega \Rightarrow 300V/V = (\frac{100}{100+10})(A_{vo})(\frac{1000}{1000+100}) = 363V/V$

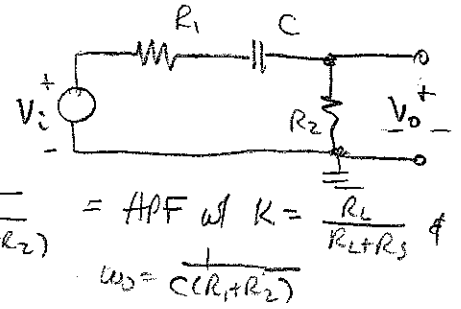3. 1.68 Find $T(s) = \frac{V_o(s)}{V_i(s)}$ & arrange in standard form
 HPF or LPF? High freq response? Corner freq. ω_0 ?
 Compute f_0 for $R_1 = 10k\Omega$, $R_2 = 40k\Omega$, $C = 0.1\mu F$.




Find $|T(j\omega_0)|$. $T(s) = \frac{R_2}{R_1 + R_2 + 1/sC} = \frac{R_2}{R_1 + R_2} \frac{s}{s + \frac{1}{C(R_1 + R_2)}}$ = HPF w/ $K = \frac{R_2}{R_1 + R_2}$ &
 $\omega_0 = \frac{1}{C(R_1 + R_2)}$

$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi C(R_1 + R_2)} = \frac{1}{2\pi(10^{-7})(50)(10^3)} = 31.8 \text{ Hz}$

Then $|T(j\omega_0)| = \frac{K}{\sqrt{2}} = \frac{40}{10+40} \left(\frac{1}{\sqrt{2}}\right) = 0.57 \text{ V/V}$

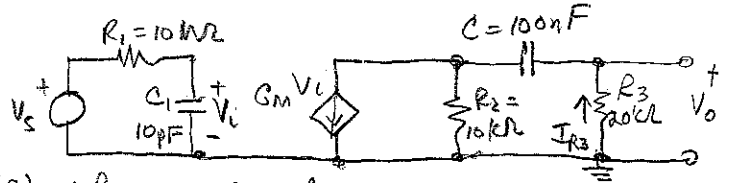4. 1.77 Find $T_i(s) = \frac{V_i(s)}{V_s(s)}$ & corresponding ω_0 .
 Find $T_o(s) = \frac{V_o(s)}{V_i(s)}$ & corresponding ω_0 .




Put TFs in standard form & find overall $T(s)$ w/ Bode plot & BW.

$V_o = -R_3 I_{R_3} = \frac{-R_2 R_3}{R_2 + R_3 + 1/sC} G_m V_i$; $V_i = \frac{1/sC_1}{R_1 + 1/sC_1} V_s$

so $T_i(s) = \frac{1}{1 + sR_1C_1}$; $T_o(s) = \frac{-sR_2R_3C}{1 + s(R_2 + R_3)C}$; $T(s) = \frac{-sR_2R_3C}{[1 + sR_1C_1][1 + s(R_2 + R_3)C]}$

Use Matlab to plot. BW is freq difference between 2 points
 where $|T(j\omega)| = \frac{1}{\sqrt{2}} |T(j\omega_0)|$

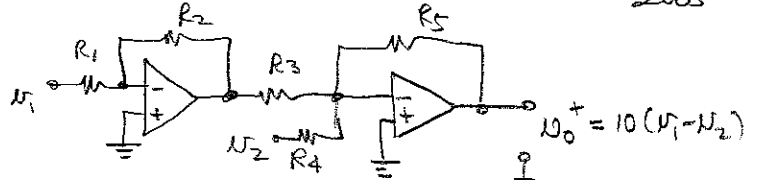- 5) 2.42 Want to obtain difference between
 $v_1 = 3 \sin(2\pi 60t) + 0.01 \sin(2\pi 1000t)$
 and $v_2 = 3 \sin(2\pi 60t) - 0.01 \sin(2\pi 1000t)$



Design circuit w/ 2 opamps & mostly 10k Ω resistors
 Provide gain of 10 @ 1000 Hz.

$R_1 = R_2 = R_3 = R_4 = 10k\Omega$; $R_5 = 100k\Omega$


$$v_o = \frac{R_2}{R_1} \cdot \frac{R_5}{R_3} v_1 - \frac{R_5}{R_4} v_2$$
 want $\frac{R_2}{R_1} \frac{R_5}{R_3} = \frac{R_5}{R_4} = 10 \Rightarrow$

$$v_o = 10v_1 - 10v_2 = 10(0.02) \sin 2\pi(1000t) = 0.2 \sin(2\pi 1000t)$$

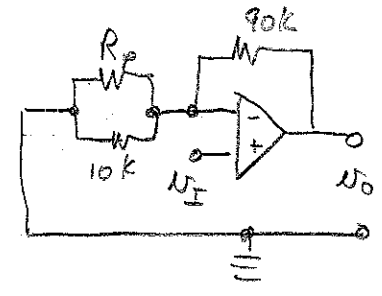- 6) 2.56 $A = 50V/V$ $G = 1 + \frac{R_2}{R_1} = 10 V/V$
 $R_1 = 10k\Omega \Rightarrow R_2 = 90k\Omega$

Compensated circuit:

$$G = \frac{v_o}{v_i} = \frac{1 + R_2/R_1}{1 + \frac{1}{A}(1 + R_2/R_1)} = \frac{1 + 90/10}{1 + \frac{1}{50}(1 + 90/10)} = \frac{10}{1.2} = 8.33 V/V$$



Add resistor in parallel w/ R_1 to compensate for drop in gain

$$R_p : 10 = \frac{1 + (\frac{90}{10} + \frac{90}{R_p})}{1 + \frac{1}{50}(1 + \frac{90}{10} + \frac{90}{R_p})} \Rightarrow R_p = 36k\Omega$$

If $A = 100$ $G_{uncomp} = \frac{1 + 90/10}{1 + \frac{1}{100}(1 + 90/10)} = 9.09 V/V$

$$G_{comp} = \frac{1 + 90/10 + 90/36}{1 + \frac{1}{100}(1 + \frac{90}{10} + \frac{90}{36})} = 11.1 V/V$$