

2.65, 2.69, 2.75
2.123, 3.4, 3.9,
3.15

Engineering 72
Electronic Circuit Applications
Assignment 3 Solution

LAW
2005

1. Q2.65 In difference amplifier, all $R = 100\text{ k}\Omega \pm x\%$. Find worst case CMRR & evaluate for $x = 0.1, 1, 8.5$.

$$\text{eq. 2.19 } A_{cm} = \frac{1}{1+R_3/R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) ; A_{cm\max} @ \frac{R_2}{R_1} \min, \frac{R_3}{R_4} \min$$

$$\text{so let } \frac{R_2}{R_1} = \frac{R_3}{R_4} = \frac{100k(1-x/100)}{100k(1+x/100)} \quad \text{Then } A_{cm\max} = \frac{1}{1+\frac{1-x/100}{1+x/100}} \left[1 - \left(\frac{1-x/100}{1+x/100}\right)^2\right]$$

$$\boxed{A_{cm\max} = \frac{2x}{x+100}} \quad \text{so let } R_1 = R_4 = 100(1+\frac{x}{100})k \\ R_2 = R_3 = 100(1-\frac{x}{100})k$$

(is very close to 1).

$$\text{CMRR} = 20 \log \left| \frac{A_d}{A_{cm}} \right|$$


$$\text{from eq. 2.21, } A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = \frac{1+\frac{x}{100}}{1-\frac{x}{100}} \left(1 + \frac{\frac{x}{100}}{1+\frac{x}{100}}\right)$$

Plug into computer/calculator. Check using approx: $A_{cm} \approx \frac{x}{50}$, $A_d \approx 1$.

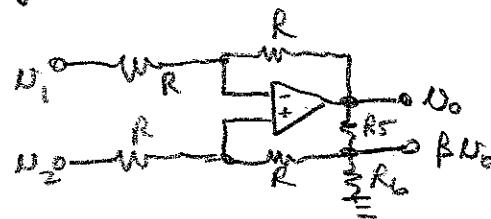2. Q2.68 $R_5, R_6 \ll R \Rightarrow \beta \approx \frac{R_6}{R_5+R_6}$

$$\text{Show } A_d = \frac{U_o}{U_{id}} = \frac{1}{1-\beta}.$$

Obtain values for $A_d = 10 \text{ V/V}$, $R_i = 2 \text{ M}\Omega$.



Use superposition

$$\text{if } U_2 = 0, \text{ by V+}, U_+ = \frac{\beta U_{o1}}{2} = U_- \quad \text{if } \sum i = 0 = \frac{U_1 - U_-}{R} + \frac{U_0 - U_-}{R} \Rightarrow U_{o1} = \frac{U_1}{\beta-1}$$

$$\text{if } U_1 = 0, \text{ by V+}, U_- = \frac{\beta U_2}{2} = U_+ \quad \text{if } \sum i = 0 = \frac{U_2 - U_+}{R} + \frac{\beta U_0 - U_+}{R} \Rightarrow U_{o2} = \frac{-U_2}{\beta-1}$$

$$\text{so } U_o = U_{o1} + U_{o2} = \frac{1}{1-\beta} (U_2 - U_1) = A_d (U_2 - U_1) \Rightarrow \text{for } A_d = 10, \beta = 0.9 = \frac{R_6}{R_5+R_6}$$

$$R_{id} = 2R = 2 \text{ M}\Omega \Rightarrow \boxed{R = 1 \text{ M}\Omega}$$

$$R_5 + R_6 < \frac{1}{100} \Rightarrow \text{choose } \boxed{(R_5 + R_6 \in 10 \text{ k}\Omega)}$$

3. Q2.75 $2R_1 = 10 \text{ k}\Omega$, $R_2 = R_3 = R_4 = 100 \text{ k}\Omega$.

(see Fig. 2.20 b in text)

For ideal components, find A_d , A_{cm} , & CMRR

$$\boxed{A_{cm} = 0} \quad (\text{how we choose the relationships between the } R_i)$$

$$\text{eq. 2.22} \Rightarrow A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = 1 \left(1 + \frac{100}{5}\right) = \boxed{21 \text{ V/V} = A_d}$$

For $\pm 1\%$ resistors, use results of 2.65 $\Rightarrow A_{cm} = \frac{2x}{x+100} \neq A_d = \frac{1+0.01}{1-0.01} \left(1 + \frac{1+0.01}{1-0.01}\right)$

use calculator; result should be close to estimate of $A_{cm} \approx \frac{1}{50}$, $A_d \approx 21$


$$\text{so CMRR} \approx 20 \log_{10} \left(\frac{21}{1/50} \right) \approx 60 \text{ dB}$$

$$\text{if } 2R_1 = 1 \text{ k}, A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = 201 \text{ V/V} ; A_{cm} \text{ still} \approx \frac{1}{50} \Rightarrow \boxed{\text{CMRR} \approx 80 \text{ dB}}$$

\Rightarrow Obtain higher CMRR if we ↑ gain in stage 1 of the amplifier

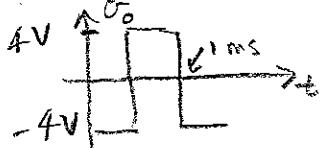
4. (2.123) $R = 10\text{k}\Omega$, $C = 0.1\mu\text{F}$

For triangle input w/ $\pm 1\text{V p-p}$ @ 1kHz, find V_o .



$$f = 1\text{kHz}, V_p = 4\text{V}, V_{avg} = 0$$

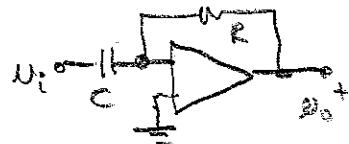For $V_p = 10\text{V}$, need to $\uparrow R$ by factor of 2.5 $\Rightarrow R = 25\text{k}\Omega$.



$$C \frac{dV_i}{dt} + \frac{V_o}{R} = 0 \Rightarrow V_o = -RC \frac{dV_i}{dt}$$

For 1V sin wave input, output is also a sin wave (shifted)

$$\text{Using 2.44a, } V_o = -RC \frac{dV_i}{dt} = -10^{-3} (2\pi \cdot 10^3) \cos(2\pi \cdot 10^3 t) \Rightarrow \text{peak} = 2\pi \text{ shifted by } \pi \text{ (neg sign)} + \frac{\pi}{2} \text{ or } \frac{3\pi}{2} = -\pi/2$$



$$\text{Using 2.44a } \frac{V_o}{V_i} = -j\omega RC \Rightarrow \text{again, } -\pi/2 \text{ phase shift}$$

& peak of $2\pi f R C = 2\pi$



Third way seems redundant -- like the 1st.

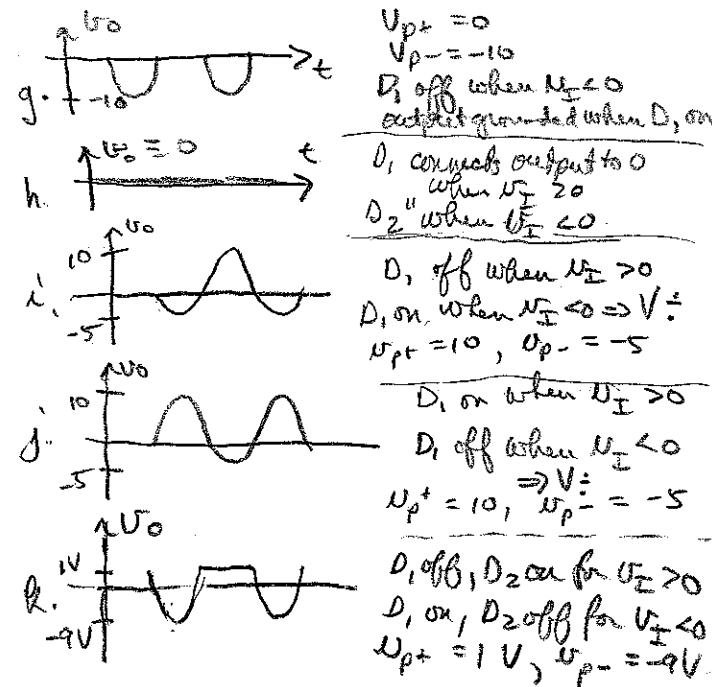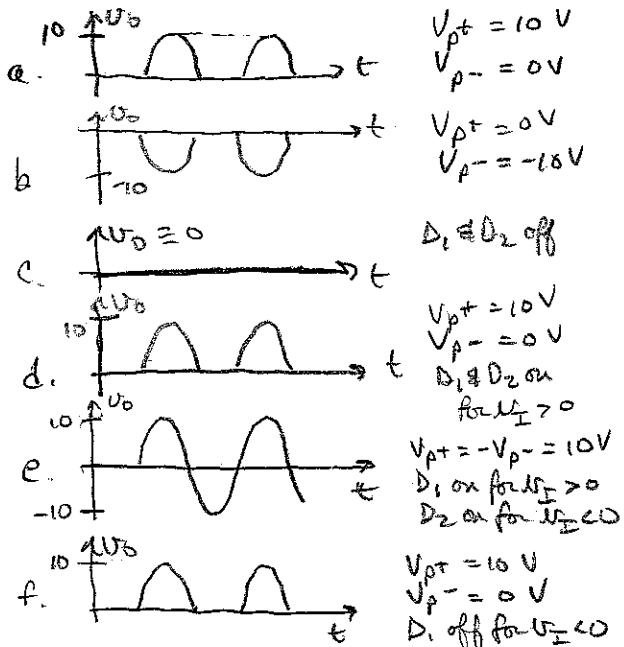5. (3.4)


$f = 1\text{kHz}$
for all
non-zero
waveforms.



6. (3.9) a. D_1 & D_2 on.

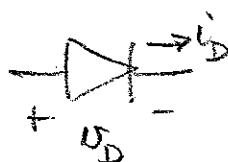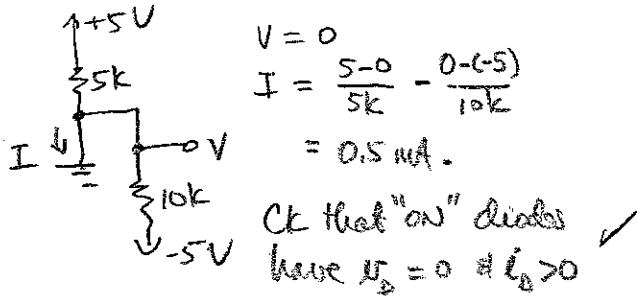

b. D_1 off; D_2 on.

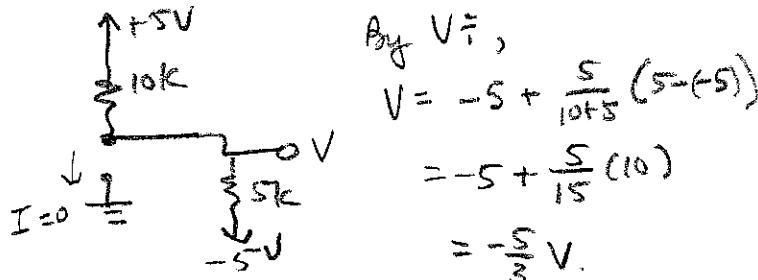

Check for D_2 on as input a & D_1 off ($i_D = 0, V_D < 0$)

7. 3.15 done in class.